

**LECTURE NOTES  
ON**

**Basic Electrical & Electronics Engineering  
(ESC-S101)**

**B. Tech. I<sup>st</sup> Semester**

**OMPAL  
Assistant Professor**



**ELECTRONICS & COMMUNICATION ENGINEERING  
UIET, CSJM UNIVERSITY  
KANPUR-208024**

# Unit-1

## Sinusoidal Steady State Analysis

1.1 Characteristics of Sinusoidal

1.2 Phasors

1.3 Phasor Relationships for R, L and C

1.4 Impedance

1.5 Parallel and Series Resonance

1.6 Examples for Sinusoidal Circuits Analysis

# Sinusoidal Steady State Analysis

- Any steady state voltage or current in a linear circuit with a sinusoidal source is a sinusoid
  - All steady state voltages and currents have the same frequency as the source
- In order to find a steady state voltage or current, all we need to know is its magnitude and its phase relative to the source (we already know its frequency)
- We do not have to find this differential equation from the circuit, nor do we have to solve it
- Instead, we use the concepts of phasors and complex impedances
- Phasors and complex impedances convert problems involving differential equations into circuit analysis problems

❖ Focus on steady state;      Focus on sinusoids.

# Sinusoidal Steady State Analysis

## 1.1 Characteristics of Sinusoidal

Key Words:

Period:  $T$ ,

Frequency:  $f$ , Radian frequency  $\omega$


Phase angle

Amplitude:  $V_m$   $I_m$

# Sinusoidal Steady State Analysis

## 1.1 Characteristics of Sinusoidal

$$v(t) = V_m \sin \omega t$$

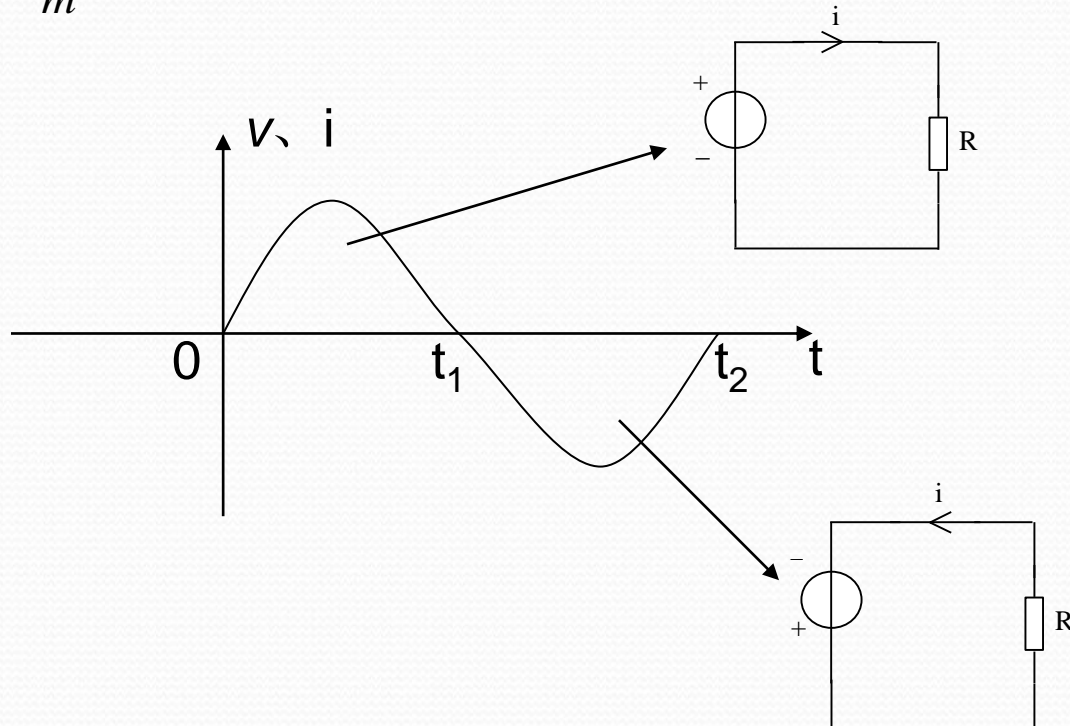

Both the polarity and magnitude of voltage are changing.

# Sinusoidal Steady State Analysis

## 1.1 Characteristics of Sinusoidal

**Period:  $T$**  — Time necessary to go through one cycle. (s)


**Frequency:  $f$**  — Cycles per second. (Hz)

$$f = 1/T$$

**Radian frequency(Angular frequency):  $\omega = 2\pi f = 2\pi/T$**  (rad/s)

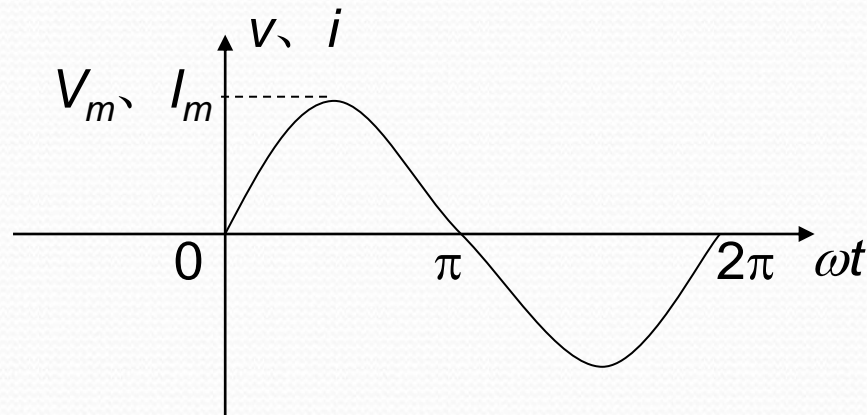**Amplitude:  $V_m$   $I_m$**

$$i = I_m \sin \omega t, \quad v = V_m \sin \omega t$$



## 1.1 Characteristics of Sinusoidal

**Effective Root Mean Square (RMS) Value of a Periodic Waveform** — is equal to the value of the direct current which is flowing through an R-ohm resistor. It delivers the same average power to the resistor as the periodic current does.

$$\frac{1}{T} \int_0^T i^2 R dt = I^2 R$$

→ Effective Value of a Periodic Waveform  $I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \sin^2 \omega t dt} = \sqrt{\frac{I_m^2}{T} \int_0^T \frac{1 - \cos 2\omega t}{2} dt} = \sqrt{\frac{1}{T} I_m^2 \cdot \frac{T}{2}} = \frac{I_m}{\sqrt{2}}$$


$$V_{eff} = \sqrt{\frac{1}{T} \int_0^T v^2 dt} = \frac{V_m}{\sqrt{2}}$$

## 1.1 Characteristics of Sinusoidal

### Phase (angle)

$$i = I_m \sin(\omega t + \varphi)$$

Phase  
angle

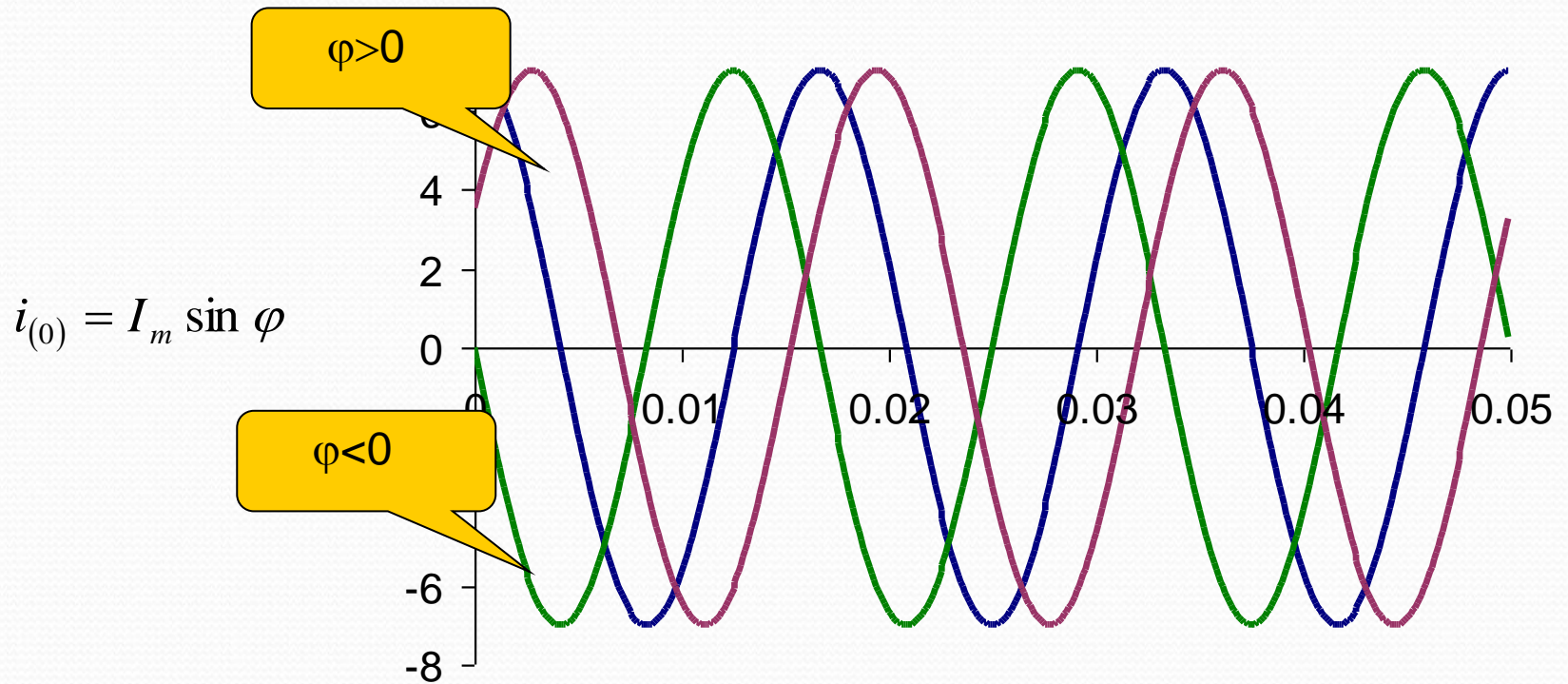



## 1.1 Characteristics of Sinusoidal

### Phase difference


$$v = V_m \sin(\omega t + \varphi_1) \quad i = I_m \sin(\omega t + \varphi_2)$$

$$\Delta\varphi = \varphi_v - \varphi_i = \omega t + \varphi_1 - (\omega t + \varphi_2) = \varphi_1 - \varphi_2$$


$\Delta\varphi = \varphi_1 - \varphi_2 > 0$  —  $v(t)$  leads  $i(t)$  by  $(\varphi_1 - \varphi_2)$ , or  $i(t)$  lags  $v(t)$  by  $(\varphi_1 - \varphi_2)$

$\Delta\varphi = \varphi_1 - \varphi_2 < 0$   $\frac{\varphi_2}{\varphi_1}$   $v(t)$  lags  $i(t)$  by  $(\varphi_2 - \varphi_1)$ , or  $i(t)$  leads  $v(t)$  by  $(\varphi_2 - \varphi_1)$
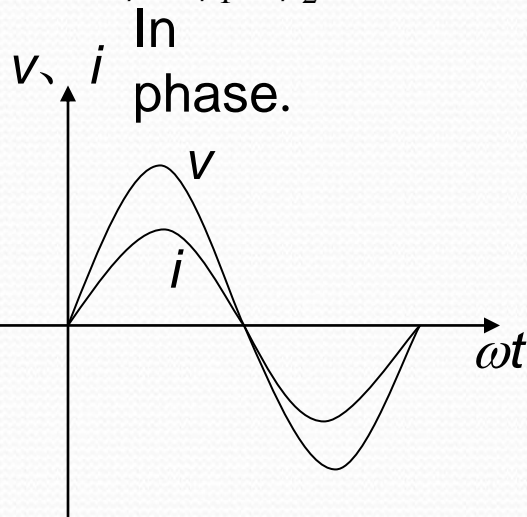
$$\Delta\varphi = \varphi_1 - \varphi_2 = 0$$



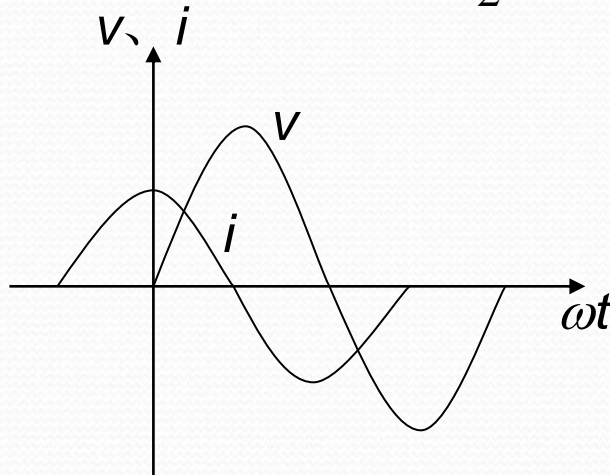
$$\Delta\varphi = \varphi_1 - \varphi_2 = \pm \frac{\pi}{2}$$



$$\Delta\varphi = \varphi_1 - \varphi_2 = \pi$$

Out of phase.

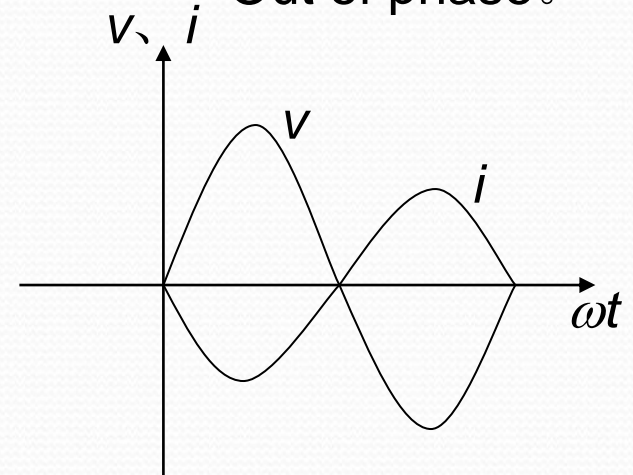

## 1.1 Characteristics of Sinusoidal

### Review

The sinusoidal waves whose phases are compared must:

- ① Be written as sine waves or cosine waves.
- ② With positive amplitudes.
- ③ Have the same frequency.

$360^\circ$  ——— does not change anything.

$90^\circ$  ——— change between sin & cos.

$180^\circ$  ——— change between + & -

$$* \sin \theta = \cos \left( \theta + \frac{2}{3} \pi \right) = \cos \left( \theta - \frac{\pi}{2} \right)$$

$$* \cos \theta = \sin \left( \theta + \frac{\pi}{2} \right)$$

## 1.1 Characteristics of Sinusoidal

### Phase difference

$$\text{P1.1, } v_1 = 220\sqrt{2} \sin(314t - 30^\circ) \quad v_2 = 220\sqrt{2} \cos(314t + 30^\circ)$$

Find  $\Delta\varphi = ?$

$$\begin{aligned} v_2 &= 220\sqrt{2} \cos(314t + 30^\circ) = 220\sqrt{2} \sin(314t + 30^\circ + 90^\circ) \\ &= 220\sqrt{2} \sin(314t + 120^\circ) \end{aligned}$$

$$\Delta\varphi = \varphi_1 - \varphi_2 = -30^\circ - 120^\circ = -150^\circ$$

$$\text{If } v_2 = -220\sqrt{2} \cos(314t + 30^\circ)$$

$$\begin{aligned} v_2 &= -220\sqrt{2} \cos(314t + 30^\circ) = 220\sqrt{2} \cos(314t + 30^\circ + 180^\circ) \\ &= 220\sqrt{2} \cos[360^\circ - (314t + 210^\circ)] \\ &= 220\sqrt{2} \sin(314t - 150^\circ + 90^\circ) \\ &= 220\sqrt{2} \sin(314t - 60^\circ) \end{aligned}$$

$$\Delta\varphi = \varphi_1 - \varphi_2 = -30^\circ + 60^\circ = 30^\circ$$

# Sinusoidal Steady State Analysis

## 1.1 Characteristics of Sinusoidal

### Phase difference

P1.2,

