

1.3 Phasor Relationships for R, L and C


Key Words:

I-V Relationship for R, L and C,

Power conversion

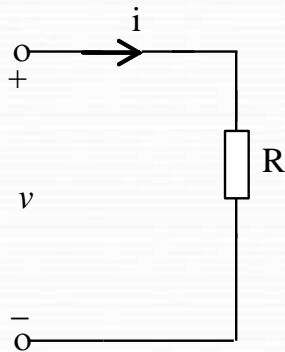1.3 Phasor Relationships for R, L and C

Resistor ● $v \sim i$ relationship for a resistor




Suppose $v = V_m \sin \omega t$

$$i = \frac{v}{R} = \frac{V_m}{R} \sin \omega t = I_m \sin \omega t$$

Relationship between RMS: $I = \frac{V}{R}$

Wave and Phasor diagrams:

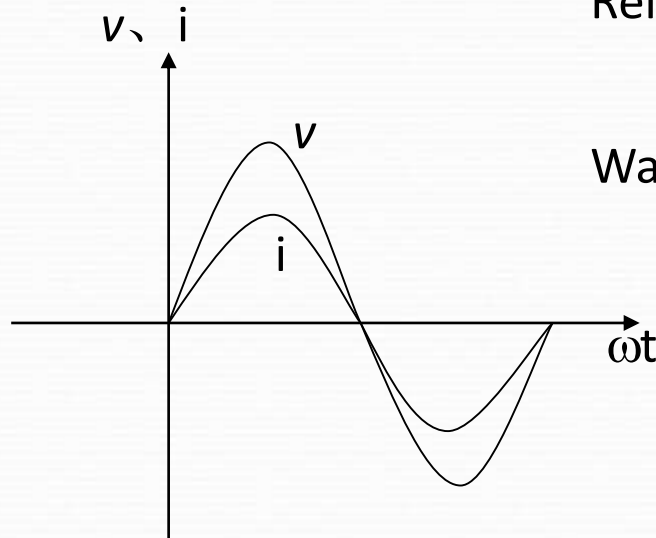

$$I = \frac{V}{R}$$

1.3 Phasor Relationships for R, L and C

Resistor ● Time domain → frequency domain


$$\begin{array}{l}
 v(t) = V_m \cos(\omega t + \theta) \quad V(t) = Ri(t) \\
 i(t) = I_m \cos(\omega t + \phi) \quad \longrightarrow \\
 \\
 V_m e^{j(\omega t + \theta)} = RI_m e^{j(\omega t + \phi)} \\
 V_m e^{j\theta} = RI_m e^{j\phi} \\
 V_m \angle \theta = RI_m \angle \phi \\
 \dot{V} = RI
 \end{array}$$

With a resistor $\vartheta = \phi$, $v(t)$ and $i(t)$ are in phase .

1.3 Phasor Relationships for R, L and C

Resistor

● Power

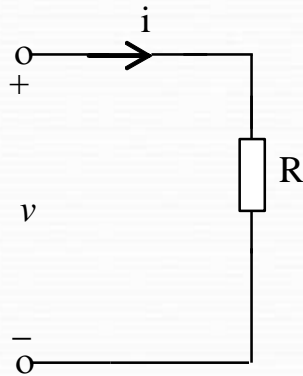

• Transient Power

$$p = vi = V_m \sin \omega t \cdot I_m \sin \omega t = I_m V_m \sin^2 \omega t$$


$$= \frac{I_m V_m}{2} (1 - \cos 2\omega t) = IV - IV \cos 2\omega t$$

Note: I and V are RMS values. $p > 0$

• Average Power

$$P = \frac{1}{T} \int_0^T p dt = \frac{1}{T} \int_0^T VI (1 - \cos 2\omega t) dt = VI$$

$$P = IV = I^2 R = \frac{V^2}{R}$$

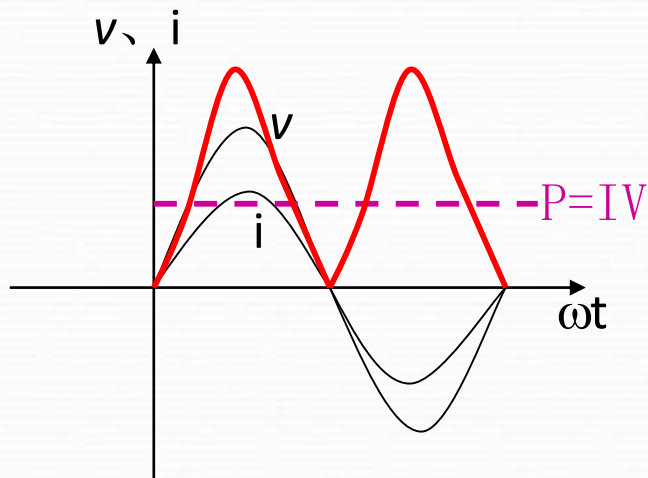

1.3 Phasor Relationships for R, L and C

Resistor

P1.4 , $v = 311 \sin 314t$, $R=10\Omega$, Find i and P .

$$V = \frac{V_m}{\sqrt{2}} = \frac{311}{\sqrt{2}} = 220(V)$$


$$I = \frac{V}{R} = \frac{220}{10} = 22(A)$$

$$i = 22\sqrt{2} \sin 314t \quad P = IV = 220 \times 22 = 4840(W)$$

1.3 Phasor Relationships for R, L and C

Inductor

● $v \sim i$ relationship

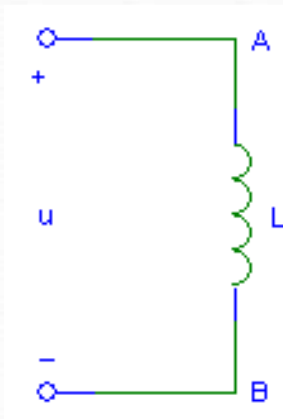

$$v = v_{AB} = L \frac{di}{dt}$$

Suppose $i = I_m \sin \omega t$


$$\begin{aligned} v &= L \frac{di}{dt} = L \frac{d(I_m \sin \omega t)}{dt} = I_m \omega L \cos \omega t \\ &= I_m \omega L \sin(\omega t + 90^\circ) \\ &= V_m \sin(\omega t + 90^\circ) \end{aligned}$$

$$i = \frac{1}{L} \int_{-\infty}^t v dt = \frac{1}{L} \int_{-\infty}^0 v dt + \frac{1}{L} \int_0^t v dt = i_0 + \frac{1}{L} \int_0^t v dt$$

1.3 Phasor Relationships for R, L and C

Inductor

● *v~i* relationship

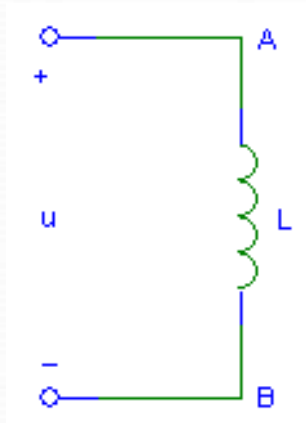

$$v = L \frac{di}{dt} = I_m \omega L \sin(\omega t + 90^\circ) = V_m \sin(\omega t + 90^\circ)$$

$$V_m = I_m \omega L$$

Relationship between RMS: $V = I \omega L$

$$I = \frac{V}{\omega L} \longrightarrow X_L = \omega L = 2\pi f L \quad (\Omega)$$


$$\longrightarrow X_L \propto f$$

For DC, $f = 0$, $\rightarrow X_L = 0$.

$\longrightarrow v(t)$ leads $i(t)$ by 90° , or $i(t)$ lags $v(t)$ by 90°

1.3 Phasor Relationships for R, L and C

Inductor

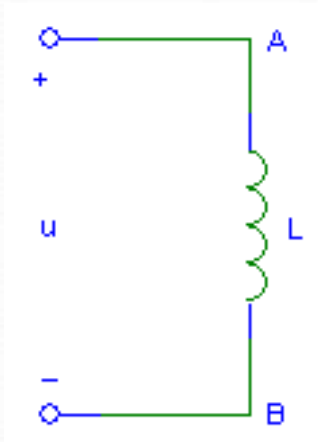● $v \sim i$ relationship

$$i(t) = I_m e^{j\omega t}$$

$$v(t) = L \frac{di}{dt} = I_m j\omega L e^{j\omega t} = j\omega L i(t)$$

Represent $v(t)$ and $i(t)$ as phasors: $\dot{V} = j\omega L \dot{I}$


$$\longrightarrow \dot{I} = \frac{\dot{V}}{j\omega L} = \frac{\dot{V}}{jX_L}$$

- The derivative in the relationship between $v(t)$ and $i(t)$ becomes a multiplication by $j\omega$ in the relationship between \dot{V} and \dot{I} .
- The time-domain differential equation has become the algebraic equation in the frequency-domain.
- Phasors allow us to express current-voltage relationships for inductors and capacitors in a way such as we express the current-voltage relationship for a resistor.


1.3 Phasor Relationships for R, L and C

Inductor ● $v \sim i$ relationship

Wave and Phasor diagrams:

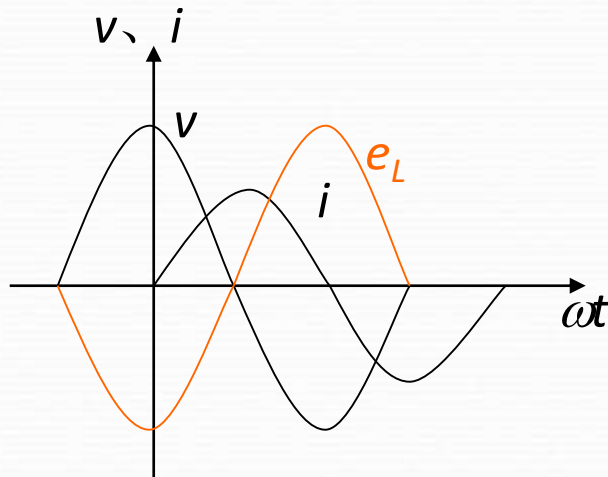

$$\dot{V} = jIX_L$$

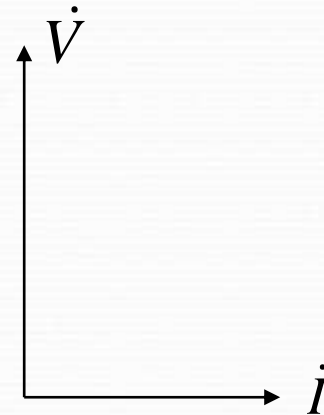

1.3 Phasor Relationships for R, L and C

Inductor

● Power


$$\begin{aligned}
 p &= vi = V_m \sin(\omega t + 90^\circ) I_m \sin \omega t = V_m I_m \cos \omega t \cdot \sin \omega t \\
 &= \frac{V_m I_m}{2} \sin 2\omega t = VI \sin 2\omega t
 \end{aligned}$$

Energy stored: $W = \int_0^t v i dt = \int_0^i L i di = \frac{1}{2} L i^2$

$$W_{\max} = \frac{1}{2} L I_m^2 = L I^2$$

Average Power $P = \frac{1}{T} \int_0^T p dt = \frac{1}{T} \int_0^T VI \sin 2\omega t dt = 0$

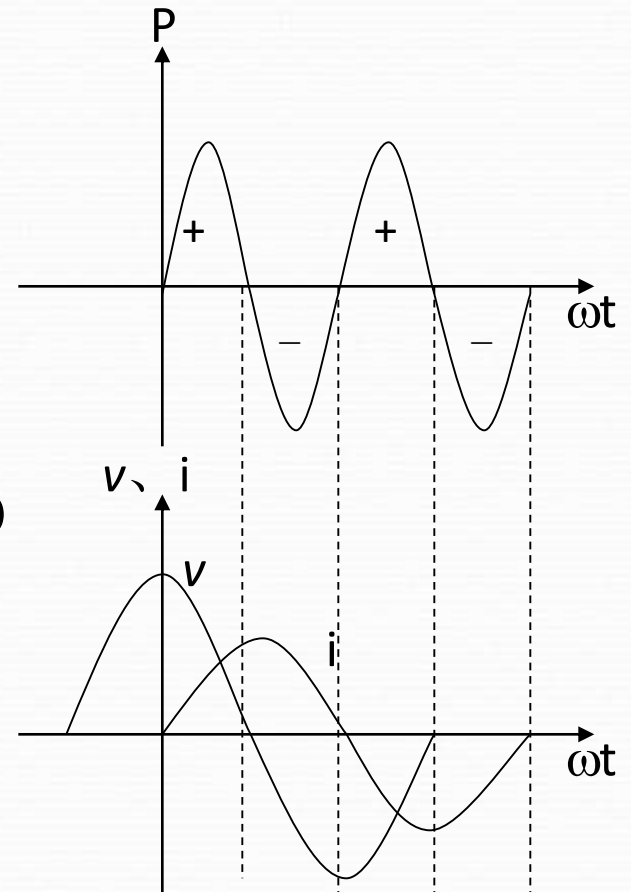Reactive Power $Q = IV = I^2 X_L = \frac{V^2}{X_L}$ (Var)



1.3 Phasor Relationships for R, L and C

Inductor

P1.5, $L = 10\text{mH}$, $v = 100\sin\omega t$, Find i_L when $f = 50\text{Hz}$ and 50kHz .

$$X_L = 2\pi fL = 2\pi \times 50 \times 10 \times 10^{-3} = 3.14(\Omega)$$

$$I_{50} = \frac{V}{X_L} = \frac{100/\sqrt{2}}{3.14} = 22.5(\text{A})$$

$$i_L(t) = 22.5\sqrt{2} \sin(\omega t - 90^\circ) \text{A}$$

$$X_L = 2\pi fL = 2\pi \times 50 \times 10^3 \times 10 \times 10^{-3} = 3140(\Omega)$$


$$I_{50k} = \frac{V}{X_L} = \frac{100/\sqrt{2}}{3.14} = 22.5(\text{mA})$$

$$i_L(t) = 22.5\sqrt{2} \sin(\omega t - 90^\circ) \text{mA}$$

1.3 Phasor Relationships for R, L and C

Capacitor

● $v \sim i$ relationship

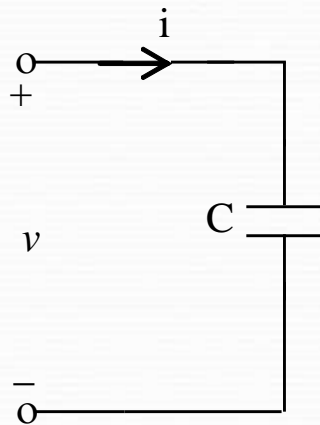

$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

Suppose: $v = V_m \sin \omega t$

$I_m = \omega C V_m$

$$i = \omega C V_m \cos \omega t = \omega C V_m \sin(\omega t + 90^\circ) = I_m \sin(\omega t + 90^\circ)$$

$$v = \frac{1}{C} \int_{-\infty}^t i dt = \frac{1}{C} \int_{-\infty}^0 i dt + \frac{1}{C} \int_0^t i dt = v_0 + \frac{1}{C} \int_0^t i dt$$

Relationship between RMS: $I = \omega C V = \frac{V}{\frac{1}{\omega C}} = \frac{V}{X_C}$

$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \quad (\Omega)$




$X_C \propto \frac{1}{f}$ For DC, $f = 0, \rightarrow X_C \rightarrow \infty$

$i(t)$ leads $v(t)$ by 90° , or $v(t)$ lags $i(t)$ by 90°

1.3 Phasor Relationships for R, L and c

Capacitor

● $v \sim i$ relationship

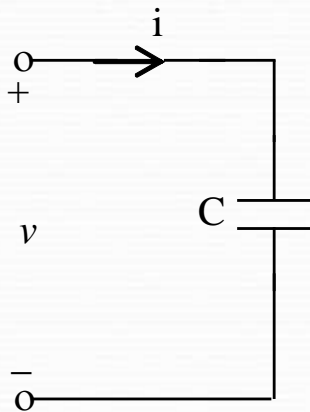

$$v(t) = V_m e^{j\omega t}$$

$$i(t) = C \frac{dv(t)}{dt} = C \frac{dV_m e^{j\omega t}}{dt} = j\omega C V_m e^{j\omega t}$$

$$\text{Represent } v(t) \text{ and } i(t) \text{ as phasors: } \dot{I} = j\omega C \dot{V} = \frac{\dot{V}}{jX_C}$$


- The derivative in the relationship between $v(t)$ and $i(t)$ becomes a multiplication by $j\omega$ in the relationship between \dot{V} and \dot{I} .
- The time-domain differential equation has become the algebraic equation in the frequency-domain.
- Phasors allow us to express current-voltage relationships for inductors and capacitors much like we express the current-voltage relationship for a resistor.

1.3 Phasor Relationships for R, L and C

Capacitor

● $v \sim i$ relationship

Wave and Phasor diagrams:

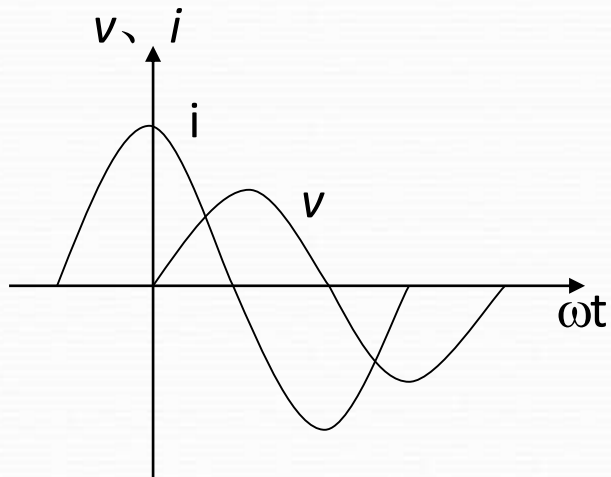

$$\dot{V} = -j\dot{I} X_C$$

The phasor diagram shows the relationship between the current phasor \dot{I} and the voltage phasor \dot{V} . The current phasor \dot{I} is on the positive vertical axis, and the voltage phasor \dot{V} is on the positive horizontal axis. This indicates that the voltage lags the current by 90° .

1.3 Phasor Relationships for R, L and C

Capacitor

● Power

$$p = vi = V_m \sin \omega t \cdot I_m \sin(\omega t + 90^\circ) = \frac{V_m I_m}{2} \sin 2\omega t = VI \sin 2\omega t$$


Energy stored:

$$W = \int_0^t v i dt = \int_0^v v \cdot C \cdot \frac{dv}{dt} \cdot dt = \int_0^v C v dv = \frac{1}{2} C v^2$$

$$W_{\max} = \frac{1}{2} C V_m^2 = C V^2$$

Average Power: $P=0$

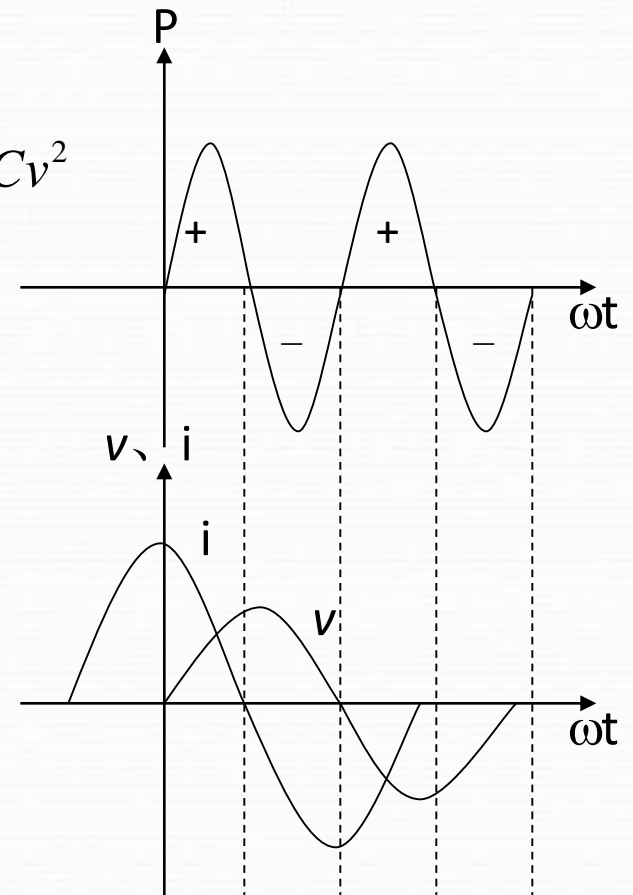Reactive Power $Q = IV = I^2 X_C = \frac{V^2}{X_C}$ (Var)



1.3 Phasor Relationships for R, L and C

Capacitor

P1.7, Suppose $C=20\mu\text{F}$, AC source $v=100\sin\omega t$, Find X_c and I for $f = 50\text{Hz}$ and 50kHz .

$$f = 50\text{Hz} \rightarrow X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = 159\Omega$$

$$I = \frac{V}{X_c} = \frac{V_m}{\sqrt{2}X_c} = 1.38\text{A}$$

$$f = 50\text{KHz} \rightarrow X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = 0.159(\Omega)$$


$$I = \frac{V}{X_c} = \frac{V_m}{\sqrt{2}X_c} = 1380(\text{A})$$

1.3 Phasor Relationships for R, L and C

Review (*v-i relationship*)


Time domain

Frequency domain

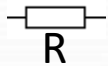

$$v = R \cdot i$$
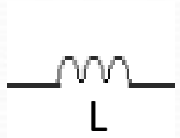
$$\dot{V} = R \cdot \dot{I}, v \text{ and } i \text{ are in phase.}$$



$$v_L = L \frac{di}{dt}$$

$$\dot{V} = j\omega L \cdot \dot{I}, X_L = \omega L, v \text{ leads } i \text{ by } 90^\circ.$$



$$v_C = C \frac{dv}{dt}$$

$$\dot{V} = \frac{1}{j\omega C} \cdot \dot{I}, X_C = \frac{1}{\omega C}, v \text{ lags } i \text{ by } 90^\circ.$$

1.3 Phasor Relationships for R, L and C

Summary

- R: $X_R = R$ $\Delta\varphi = 0$
- L: $X_L = \omega L = 2\pi f L \propto f$ $\Delta\varphi = \varphi_v - \varphi_i = \frac{\pi}{2}$
- C: $X_C = \frac{1}{\omega c} = \frac{1}{2\pi f c} \propto \frac{1}{f}$ $\Delta\varphi = \varphi_v - \varphi_i = -\frac{\pi}{2}$

- $V = IX$

- Frequency characteristics of an Ideal Inductor and Capacitor:
 A capacitor is an open circuit to DC currents;
 A Inductor is a short circuit to DC currents.