

1.4 Impedance

Key Words:

complex currents and voltages.

Impedance

Phasor Diagrams

1.4 Impedance

Complex voltage, Complex current, Complex Impedance

- AC steady-state analysis using phasors allows us to express the relationship between current and voltage using a formula that looks like Ohm's law:

$$\dot{V} = \dot{I}Z$$

Z is called impedance.
measured in ohms (Ω)

$$\dot{V} = V_m e^{j\varphi_v} = V_m \angle \varphi_v$$

$$\dot{I} = I_m e^{j\varphi_i} = I_m \angle \varphi_i$$

$$Z = \frac{\dot{V}}{\dot{I}} = \frac{V_m}{I_m} e^{j(\varphi_v - \varphi_i)} = |Z| e^{j\varphi} = |Z| \angle \varphi$$

1.4 Impedance

Complex Impedance

$$\mathbf{Z} = \frac{\dot{V}}{\dot{I}} = \frac{V_m}{I_m} e^{j(\varphi_v - \varphi_i)} = |\mathbf{Z}| e^{j\varphi} = |\mathbf{Z}| \angle \varphi$$

- Complex impedance describes the relationship between the voltage across an element (expressed as a phasor) and the current through the element (expressed as a phasor)
- Impedance is a complex number and is **not** a phasor (why?).
- Impedance depends on frequency

1.4 Impedance

Complex Impedance

Resistor——The impedance is R

$$Z_R = R \quad \Delta\varphi = 0; \text{ or } Z_R = R \angle 0$$

Capacitor——The impedance is $1/j\omega C$

$$Z_c = \frac{1}{\omega C} e^{-j\frac{\pi}{2}} = \frac{-j}{\omega C} = -jX_c \quad \text{or} \quad Z_c = \frac{1}{\omega C} \angle -90^\circ$$

$$(\Delta\varphi = \varphi_v - \varphi_i = -\frac{\pi}{2})$$

Inductor——The impedance is $j\omega L$

$$Z_L = \omega L e^{j\frac{\pi}{2}} = j\omega L = jX_L \quad \text{or} \quad Z_L = \omega L \angle 90^\circ$$


$$(\Delta\varphi = \varphi_v - \varphi_i = \frac{\pi}{2})$$

Sinusoidal Steady State Analysis

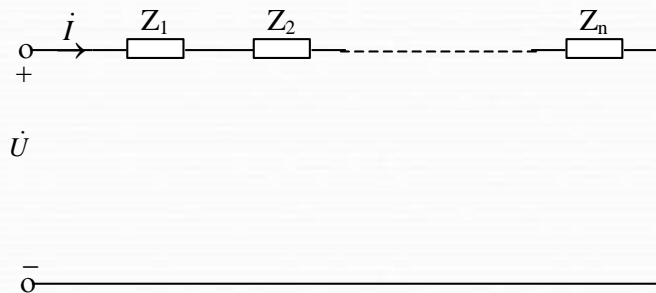
1.4 Impedance

Complex Impedance

Impedance in series/parallel can be combined as resistors.


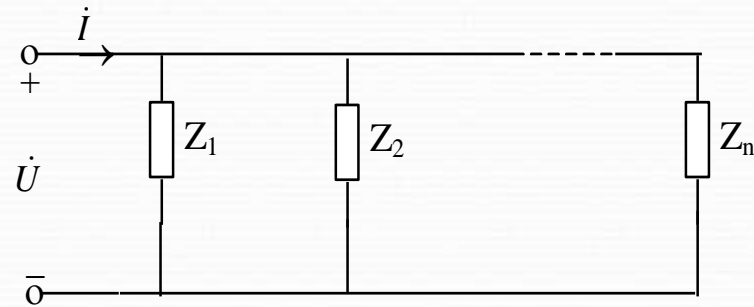
$$Z = Z_1 + Z_2 + \dots + Z_n = \sum_{k=1}^n Z_k$$



$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} = \sum_{k=1}^n \frac{1}{Z_k}$$

Voltage divider:

$$\dot{V}_i = \dot{V} \frac{Z_i}{\sum_{k=1}^n Z_k}$$


Current divider:

$$\dot{I}_1 = \dot{I} \frac{Z_2}{Z_1 + Z_2} \quad \dot{I}_2 = \dot{I} \frac{Z_1}{Z_1 + Z_2}$$

1.4 Impedance

Complex Impedance

P4.8,

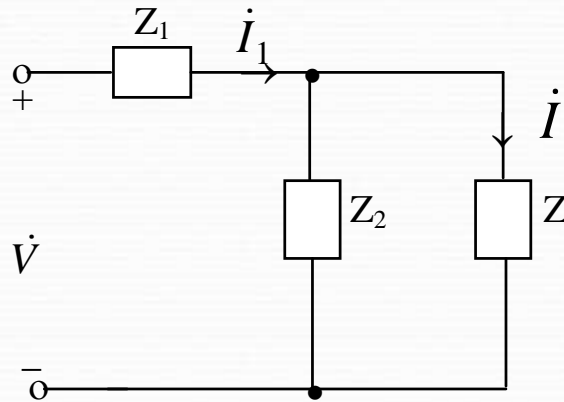

$$\dot{i} = \dot{i}_1 \frac{Z_2}{Z + Z_2}$$


$$\dot{i}_1 = \frac{\dot{V}}{Z_1 + \left(\frac{1}{Z_2} + \frac{1}{Z} \right)^{-1}} = \frac{\dot{V}(Z + Z_2)}{ZZ_1 + Z_2Z_1 + ZZ_2}$$

$$\dot{i} = \frac{\dot{V}Z_2}{ZZ_1 + Z_2Z_1 + ZZ_2}$$

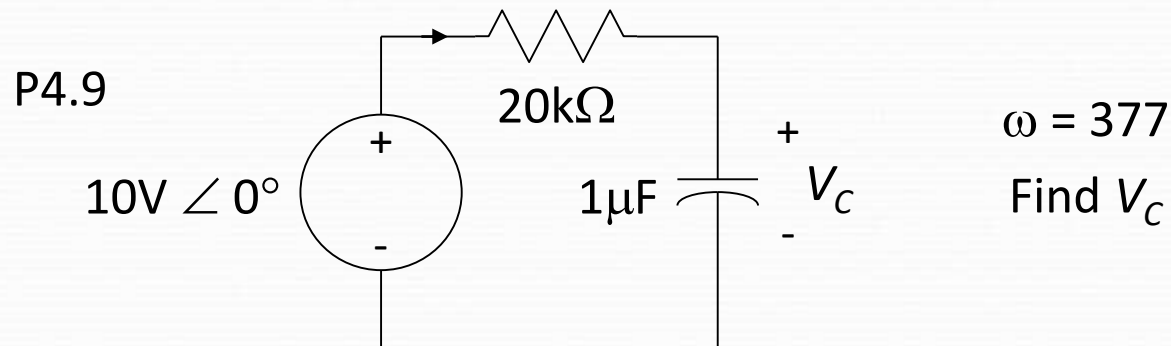1.4 Impedance

Complex Impedance

Phasors and complex impedance allow us to use Ohm's law with complex numbers to compute current from voltage and voltage from current



- How do we find V_C ?
- First compute impedances for resistor and capacitor:



$$Z_R = 20k\Omega = 20k\Omega \angle 0^\circ$$

$$Z_C = 1/j(377 * 1\mu F) = 2.65k\Omega \angle -90^\circ$$

Sinusoidal Steady State Analysis

1.4 Impedance

Complex Impedance

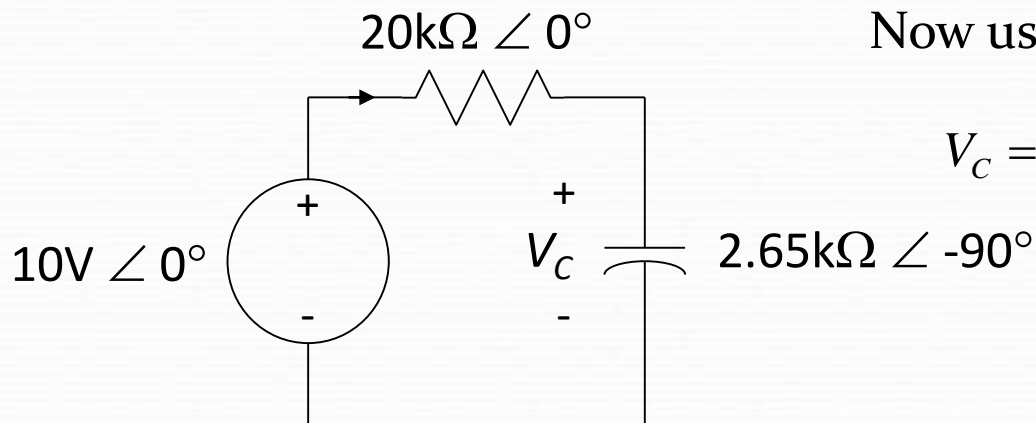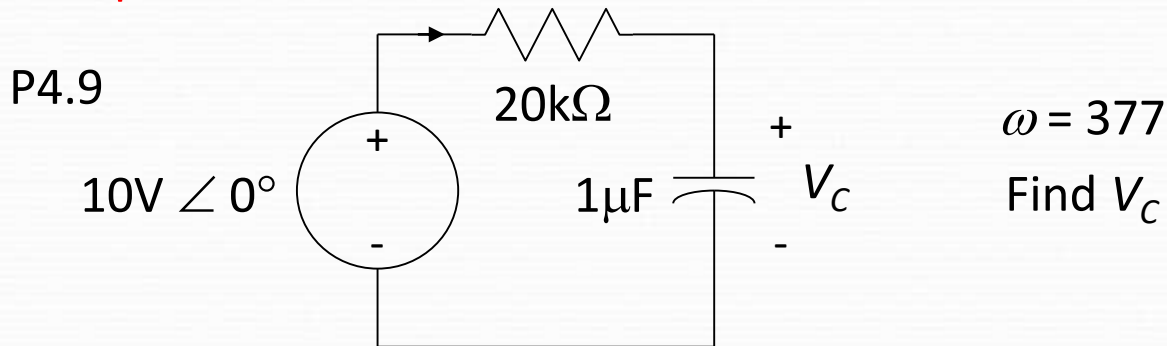

Now use the voltage divider to find V_C :

$$V_C = 10V \angle 0^\circ \left(\frac{2.65k\Omega \angle -90^\circ}{2.65k\Omega \angle -90^\circ + 20k\Omega \angle 0^\circ} \right)$$

$$\begin{aligned} V_C &= 10V \angle 0^\circ \frac{2.65 \angle -90^\circ}{20.17 \angle -7.54^\circ} \\ &= 1.31V \angle -82.46^\circ \end{aligned}$$

1.4 Impedance

Complex Impedance

Impedance allows us to use the same solution techniques for AC steady state as we use for DC steady state.

- All the analysis techniques we have learned for the linear circuits are applicable to compute phasors
 - KCL & KVL
 - node analysis / loop analysis
 - superposition
 - Thevenin equivalents / Norton equivalents
 - source exchange
- The only difference is that now complex numbers are used.

1.4 Impedance

Kirchhoff's Laws

KCL and KVL hold as well in phasor domain.

KCL:
$$\sum_{k=1}^n i_k = 0$$
 i_k^- Transient current of the # k branch

$$\sum_{k=1}^n \dot{I}_k = 0$$

KVL:
$$\sum_{k=1}^n v_k = 0$$
 v_k^- Transient voltage of the # k branch

$$\sum_{k=1}^n \dot{V}_k = 0$$

1.4 Impedance


Admittance

- $I = YV$, Y is called admittance, the reciprocal of impedance, measured in siemens (S)
- Resistor:
 - The admittance is $1/R$
- Inductor:
 - The admittance is $1/j\omega L$
- Capacitor:
 - The admittance is $j\omega C$

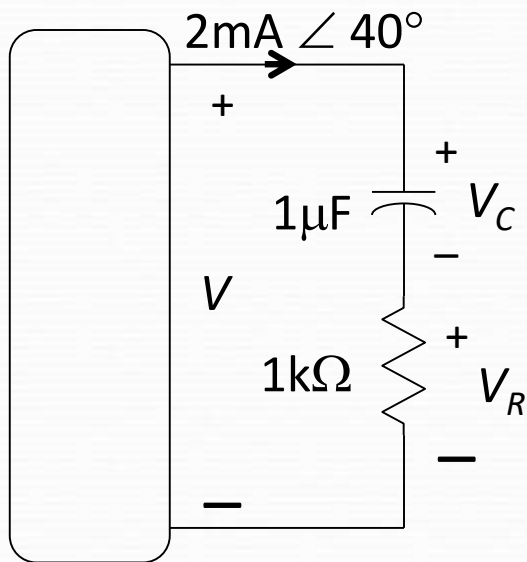1.4 Impedance

Phasor Diagrams

- A phasor diagram is just a graph of several phasors on the complex plane (using real and imaginary axes).
- A phasor diagram helps to visualize the relationships between currents and voltages.



$$I = 2\text{mA} \angle 40^\circ, \quad V_R = 2\text{V} \angle 40^\circ$$

$$V_C = 5.31\text{V} \angle -50^\circ, \quad V = 5.67\text{V} \angle -29.37^\circ$$

Imaginary Axis

