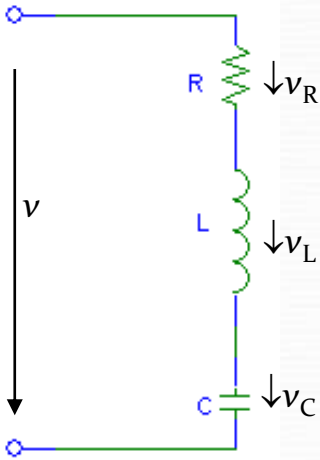


# Sinusoidal Steady State Analysis

## 1.5 Series and Parallel Resonance

### Series RLC Circuit (2nd Order RLC Circuit)



$$v = v_R + v_L + v_C$$

Phasor  $\dot{V} = \dot{V}_R + \dot{V}_L + \dot{V}_C$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$


$\Rightarrow$   $= \sqrt{(IR)^2 + (IX_L - IX_C)^2}$

$$= I\sqrt{R^2 + (X_L - X_C)^2}$$

$$= I\sqrt{R^2 + X^2} \quad (X = X_L - X_C)$$

$$= IZ$$
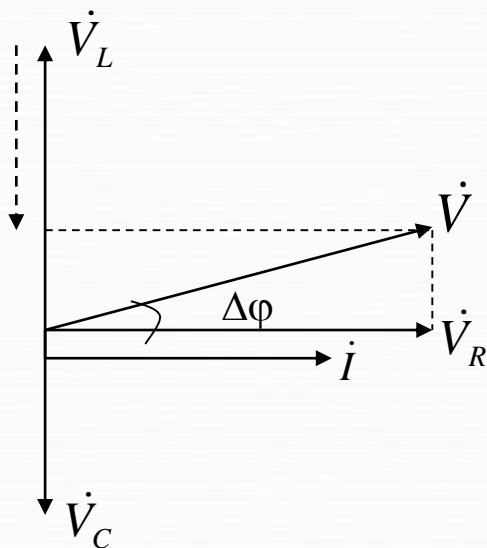
$$Z = \sqrt{R^2 + X^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$




# Sinusoidal Steady State Analysis

## 1.5 Series and Parallel Resonance
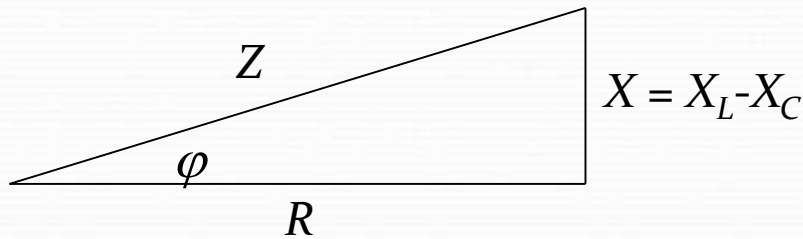
### Series RLC Circuit (2nd Order RLC Circuit)


$$V = \sqrt{V_R^2 + (V_L - V_C)^2} = IZ \quad Z = \sqrt{R^2 + X^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$



Phase difference:

$$= \arctg \frac{V_L - V_C}{V_R}$$

$$= \arctg \frac{X_L - X_C}{R}$$

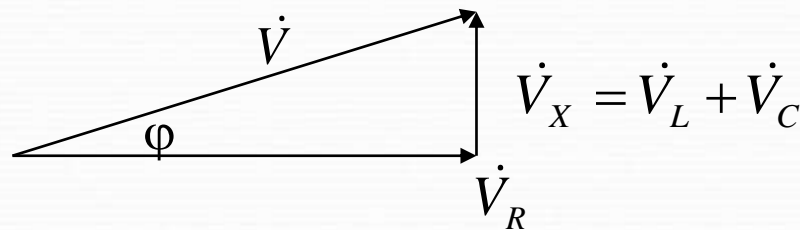

$X_L > X_C \rightarrow \varphi > 0$ ,  $v$  leads  $i$  by  $\varphi$  — Inductance Circuit


$X_L < X_C \rightarrow \varphi < 0$ ,  $v$  lags  $i$  by  $\varphi$  — Capacitance Circuit

$X_L = X_C \rightarrow \varphi = 0$ ,  $v$  and  $i$  in phase — Resistors Circuit

# Sinusoidal Steady State Analysis

## 1.5 Series and Parallel Resonance
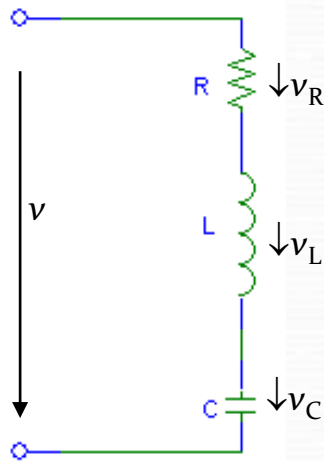
### Series RLC Circuit (2nd Order RLC Circuit)



$$\begin{aligned}\dot{V} &= \dot{V}_R + \dot{V}_L + \dot{V}_C = \dot{I}R + j\dot{I}X_L - j\dot{I}X_C \\ &= \dot{I}(R + j(X_L - X_C)) = \dot{I}(R + jX) = \dot{I}Z\end{aligned}$$

$$\longrightarrow Z = \frac{\dot{V}}{\dot{I}} = R + j(X_L - X_C)$$

$$Z = R + jX = |Z| \angle \varphi \begin{cases} |Z| = \sqrt{R^2 + (X_L - X_C)^2} \\ \varphi = \arctg \frac{X_L - X_C}{R} \end{cases}$$


$$\varphi = \varphi_v - \varphi_i$$

# Sinusoidal Steady State Analysis

## 1.5 Series and Parallel Resonance
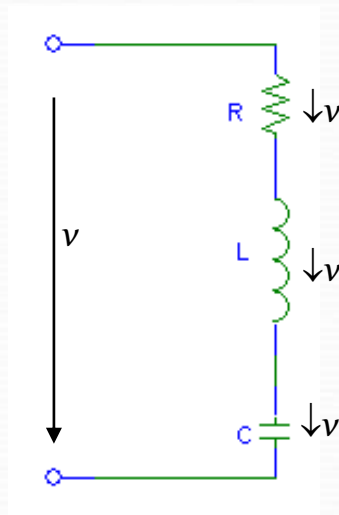
### Series RLC Circuit (2nd Order RLC Circuit)

P4.9, R. L. C Series Circuit,  $R = 30\Omega$ ,  $L = 127\text{mH}$ ,  $C = 40\mu\text{F}$ , Source  $v = 220\sqrt{2} \sin(314t + 20^\circ)$ . Find 1)  $X_L$ ,  $X_C$ ,  $Z$ ; 2)  $\dot{I}$  and  $i$ ; 3)  $\dot{V}_R$  and  $v_R$ ;  $\dot{V}_L$  and  $v_L$ ;  $\dot{V}_C$  and  $v_C$ ; 4) Phasor diagrams;



P4.10, Computing  $\dot{I}$  by (complex numbers) Phasors

# Sinusoidal Steady State Analysis

## 1.5 Series and Parallel Resonance



### Series Resonance (2nd Order RLC Circuit)

$$\dot{V} = \dot{V}_R + \dot{V}_L + \dot{V}_C = iR + jIX_L - jIX_C \quad \varphi = \arctg \frac{V_L - V_C}{V_R} = \arctg \frac{X_L - X_C}{R}$$

When  $X_L = X_C$ ,  $\frac{1}{\omega C} = \omega L \rightarrow V_L = V_C \longrightarrow \omega_0 = \frac{1}{\sqrt{LC}}$  or  $f_0 = \frac{1}{2\pi\sqrt{LC}}$

Resonance condition Resonance frequency

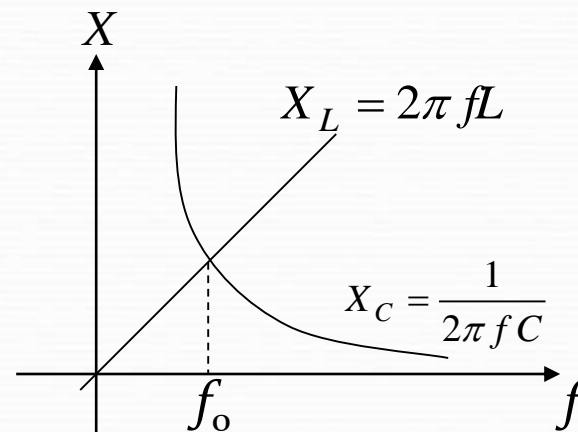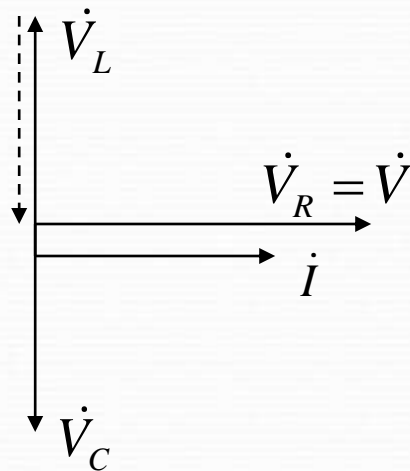$\longrightarrow V_R = V$  and  $\varphi = 0$  — **Series Resonance**



# Sinusoidal Steady State Analysis

## 1.5 Parallel and Series Resonance

### Series Resonance (2nd Order RLC Circuit)

Resonance condition:  $X_L = X_C \quad \left(\frac{1}{\omega C} = \omega L\right) \quad \rightarrow V_L = V_C$

- $Z_0 = \sqrt{R^2 + (X_L - X_C)^2} = R \rightarrow I_0 = \frac{V}{Z_0} = \frac{V}{R}$

$Z_{min}$ ; when  $V = \text{constant}$ ,  $I = I_{max} = I_0$ .

- When  $X_L = X_C \gg R \rightarrow I_0 X_L = I_0 X_C \gg I_0 R \rightarrow V_L = V_C \gg V$


- Quality factor  $Q$ ,

$$Q = \frac{V_L}{V} = \frac{V_C}{V} = \frac{X_L}{R} = \frac{X_C}{R}$$

# Sinusoidal Steady State Analysis

## 1.5 Series and Parallel Resonance

### Parallel RLC Circuit

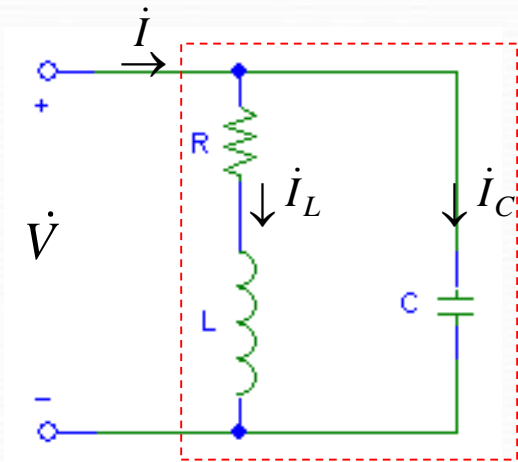

$$\begin{aligned}
 Y &= \frac{1}{R + j\omega L} + \frac{1}{-j/\omega C} = \frac{1}{R + j\omega L} + j\omega C \\
 &= \frac{R - j\omega L}{(R + j\omega L)(R - j\omega L)} + j\omega C \\
 &= \frac{R}{R^2 + \omega^2 L^2} + j\left(\omega C - \frac{\omega L}{R^2 + \omega^2 L^2}\right)
 \end{aligned}$$

When  $\left(\omega C - \frac{\omega L}{R^2 + \omega^2 L^2}\right) = 0$ ,  $Y_0 = \frac{R}{R^2 + \omega^2 L^2}$

$\dot{V}$  In phase with  $\dot{i}$

→ **Parallel Resonance**

Parallel Resonance  
frequency

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{CR^2}{L}}$$

In generally  $R \ll X_L$  →


$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \left(f_0 = \frac{1}{2\pi\sqrt{LC}}\right)$$

→  $Z_{max} \quad I_{min}: \quad I = I_0 = VY_0 = V \frac{R}{R^2 + \omega_0^2 L^2} = V \frac{R}{R^2 + \frac{1}{LC} L^2} = V \frac{R}{R^2 + \frac{L}{C}} \approx \frac{RC}{L} V$

# Sinusoidal Steady State Analysis

## 1.5 Series and Parallel Resonance

### Parallel RLC Circuit

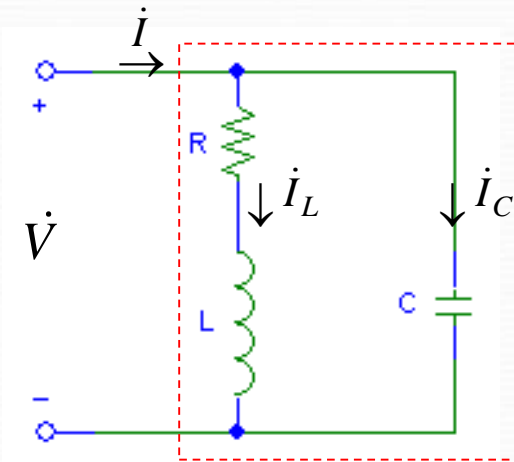

$$\dot{I}_L = \dot{V} \frac{1}{R + j\omega_0 L} \approx -j \frac{\dot{V}}{\omega_0 L} = -j \sqrt{\frac{C}{L}} \dot{V}$$

$$\dot{I}_C = j\omega_0 C \dot{V} = j \sqrt{\frac{C}{L}} \dot{V}$$

$$|\dot{I}_L| = |\dot{I}_C| \gg |\dot{I}_0| \approx 0 \longrightarrow Z \rightarrow \infty.$$

• Quality factor Q,

$$Q = \frac{I_C}{I_0} = \frac{I_L}{I_0} = \frac{Y_L}{Y_0} = \frac{Y_C}{Y_0}$$

$$\dot{I}_L = -jQ\dot{I}_0$$

$$\dot{I}_C = jQ\dot{I}_0$$

$$Q \approx \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$




# Sinusoidal Steady State Analysis

## 1.5 Series and Parallel Resonance

### Parallel RLC Circuit

P4.10,  $R_1 = 3\Omega$ ,  $X_L = 4\Omega$ ,  $R_2 = 8\Omega$ ,  $X_C = 6\Omega$   $v = 220\sqrt{2} \sin 314t$

Find  $i_1$ ,  $i_2$ ,  $i$

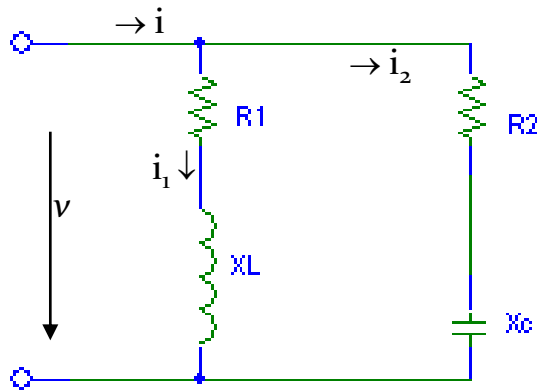

# Sinusoidal Steady State Analysis

## 1.5 Series and Parallel Resonance

### Parallel RLC Circuit

#### Review

For sinusoidal circuit, Series :  $v = v_1 + v_2$        $V \neq V_1 + V_2$       ?

Parallel :  $i = i_1 + i_2$        $I \neq I_1 + I_2$

Two Simple Methods:

Phasor Diagrams and Complex Numbers