

Sinusoidal Steady State Analysis

1.6 Examples for Sinusoidal Circuits Analysis

Key Words:

Bypass Capacitor

RC Phase Difference


Low-Pass and High-Pass Filter

Sinusoidal Steady State Analysis

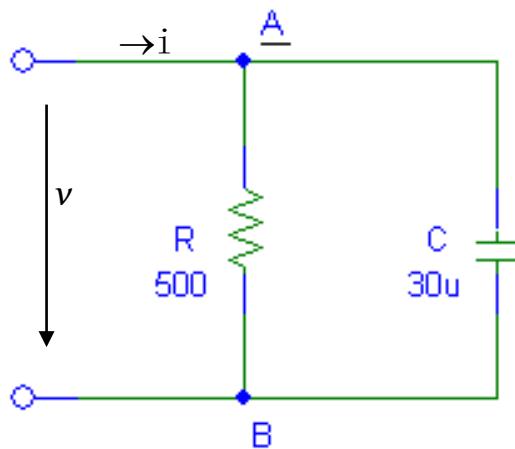1.6 Examples for Sinusoidal Circuits Analysis

Bypass Capacitor

P4.11, Let $i = 3 \times 10^{-3} \sqrt{2} \sin \omega t = 3 \times 10^{-3} \sqrt{2} \sin 2\pi f t = 3 \times 10^{-3} \sqrt{2} \sin 1000\pi t$
 $f = 500\text{Hz}$, Determine V_{AB} before the C is connected . And V_{AB} after parallel $C = 30\mu\text{F}$



Before C is connected

$$V_{AB} = IR = 3 \times 10^{-3} \times 500 = 1.5(V)$$

After C is connected

$$X_C = \frac{1}{2\pi f C} = \frac{1}{1000 \times 30 \times 10^{-6}} = 10(\Omega)$$

$$Z = \left(\frac{1}{R} + \frac{1}{-jX_C} \right)^{-1} = 0.2 - 10j = 10 \angle -88.85^\circ$$


$$\rightarrow V_{AB} = I|Z| = 3 \times 10^{-3} \times 10 = 30(mV)$$

Sinusoidal Steady State Analysis

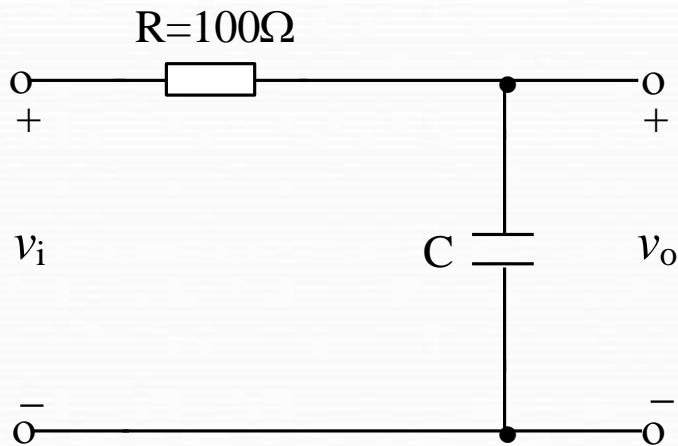1.6 Examples for Sinusoidal Circuits Analysis

RC Phase Difference

P4.12, $f = 300\text{Hz}$, $R = 100\Omega$. If $\varphi_{v_o} - \varphi_{v_i} = \pi/4$, $C = ?$



$$\dot{V}_i = I(R - jX_C) = |V_i| \angle \varphi_{v_i}$$

$$\dot{V}_o = I(-jX_C) = |V_o| \angle \varphi_{v_o} = |V_o| \angle -90^\circ$$

$$X_C = \frac{1}{\omega C} = \frac{5.31 \times 10^{-4}}{C} \Omega$$

$$\frac{\dot{V}_o}{\dot{V}_i} = \frac{-jX_C}{R - jX_C} = \frac{|V_o| \angle -90^\circ}{|V_i| \angle \arctg \frac{-5.31 \times 10^{-6}}{C}}$$

$$\varphi_{v_o} - \varphi_{v_i} = -\frac{\pi}{2} - \arctg \frac{-5.31 \times 10^{-6}}{C} = \frac{\pi}{4}$$

$$\arctg \frac{-5.31 \times 10^{-6}}{C} = -\frac{\pi}{4}$$

$$\frac{-5.31 \times 10^{-6}}{C} = -0.0411$$


$$C = 1.29 \times 10^{-4} \text{ F}$$



Ch4 Sinusoidal Steady State Analysis

4.6 Examples for Sinusoidal Circuits Analysis

Low-Pass and High-Pass Filter

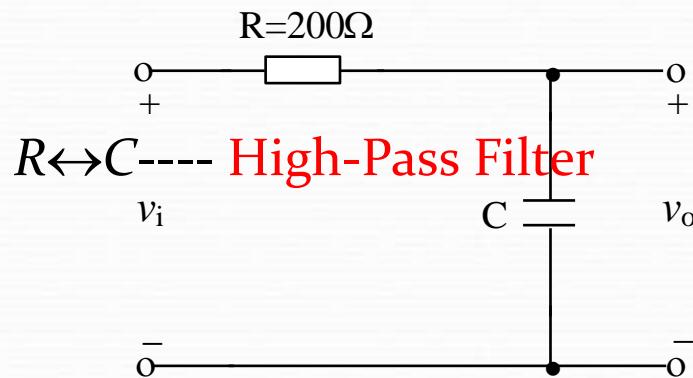

$$X_C \propto \frac{1}{f}$$

$$\frac{V_R}{V_C} = \frac{R}{\frac{1}{\omega C}} \longrightarrow V_R X_C = RV_C$$

P4.13, The voltage sources are $v_i = 240 + 100 \sin 2\pi 100t$ (V), $R = 200\Omega$, $C = 50\mu F$, Determine V_{AC} and V_{DC} in output voltage v_o .

$$V_{DC} = 240V$$

$$V_{AC} = X_C \cdot \frac{V}{Z} = \frac{32}{200} \times 100 = 16(V)$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 100 \times 50 \times 10^{-6}} = 32\Omega$$


$$Z = \sqrt{R^2 + X_C^2} = \sqrt{200^2 + 32^2} \approx 200\Omega$$

Sinusoidal Steady State Analysis

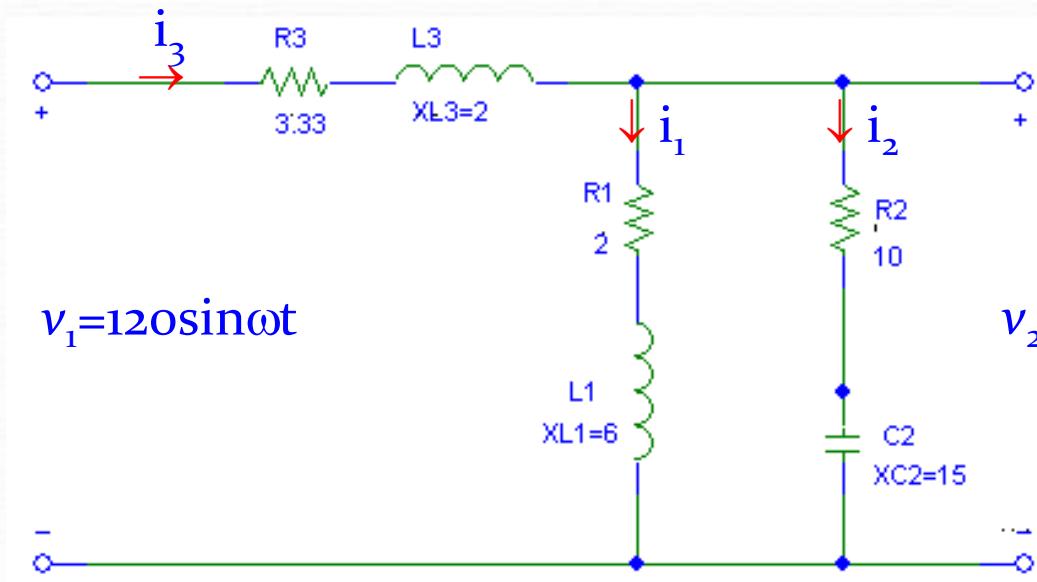1.6 Examples for Sinusoidal Circuits Analysis

Complex Numbers Analysis

P4.14, Find i_1 i_2 i_3 \dot{V}_2 in the circuit of the following fig.



Sinusoidal Steady State Analysis

1.6 Examples for Sinusoidal Circuits Analysis

Complex Numbers Analysis

P4.15, Let $V_m = 100V$. Use Thevenin's theorem to find \dot{I}_{CD}

