

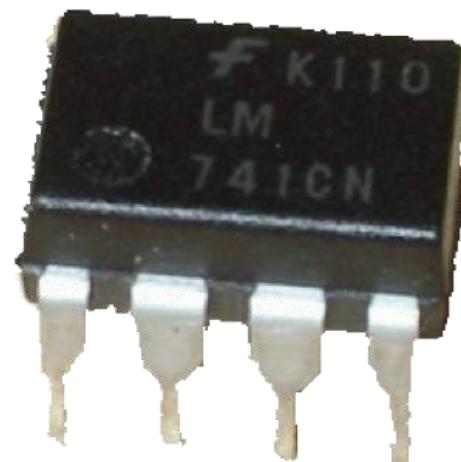

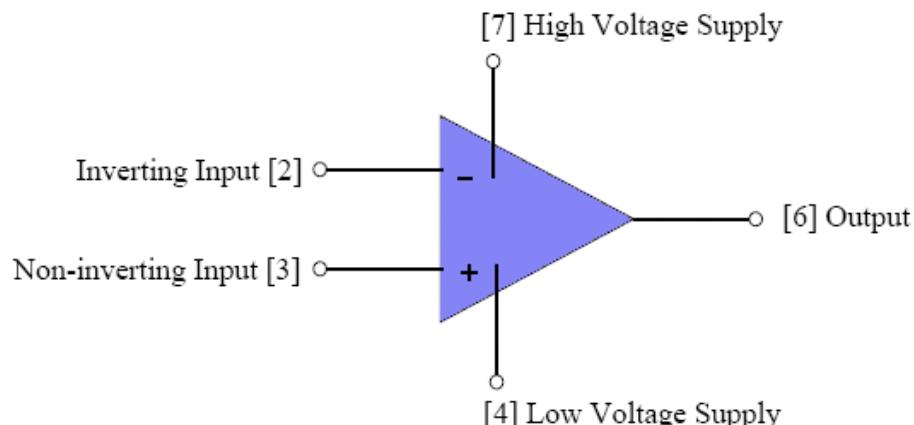
# Introduction

- Operational Amplifiers are represented both schematically and realistically below:
  - Active component!



# Operational Amplifier

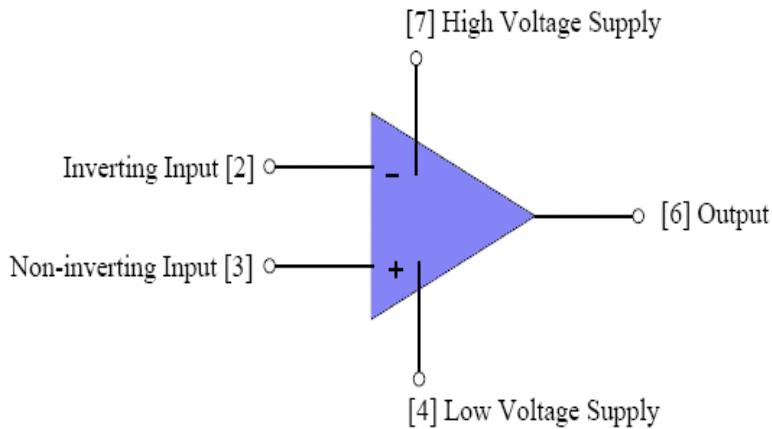


- Output gain high
  - $A \sim= 10^6$
- Tiny difference in the input voltages result in a very large output voltage
  - Output limited by supply voltages
- Comparator
  - If  $V_+ > V_-$ ,  $V_{out} = HVS$
  - If  $V_+ < V_-$ ,  $V_{out} = LVS$
  - If  $V_+ = V_-$ ,  $V_{out} = 0V$

# Ideal Op Amp

- $Z_{in}$  is infinite
- $Z_{out}$  is zero
- Amplification (Gain)  $V_{out} / V_{in} = \infty$
- Unlimited bandwidth
- $V_{out} = 0$  when Voltage inputs = 0


# Non-inverting Op-Amp

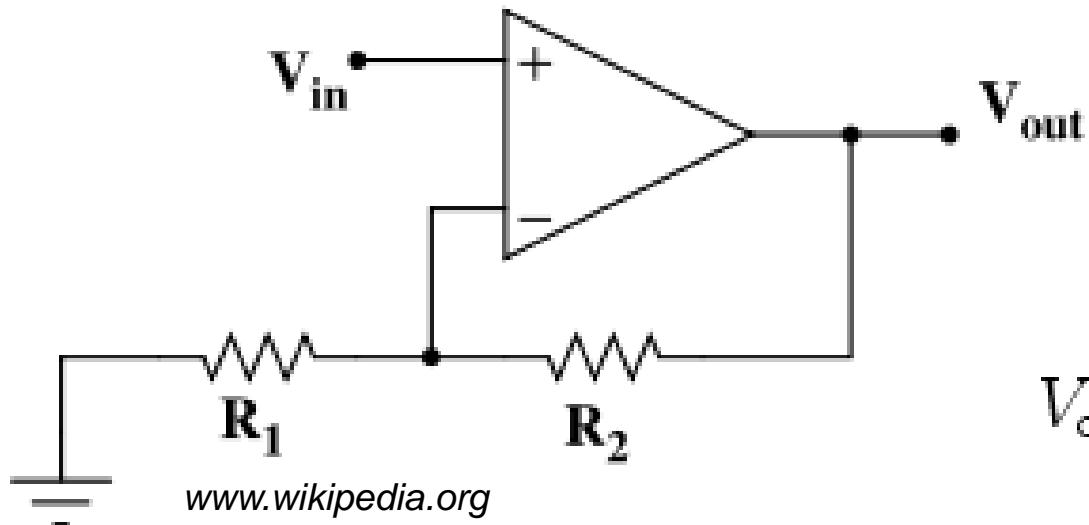

$$V_{out} = V_{in} \left( 1 + \frac{R_2}{R_1} \right)$$

**Uses: Amplify...straight up**

# Inverting Op-Amp

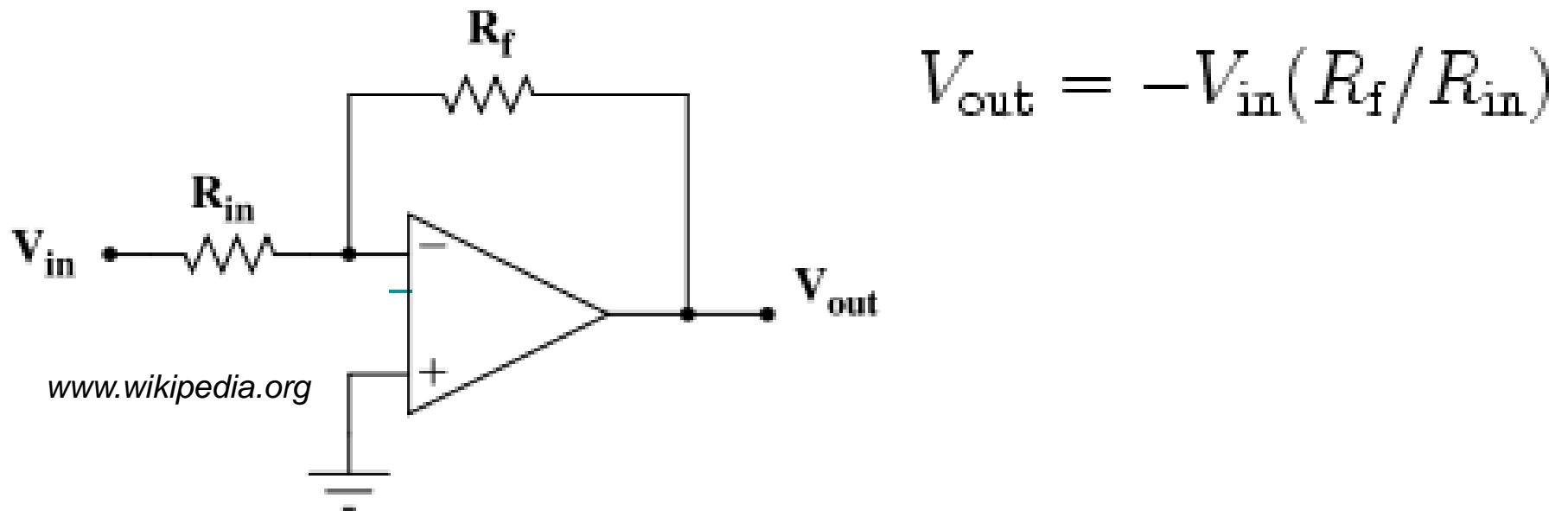

Uses: Analog inverter