

Lecture Outline:

Introduction.

Fixed V_i , Fixed R_L .

Fixed V_i , Variable R_L .

Zener effect

The **Zener effect** is the breakdown mechanism if the reverse bias required to force **breakdown occurs at low voltages**.

Consider the heavily doped p-n junction shown to the left and then apply a reverse bias to the junction.

Reverse bias brings the conduction band very close to the valence band. This brings many occupied states on the p-side into energetic alignment with vacant states on the n-side. Electrons **tunnel from the valence** band to the conduction band giving rise to a reverse current.

This is the **Zener effect**.


So what do we need to cause **Zener breakdown**?

The basic requirements to drive a tunneling current are:


- A large number of electrons
- A large number of holes
- Separated by a narrow barrier of finite height.
- Tunneling depends heavily on the barrier width so we want to keep the junction sharp and doping high.
- This will ensure that the transition region W extends only a very short distance from each side of the junction.
- Failure to attain high doping or sharp junctions will result in no tunneling current.

Zener Breakdown

- Zener breakdown occurs when a sufficiently large reverse-bias is applied across a *p–n junction diode*. *The resulting* electric field at the junction imparts a very large force on a bound electron, enough to dislodge it from its covalent bond.
- The breaking of the covalent bonds produces a large number of EHP (electron–hole pairs). Consequently the reverse current becomes very large. This type of breakdown phenomena is known as **Zener breakdown**.

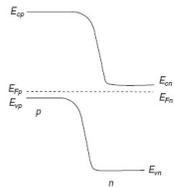

Energy band diagram of a Zener diode

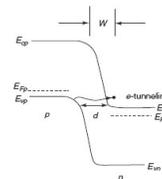


Reverse bias with electron tunnelling from p to n leads to Zener breakdown

When does it happen...


- Occurs in Si for fields $\sim 10^6$ V/cm
- Must have high impurity concentrations
- Occurs in general for reverse biases of less than $4E_g/q$.

❖ Comparison between Zener and avalanche breakdown

<i>Zener Breakdown</i>	<i>Avalanche Breakdown</i>
1. Narrow depletion region and quantum mechanical tunneling takes place.	1. Higher Depletion region width and electron tunneling is negligible.
2. Highly doped diode with reverse-bias is required.	2. Low doped diode with reverse-bias is sufficient.
3. Operates at low voltage up to few volts reverse-bias.	3. Breakdown occurs at high reverse-bias from a few volts to thousands of volts.
4. Impact ionization does not occur in this case.	4. This breakdown mechanism involves the impact ionization of host atoms by energetic carriers.

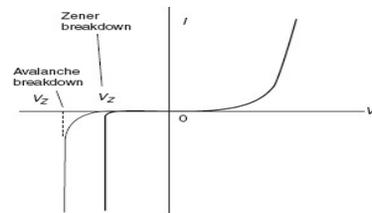

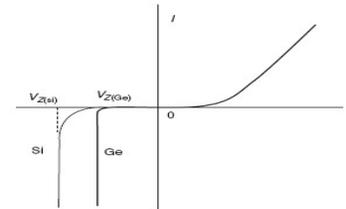The I-V characteristics comparison between Zener and avalanche breakdown




Comparison of Zener breakdown of Ge and Si semiconductor diodes with respect to I-V curve

Introduction

The basic function of **Zener diode** is to maintain a specific voltage across its terminals within given limits of line or load change.

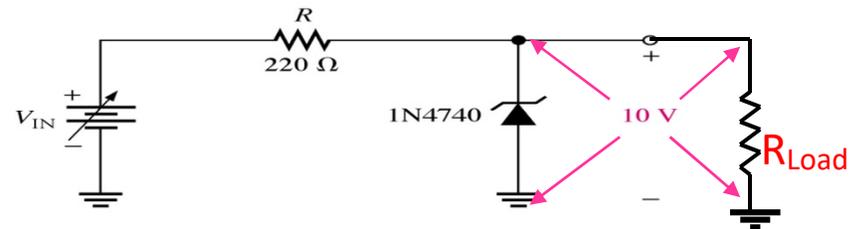Typically it is used for providing a stable reference voltage for use in power supplies and other equipments.




This particular Zener circuit will work to maintain 10volts across the load.

Zener Diode – Operating Range

A **Zener diode** is much like a normal diode (rectifier diode) when connected in forward bias, the exception being is that; it is placed in the circuit in **reverse bias** and **operates in reverse break-down region**.

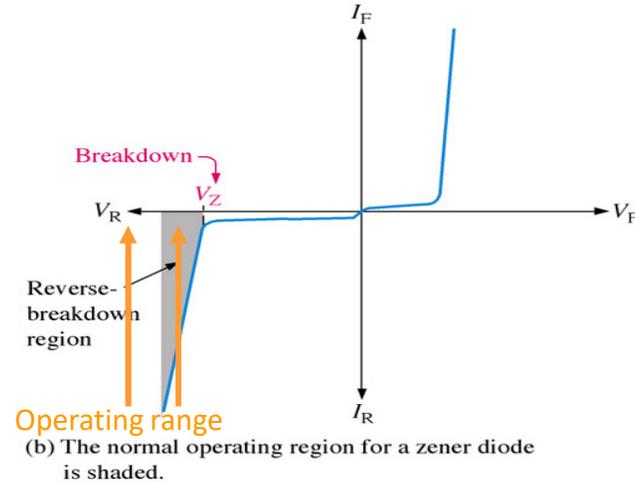This typical characteristic curve illustrates the operating range for a Zener diode. Note that its forward characteristics are same like a normal diode.




Zener Diodes – Regulation Ranges

The Zener diode's breakdown characteristics are determined by the doping process.

Low voltage Zeners ($< 5V$), operate in the Zener breakdown range.

Those diodes which are designed to operate ($> 5V$) operate mostly in avalanche breakdown range.

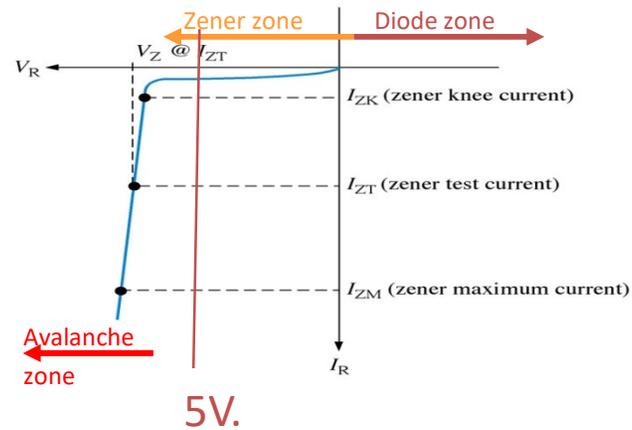Zeners are available with voltage breakdowns of **1.8V to 200V**.



This curve illustrates the minimum and maximum ranges of current operation that the Zener can effectively maintain its voltage.

Zener Diode – Breakdown Characteristics

Note very small reverse current (before “knee”).

Breakdown occurs @ knee.

Breakdown Characteristics:

V_Z remains near constant


V_Z provides:

- Reference Voltage
- Voltage Regulation

I_Z increases rapidly

I_{ZMAX} is achieved quickly


Exceeding I_{ZMAX} is fatal

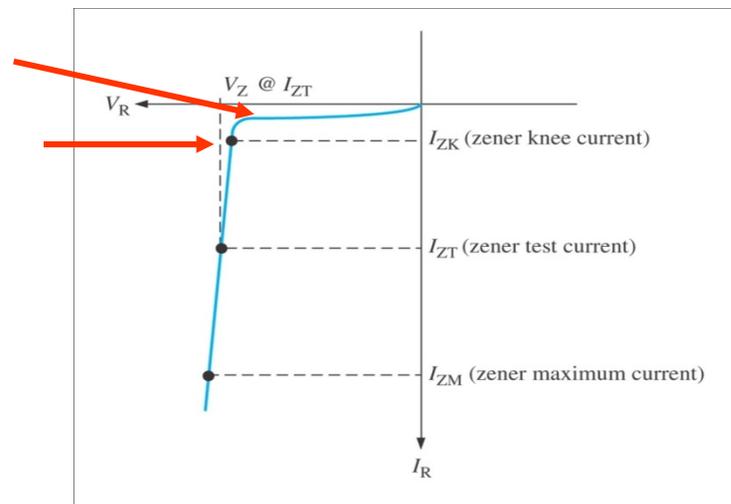

Zener Diode – Equivalent Circuit


Ideal Zener exhibits a **constant voltage**, regardless of current draw.

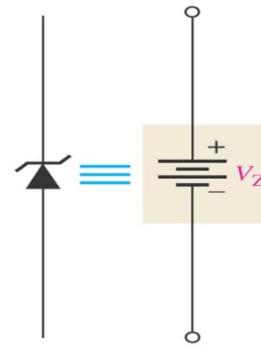Ideal Zener exhibits **No Resistance** characteristics.



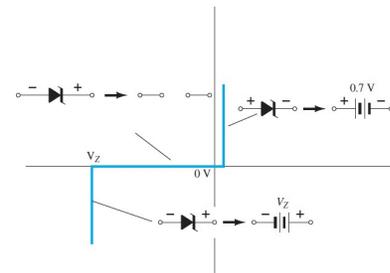(a) Ideal

- The Zener diode has three regions of operations. Each region has its own approximation model.
- It can be used as a part of protection circuit or as a voltage regulator.
- The use of the Zener diode as a regulator is so common that three conditions surrounding the analysis of the basic Zener regulator are considered:
 - 1 Fixed load and fixed supply voltage.
 - 2 Fixed supply voltage and variable load.
 - 3 Variable supply voltage and fixed load.
- The first case is already studied in the previous semester and will be briefly reviewed.



Zener diode characteristics


Fixed V_i , Fixed R_L :

Example

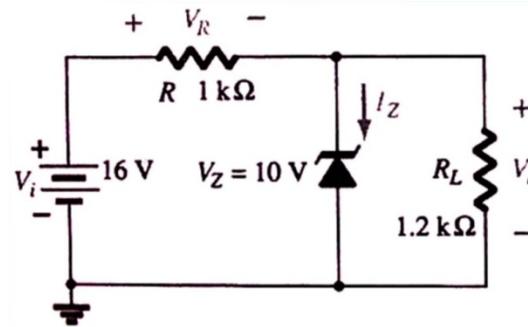Example

For the Zener diode regulator,

- 1 Determine V_L , V_R , I_Z and P_Z .
- 2 If the load is changed to $R_L = 3 \text{ k}\Omega$, repeat the above problem.



Example

Fixed V_i , Fixed R_L :

Solution:

- Determine the voltage across the Zener diode to determine its state:

$$V_{zener} = V_L = \frac{V_i R_L}{R_L + R} = 16 \frac{1.2}{1 + 1.2} = 8.73 \text{ V}$$


Since the voltage across the Zener is smaller than V_Z and the diode is reverse, then the Zener is OFF.

$$V_L = V_{zener} = 8.73 \text{ V}$$

$$V_R = V_i - V_L = 16 - 8.73 = 7.27 \text{ V}$$

$$I_Z = 0$$

$$P_Z = 0 \text{ Watts}$$

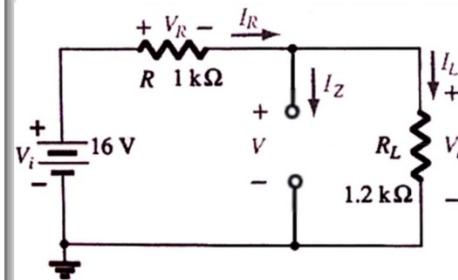

Example

Fixed V_i , Fixed R_L :

Solution:

2 If $R_L = 3 \text{ k}\Omega$:


$$V_{zener} = V_i \frac{R_L}{R + R_L} = \frac{16 \times 3}{1 + 3} = 12 \text{ V}$$

Since the voltage across the zener is greater than V_Z then the zener is operating in the zener region and can be approximated as battery with V_Z :

$$V_L = V_Z = 10 \text{ V}$$

$$V_R = V_i - V_L = 16 - 10 = 6 \text{ V}$$
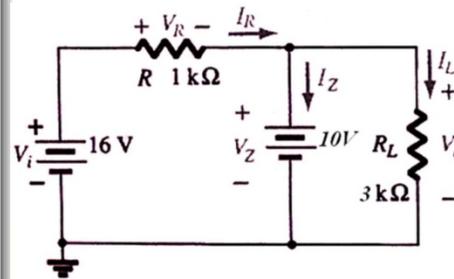
$$I_R = \frac{V_R}{R} = \frac{6 \text{ V}}{1 \text{ k}\Omega} = 6 \text{ mA}$$



Example

Fixed V_i , Fixed R_L :


Solution:

$$I_L = \frac{V_L}{R_L} = \frac{10V}{3k\Omega} = 3.33 \text{ mA}$$

$$I_Z = I_R - I_L = 6 - 3.33 = 2.67 \text{ mA}$$

The power dissipated by the Zener diode is:

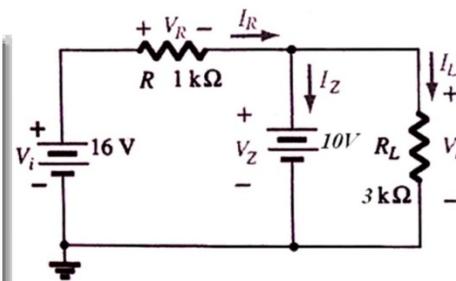
$$P_Z = I_Z \times V_Z = 26.7 \text{ mW}$$



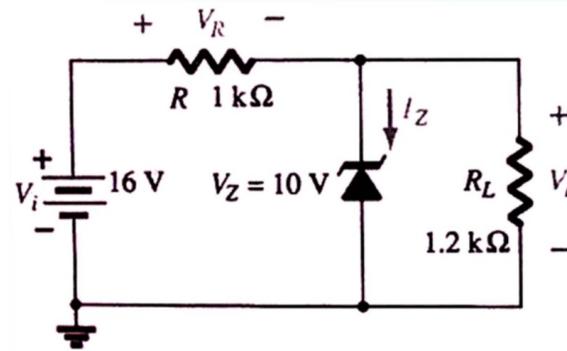Example

Fixed V_i , Variable R_L :

- The load resistance R_L determines the state of the Zener (on or off).
- Too small a R_L will result in a voltage V_L across the load resistor less than V_Z , and the Zener device will be in the "off" state.
- We need to find the range of load resistance that ensure the on state for the zener diode



$$V_L = V \frac{R_L}{R + R_L}$$

Fixed V_i , Variable R_L :

To determine the minimum load resistance, R_{Lmin} :


It is the resistance that will result in a load voltage $V_L = V_Z$:

$$V_L = V_Z = V \frac{R_L}{R + R_L}$$

$$R_{Lmin} = \frac{R V_Z}{V_i - V_Z}$$

So, if a load resistance is greater than R_{Lmin} then the Zener will be on and:
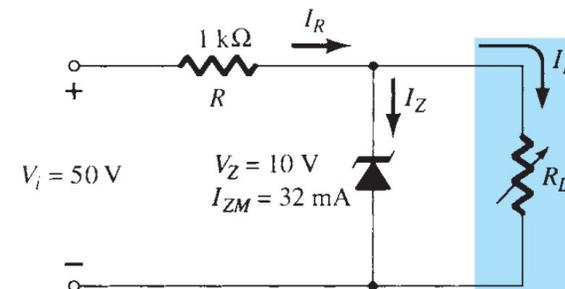
$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}}$$



Fixed V_i , Variable R_L :

To determine the maximum load resistance, R_{Lmax} :

Once the diode is ON, the voltage across R is fixed at:

$$V_R = V_i - V_Z$$

and,

$$I_R = \frac{V_R}{R}$$


The Zener current is:

$$I_Z = I_R - I_L$$

I_Z is limited to the maximum zener current I_{ZM} from the data sheet.

$$I_{Lmin} = I_R - I_{ZM}$$


$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

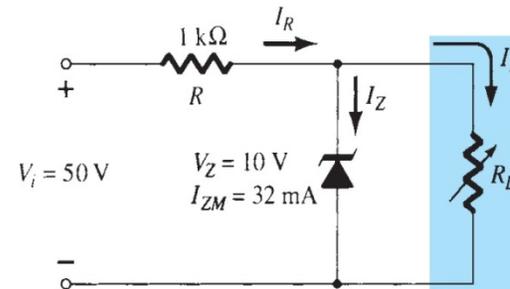

Fixed V_i , Variable R_L :

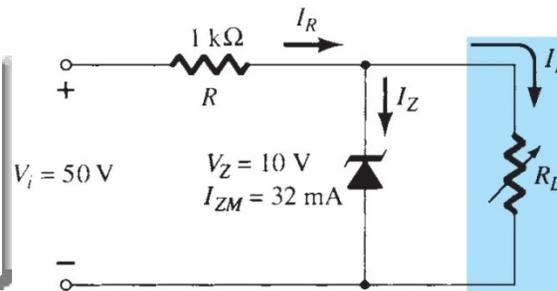Example:

- 1 For the shown network, determine the range of R_L and I_L that will result in V_L being maintained at 10 V.
- 2 Determine the maximum wattage rating of the diode.




Fixed V_i , Variable R_L :

Solution:

$$R_{Lmin} = \frac{R V_Z}{V_i - V_Z} = \frac{1 \text{ k}\Omega \cdot 10\text{V}}{50\text{V} - 10\text{V}}$$

$$R_{Lmin} = 250 \Omega$$
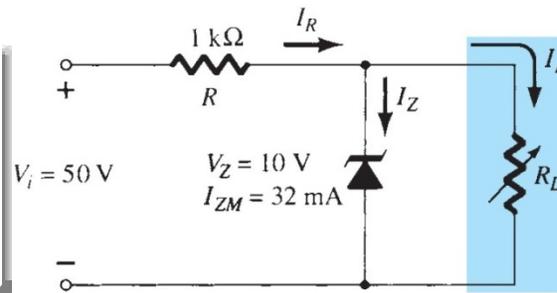
$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}} = \frac{10}{250} = 40\text{mA}$$



Fixed V_i , Variable R_L :


Solution:




$$V_R = V_i - V_Z = 50 - 10 = 40 \text{ V}$$

$$I_R = \frac{V_R}{R} = \frac{40 \text{ V}}{1 \text{ k}\Omega} = 40 \text{ mA}$$

$$I_{Lmin} = I_R - I_{ZM} = 40 - 32 = 8 \text{ mA}$$
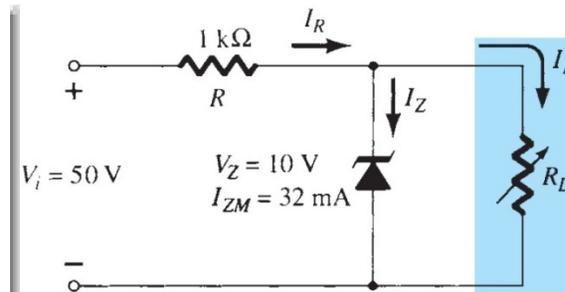
$$R_{Lmax} = \frac{V_Z}{I_{Lmin}} = \frac{10 \text{ V}}{8 \text{ mA}}$$



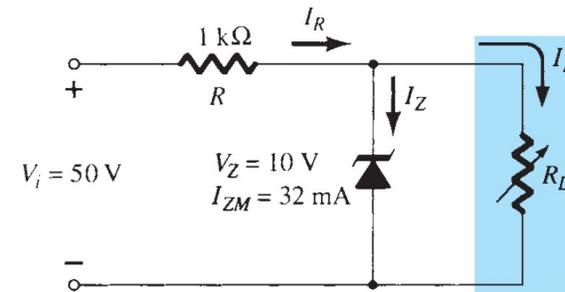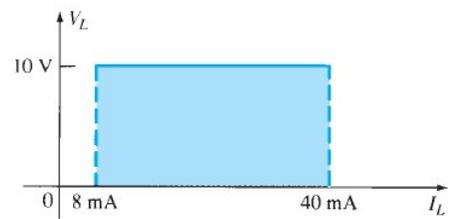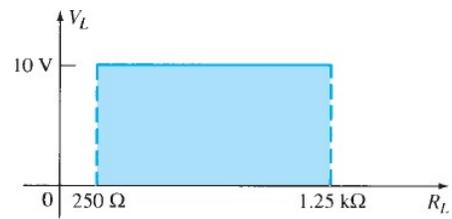Fixed V_i , Variable R_L :

Fixed V_i , Variable R_L :

Solution:

$$P_{Zmax} = V_Z I_{ZM} = (10 \text{ V})(32 \text{ mA}) = 320 \text{ mW}$$

