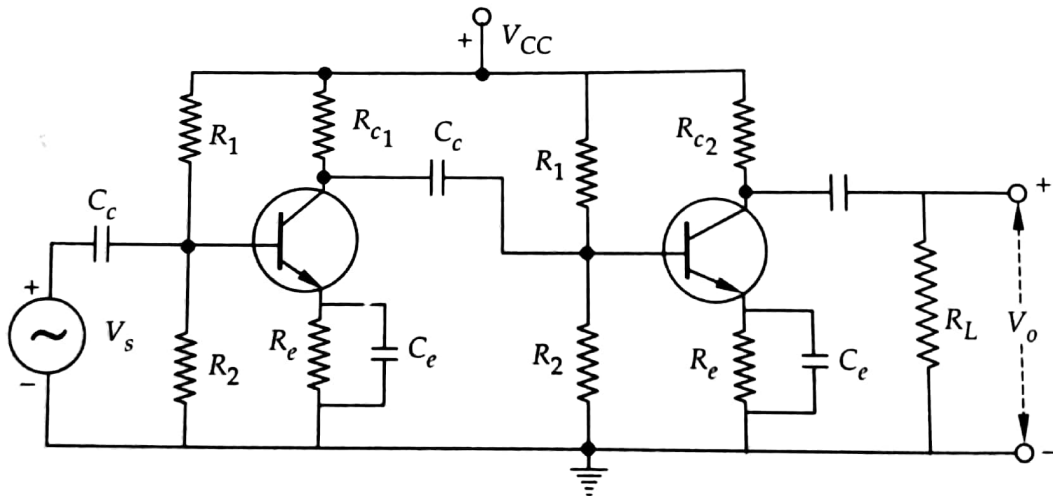


### SOLVED EXAMPLES


**Example 1.** Draw a circuit diagram of two stage R-C coupled amplifier. Draw its a.c. equivalent circuit at mid-frequency range. Give expressions for (1) Input impedance, (2) Output impedance and (3) Voltage gain.

The circuit diagram of two stage R-C coupled amplifier is shown in fig. (11·48).



**Fig. 11-48** Two stage R-C coupled amplifier

Its a.c. equivalent circuit at mid-frequency range is shown in fig. (11·49).

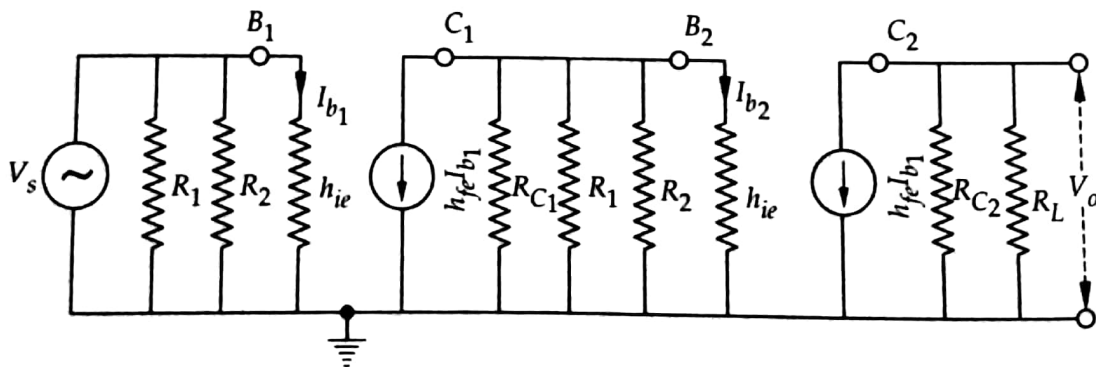

**Fig. 11-49** A.C. equivalent circuit of two stage R-C coupled amplifier

(1) **Input impedance.** The input impedance is a parallel combination of  $R_1$ ,  $R_2$ , and  $h_{ie}$ . i.e.,

$$Z_i = R_1 \parallel R_2 \parallel h_{ie}$$

(2) **The Output impedance.** The output impedance is a parallel combination of  $R_{C2}$  and  $R_L$ .  
Hence

$$Z_o = R_{C2} \parallel R_L$$

(3) **Voltage gain  $(A_v)_m$ .** The overall gain is given by

$$(A_v)_m = A_1 \times A_2$$

where,  $A_1$  is the gain of first stage and  $A_2$ , the gain of second stage.

$$A_1 = \frac{-h_{fe} (R_{ac})_1}{h_{ie}} \text{ where } (R_{ac})_1 = \text{output resistance of first transistor}$$

$$(R_{ac})_1 = R_{C1} \parallel R_1 \parallel R_2 \parallel h_{ie}$$

$$\text{and } A_2 = \frac{-h_{fe} (R_{ac})_2}{h_{ie}}, \text{ where } (R_{ac})_2 = \text{Output resistance of second transistor}$$

$$(R_{ac})_2 = R_{C2} \parallel R_L$$

**Example 2.** A transistor is connected as a common-emitter amplifier with load resistance  $R_L = 10 \text{ k}\Omega$ . The  $h$ -parameters are  $h_{ie} = 5 \text{ k}\Omega$  and  $h_{fe} = 330$ . Calculate the overall voltage gain for mid frequency range when four such stages are connected in cascade by RC coupling. Assume that source resistance is negligible to  $h_{ie}$ .

The gain of R-C coupled amplifier at mid-frequency range is given by

$$(A_v)_m = - \frac{h_{fe} R_L}{h_{ie} + R_L}$$

$$\text{For first stage, } (A_{v1})_m = - \frac{330 \times 10}{5 + 10} = - \frac{3300}{15} = - 220$$

$$\text{For second stage, } (A_{v2})_m = - \frac{330 \times 10}{5 + 10} = - 220$$

$$\text{For third stage, } (A_{v3})_m = - 220$$

$$\text{For fourth stage, } (A_{v4})_m = - \frac{h_{fe} R_L}{h_{ie}}$$

because the output of the fourth stage appears across  $R_L$  only

$$= - \frac{330 \times 10}{5} = - 660$$

$$\therefore (A_v)_m = (A_{v1})_m \times (A_{v2})_m \times (A_{v3})_m \times (A_{v4})_m = 7 \times 10^9$$

**Example 3.** A two-stage common emitter R-C coupled amplifier uses transistor of the type BC 149 B of which the  $h$ -parameters are  $h_{ie} = 4.5 \text{ k}\Omega$  and  $h_{fe} = 330$ . If the load resistance  $R_L = 5.5 \text{ k}\Omega$ , find the required value of the coupling capacitor  $C$  so that the lower cut-off frequency is 60 Hz.

We know that lower cut-off frequency  $f_1$  is given by

$$f_1 = \frac{1}{2\pi C (h_{ie} + R_L)}$$

$$C = \frac{1}{2\pi f_1 (h_{ie} + R_L)}$$

Substituting the given values, we get

$$C = \frac{1}{2 \times 3.14 \times 60 \{(4.5 + 5.5) \times 10^3\}} = \frac{10^{-5}}{2 \times 3.14 \times 6} \text{ F}$$

$$= 0.026 \times 10^{-5} \text{ F} = 0.26 \mu\text{F}$$

**Example 4.** Design the circuit shown in fig. (11.50), called as Cascade circuit, to meet the following specifications:

$$V_{ce1} = V_{ce2} = 2.5 \text{ V}, V_{RE} = 0.7, I_{c1} = I_{c2} \approx 1 \text{ mA}$$

$$\text{and } I_{R1} \approx I_{R2} \approx I_{R3} \approx 0.10 \text{ mA}$$

Neglecting base currents,

$$I_{\text{Bias}} = I_{R1} = I_{R2} = I_{R3} = 0.10 \text{ mA}$$

$$\text{Now, } R_1 + R_2 + R_3 = \frac{V_{CC}}{I_{\text{Bias}}} = \frac{9}{0.10} = 90 \text{ k}\Omega$$

The voltage,  $V_{B1}$  at the base of  $Q_1$  is given by

$$V_{B1} = V_{RE} + V_{BE(\text{on})} = 0.7 + 0.7 = 1.4 \text{ V}$$

$$\therefore R_3 = \frac{V_{B1}}{I_{\text{Bias}}} = \frac{1.4}{0.10} = 14 \text{ k}\Omega$$

The voltage  $V_{B2}$  at the base of  $Q_2$  is given by

$$V_{B2} = V_{RE} + V_{CE1} + V_{BE(\text{on})}$$

$$= 0.7 + 2.5 + 0.7 = 3.9 \text{ V}$$

$$\therefore R_2 = \frac{V_{B2} - V_{B1}}{I_{\text{Bias}}} = \frac{3.9 - 1.4}{0.10} = 25 \text{ k}\Omega$$

Now we obtain

$$R_1 = 90 - R_2 - R_3 = 90 - 25 - 14 = 51 \text{ k}\Omega$$

The emitter resistor  $R_E$  is given by

$$R_E = \frac{V_{RE}}{I_{C1}} = \frac{0.7}{1} = 0.7 \text{ k}\Omega$$

The voltage at the collector of  $Q_2$  is

$$V_{C2} = V_{RE} + V_{CE1} + V_{CE2} = 0.7 + 2.5 + 2.5 = 5.7 \text{ V}$$

$$\therefore R_C = \frac{V_{CC} - V_{C2}}{I_{C2}} = \frac{9 - 5.7}{1} = 3.3 \text{ k}\Omega$$

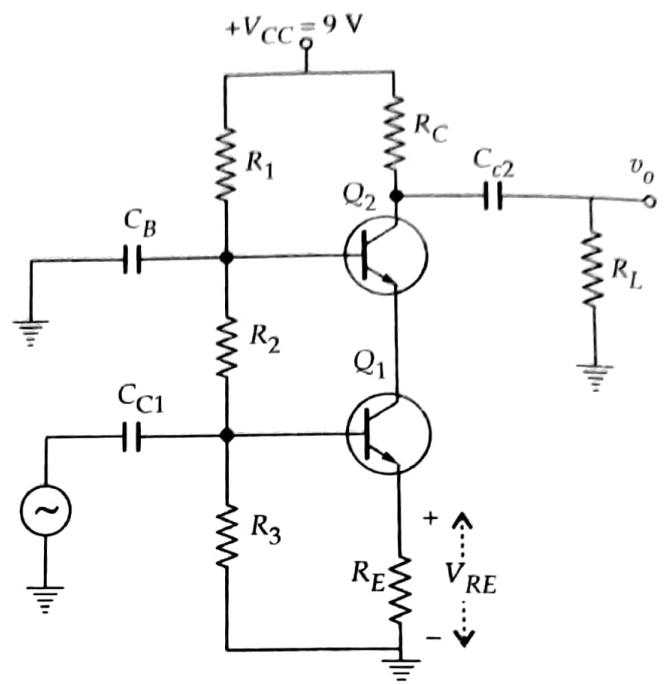


Fig. 11.50 Cascade circuit

**Example 1.** The parameters of a transistor two stages R – C coupled amplifier are  $h_{fe} = 50$ ,  $h_{ie} = 1.1 \text{ k}\Omega$ ,  $h_{oe} = 0$ , and  $R_L = 2 \text{ k}\Omega$ . Find (a) mid band gain, (b) value of coupling capacitor C to give a lower 3 db frequency of 20 Hz, (c) the value of C necessary to ensure less than 10% tilt for a 100 Hz square wave input.

$$(a) (A_v)_m = \frac{h_{fe} R_L}{h_{ie} + R_L} = \frac{50 \times (2 \times 10^3)}{(1.1 \times 10^3) + (2 \times 10^3)} = 32.26$$

(b) The lower cut-off frequency  $f$  is given by

$$f_1 = \frac{1}{2\pi C (h_{ie} + R_L)}$$

or 
$$20 = \frac{1}{2\pi \times C [(1.1 \times 10^3) + (2 \times 10^3)]}$$

Solving for C, we get


$$C = 2.567 \mu\text{F}$$

(c) Percentage tilt,  $P = \frac{\pi f_1}{f} \times 100$

$$\therefore f_1 = \frac{P f}{\pi \times 100} = \frac{10 \times 100}{100 \pi} = \frac{10}{\pi} \text{ Hz}$$

and 
$$C = \frac{1}{2\pi \times (10/\pi) [(1.1 \times 10^3) + (2 \times 10^3)]} = 16.13 \mu\text{F}$$


**Example 1.** The amplifier shown in fig. [11-21 (a)] uses a transistor with the following parameters:  
 $h_{ie} = 1.1 \text{ k}\Omega$ ,  $h_{fe} = 50$ ,  $h_{re} = 2.5 \times 10^{-4}$ ,  $h_{oe} = 25 \times 10^{-6} \text{ A/V}$

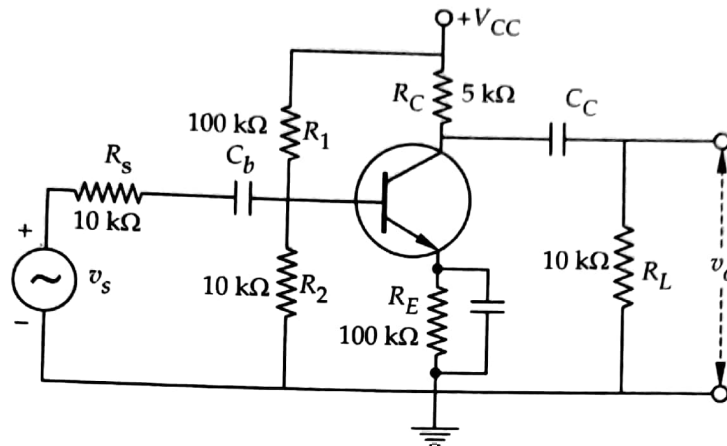

**Fig. 11-21 (a)**

Calculate: (i)  $A_i$  and  $A_{is}$ , (ii)  $A_v$  and  $A_{vs}$ , (iii)  $R_o'$  and  $R_i'$

The approximate hybrid equivalent circuit is shown in fig. [11-21 (b)].

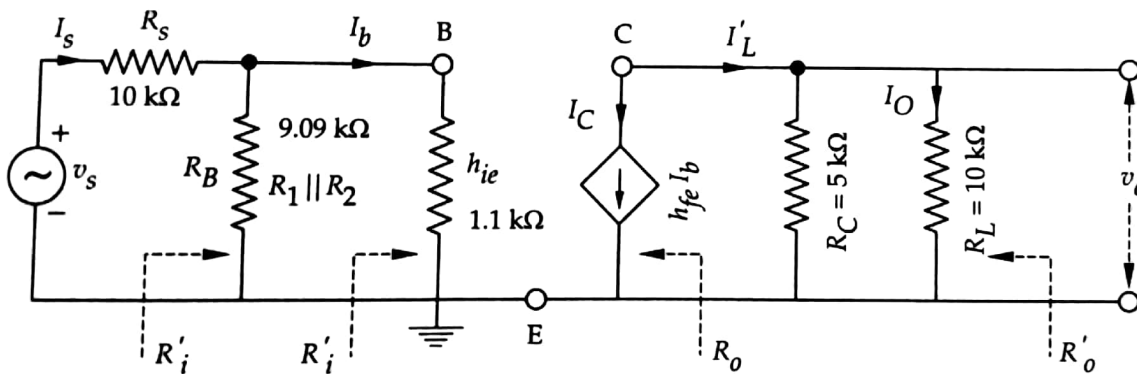

**Fig. 11-21 (b) Equivalent circuit**

From fig. [11-21 (b)],  $R_i = h_{ie} = 1.1 \text{ k}\Omega$

and  $R_i' = h_{ie} \parallel R_B = 1.1 \text{ k}\Omega \parallel (9.09 \text{ k}\Omega) = 981.26 \Omega$

(i)  $A_i = \frac{I_L'}{I_b} = \frac{h_{fe} I_b}{I_b} = h_{fe} = -50$

$$A_{is} = \frac{I_L}{I_s} = \frac{I_L}{I_C} \times \frac{I_C}{I_b} \times \frac{I_b}{I_s}$$

From fig. [11-21 (b)],  $\frac{I_L}{I_C} = \frac{-R_C}{(R_C + R_L)} \cdot \frac{I_C}{I_b} = h_{fe}$  and  $\frac{I_b}{I_s} = \frac{R_B}{(h_{ie} + R_B)}$

$$\therefore A_{is} = \frac{-R_C h_{fe} R_B}{(R_C + R_L)(h_{ie} + R_B)}$$

where  $R_B = (R_1 \parallel R_2) = 9.09 \text{ k}\Omega$ .

Substituting all the values, we get

$$A_{is} = -\frac{(5 \times 10^3) \times 50 \times 9.09 \times 10^3}{[(5 + 10) \times 10^3][9.09 \times 10^3]} = -14.87$$

$$\text{(ii) } A_v = A_i \times (R_L' / R_i) = A_i \left[ \frac{(R_C \parallel R_L)}{R_i} \right]$$

$$= -50 \left[ \frac{3.33 \text{ k}\Omega}{1.1 \text{ k}\Omega} \right] = -151.52 \quad (\text{where } R_C \parallel R_L = 3.33 \text{ k}\Omega)$$

$$A_{vs} = A_v \times \left[ \frac{R_i'}{R_i' + R_s} \right] = -151.52 \times \left[ \frac{981.26}{981.26 + (10 \times 10^3)} \right]$$

or  $A_{vs} = -13.54$

**(iii)** Here,  $R_o = \infty$

and  $R_o' = (R_o \parallel R_C \parallel R_L) = \infty \parallel (R_C \parallel R_L) = (R_C \parallel R_L)$

$$R_o' = (5 \text{ k}\Omega \parallel 10 \text{ k}\Omega) = 3.33 \text{ k}\Omega$$