

19.7 THE MOS DIFFERENTIAL AMPLIFIER WITH ACTIVE LOAD

We know that if the drain resistance R_D of MOSFET amplifier is replaced by a constant current source, then this results in much higher voltage gain. The same idea applies to differential amplifier. The aim of this article is to consider the active loaded differential amplifier and converting the output from differential to a single ended. The term *active load* refers to the use of current source in place of resistor as a load in the amplifier configuration.

19.7.1 DIFFERENTIAL-TO-SINGLE-ENDED CONVERSION

We have considered the differential amplifier in which the output was taken between two drains (or collectors). This result in the double value of differential gain. Now, we consider the basic approach for differential to single-ended conversion in which the output is taken between the drain (or collector) of one transistor and ground. This is known as differential-to-single-ended conversion.

Figure (19.37) shows the simplest basic approach for differential-to-single ended conversion.

 


Fig. 19-37 Simple approach for differential to single-ended conversion

In the circuit we ignore the drain current signal of transistor Q_1 and eliminate its drain resistor. The output is taken between drain of transistor Q_2 and ground. In such a situation, the gain reduces to half. Therefore, the drain current of Q_1 may be utilized in some other applications.

19.7-2 THE ACTIVE-LOADED MOS DIFFERENTIAL PAIR

We can use an active load in conjunction with MOSFET differential pair. Figure (19.38) shows a MOSFET differential amplifier formed by transistor Q_1 and Q_2 with an active load formed by transistors Q_3 and Q_4 . These are known as current mirrors.

When common-mode input signal is applied.

To consider the operation of the circuit, let the two input terminals are connected to a d.c. voltage. In this case the output voltage will be zero. Let us consider the situation shown in fig. (19.39). We assume that the circuit is in perfect matching. The bias current I is equally divided between Q_1 and Q_2 . Now the

 


Fig. 19-38 Active loaded MOS differential pair

drain current $\left(\frac{I}{2}\right)$ of Q_1 is fed to the input of transistor of mirror Q_3 . Further, a replica of this current is provided by the output transistor of the mirror Q_4 . The drain voltage of Q_4 will track the voltage at the drain of Q_3 . Therefore, the voltage at the output will be $V_{DD} - V_{SG3}$.

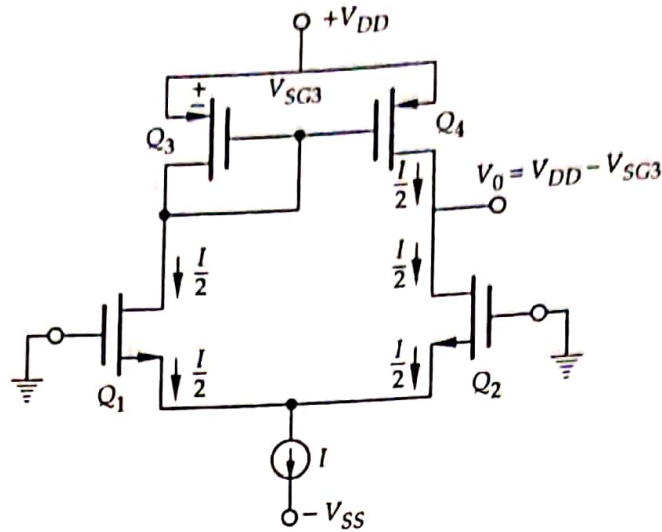


Fig. 19-39 Circuit at equilibrium

When differential-mode input signal is applied

Next, we consider the circuit with a differential input signal v_{id} applied to the input as shown in fig. (19-40).

 


Fig. 19-40 Circuit with differential input signal applied

When small signal input is applied, then in the equivalent circuit all the d.c. sources including I are removed. We also ignore r_0 of all the transistors. It is obvious from the fig. (19-40) that a virtual ground will develop at common-source terminal of Q_1 and Q_2 . Transistor Q_1 conducts a current $i = g_{m1}(v_{id}/2)$ and Q_2 also conducts an equal current but in opposite direction. The drain signal current of Q_1 is fed to the input of $Q_3 - Q_4$ mirror. As a result, the transistor Q_4 provided a drain current i . Now, the output current is $2i$. The factor 2 is a result of current mirror action. If a load resistance is connected to the output node, the current $2i$ will flow through it giving an output voltage v_0 . In the absence of the output load, the output voltage will be determined by the output current $2i$ and output resistance of the circuit.

19.7-3 DIFFERENTIAL GAIN OF THE ACTIVE-LOADED MOS PAIR (A_d)

The aim of this article is to derive an expression for the differential gain (v_o/v_{id}) of active loaded MOS differential pair. We shall also take into consideration the input resistance r_0 of the transistor.

Figure (19-41) shows a MOSFET differential amplifier with active load. Q_1 and Q_2 are n -channel devices and form the differential pair. The differential pair is biased with a current source I . The load circuit consists of transistors Q_3 and Q_4 both p -channel devices and connected in current mirror configuration. A one sided output is taken from the common drains of Q_2 and Q_4 .

 


Fig. 19-41 MOSFET differential amplifier with active load

When a common-mode voltage of $v_1 = v_2 = v_{CM}$ is applied, the current I splits evenly between Q_1 and Q_2 . In this case, $I_{D1} = I_{D2} = I/2$. Further, there are no gate currents, i.e. $i_{D3} = i_{D1}$ and $i_{D4} = i_{D2}$.

If a small differential mode input voltage $v_{id} = v_1 - v_2$ is applied then the drain currents i_{D1} and i_{D2} of transistors Q_1 and Q_2 are expressed as

$$i_{D1} = \frac{I}{2} + i_d \quad \dots(1)$$

and

$$i_{D2} = \frac{I}{2} - i_d \quad \dots(2)$$

where i_d is signal current.

For small value of v_{id} , we have

$$i_d = \frac{(g_m v_{id})}{2} \quad \dots(3)$$

It is obvious from the fig. (19-41) that M_1 and M_3 are in series, therefore,

$$i_{D3} = i_{D1} = \frac{I}{2} + i_d \quad \dots(4)$$

As M_3 and M_4 constitute the current mirrors and hence,

$$i_{D4} = i_{D3} = \frac{I}{2} + i_d \quad \dots(5)$$

Figure (19-42) shows the equivalent circuit of differential amp. with active load and showing the signal currents.

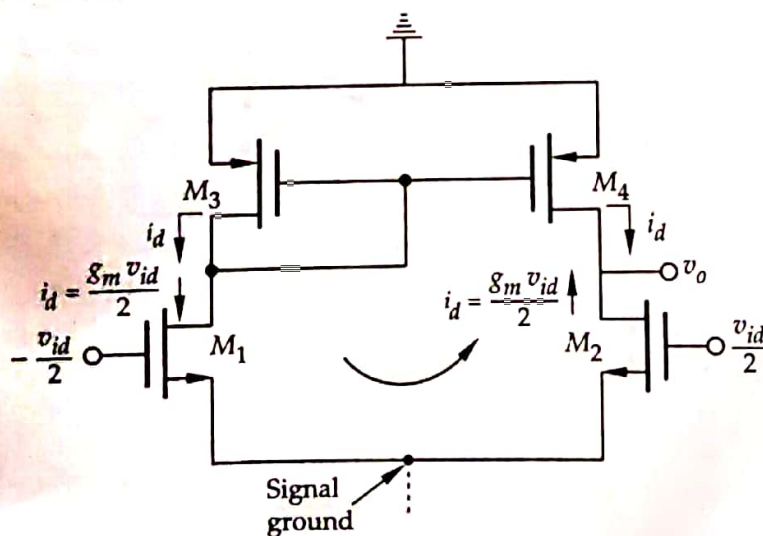


Fig. 19-42 Equivalent circuit of MOSFET differential amplifier with active load

Figure [19.43 (a)] shows the a.c. equivalent circuit of diff. amp. with active load at the drain node of M_2 and M_4 . The circuit is rearranged by combining the signal grounds at a common point as shown in fig. [19.43 (b)].

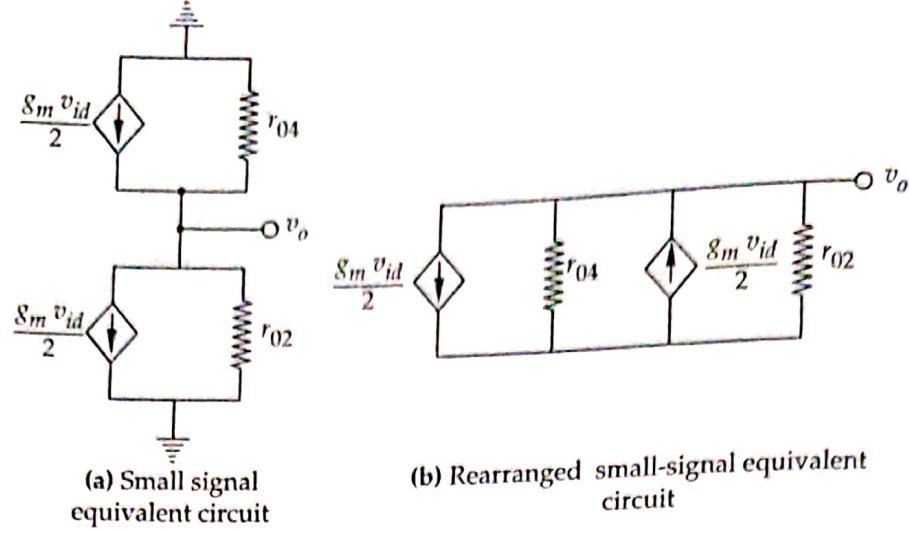


Fig. 19.43

From fig. [19.43 (b)]
$$v_0 = 2 \left(\frac{g_m v_{id}}{2} \right) (r_{02} \parallel r_{04}) \quad \dots(6)$$

Therefore, small signal differential-mode voltage gain is

$$A_d = \frac{v_0}{v_{id}} = g_m (r_{02} \parallel r_{04}) \quad \dots(7)$$

In case $r_{02} = r_{04} = r_0$, then

$$A_d = \frac{1}{2} g_m r_0 = \frac{A_0}{2} \quad \dots(8)$$

where A_0 is the intrinsic gain of MOS transistor.

19.7-4 OUTPUT RESISTANCE R_0

Figure (19.44) shows the circuit for determining the output resistance R_0 . The current distribution is also shown in the figure.

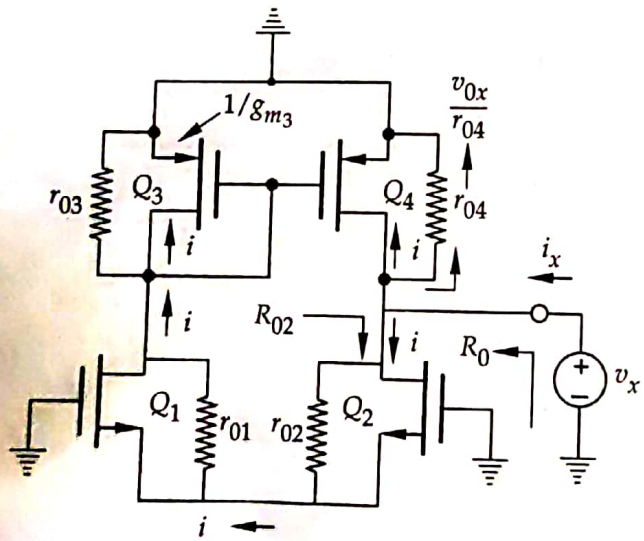


Fig. 19.44 Circuit for determining R_0

The transistor Q_2 is a common gate transistor. Its source lead is connected to the input resistance of transistor Q_1 . The latter is connected in common gate configuration with a small resistance in the drain. This is approximately equal to $\frac{1}{g_{m3}}$. Therefore, the input resistance is approximately $\frac{1}{g_{m1}}$. Now, the output resistance of transistor Q_2 is

$$R_{02} = r_{02} + (1 + g_{m2} r_{02}) \left(\frac{1}{g_{m1}} \right)$$

or
At the output, node,

$$R_{02} = 2 r_{02} \quad (\because g_{m2} r_{02} \gg 1 \text{ and } g_{m1} = g_{m2} = g_m) \quad \dots(9)$$

$$i_x = i + i + \left(\frac{v_x}{r_{04}} \right) = \left(2i + \frac{v_x}{r_{04}} \right) \quad \dots(10)$$

or

$$i_x = 2 \left(\frac{v_x}{R_{02}} \right) = \left(\frac{v_x}{r_{04}} \right)$$

or

$$i_x = 2 \left(\frac{v_x}{2r_{02}} \right) + \left(\frac{v_x}{r_{04}} \right) = \left(\frac{v_x}{r_{02}} + \frac{v_x}{r_{04}} \right)$$

or

$$i_x = v_x \left[\frac{1}{r_{02}} + \frac{1}{r_{04}} \right] = v_x \left(\frac{r_{04} + r_{02}}{r_{02} r_{04}} \right)$$

The output resistance R_0 is given by

$$R_0 = \frac{v_x}{i_x} = (r_{02} \parallel r_{04}) \quad \dots(11)$$

Therefore,

$$R_0 = (r_{02} \parallel r_{04})$$

The differential gain is given by $A_d = \frac{v_0}{i_d} = g_m R_0$

$$A_d = g_m (r_{02} \parallel r_{04}) \quad \dots(12)$$

19.7-5 DETERMINATION OF TRANSCONDUCTANCE (G_m)

Figure (19.45) shows the circuit arrangement for determining G_m . In the circuit, the output current is short circuited to ground to find G_m . Now, the circuit becomes symmetrical because the voltage between drain of Q_1 and ground is very small. This is due to low resistance between that node and ground which is equal to $1/g_{m3}$. The simplified equivalent circuit of each pair is shown in fig. [19.46 (a) and (b)].

From fig. [19.46 (a)], the voltage v_{gs3} is given by

$$v_{gs3} = -g_{m1} \left(\frac{1}{g_{m3}} \parallel r_{03} \parallel r_{01} \right) \quad \dots(13)$$

As r_{01} and $r_{03} \gg (1/g_{m3})$, eq. (13) can be written as

$$v_{gs3} \cong -g_{m1} \left(\frac{v_{id}}{2} \right) \left(\frac{1}{g_{m3}} \right) \cong - \left(\frac{g_{m1}}{g_{m3}} \right) \left(\frac{v_{id}}{2} \right) \quad \dots(14)$$

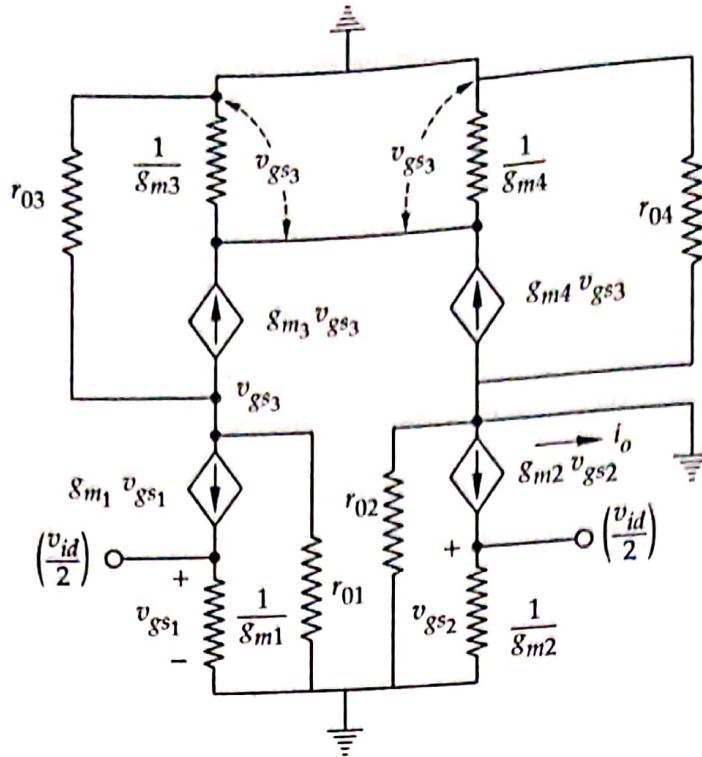


Fig. 19-45

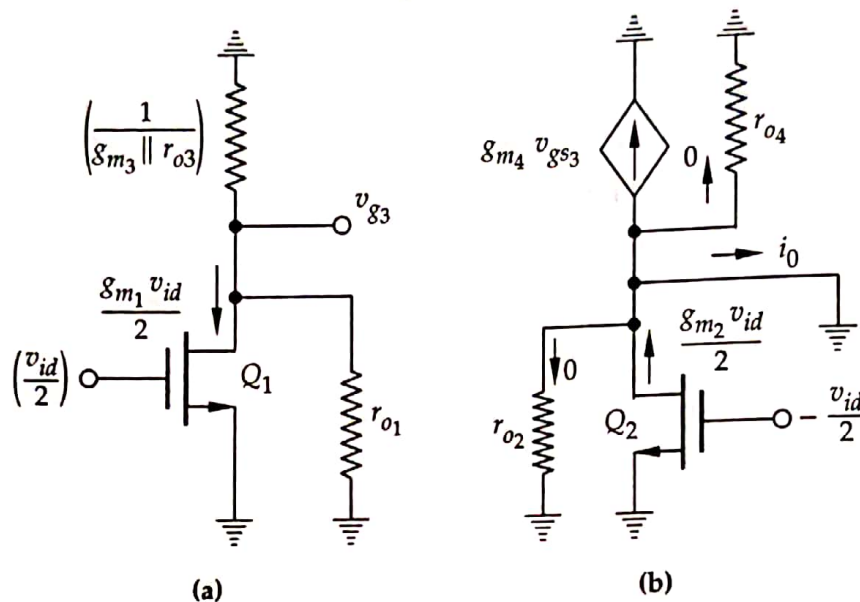


Fig. 19-46 Determination of transconductance G_m

This voltage controls the drain current of Q_4 resulting in a current $g_{m4} v_{gs3}$. The output current i_o is given by

$$i_o = -g_{m4} v_{gs3} + g_{m2} \left(\frac{v_{id}}{2} \right) \quad \dots(15)$$

It is important to mention here that ground at the output node causes the currents r_{o2} and r_{o4} to be zero as shown in fig. [19-46 (b)].

Substituting the value of v_{gs3} from eq. (14) in eq. (15) we get

$$i_o = g_{m4} \left(\frac{g_{m1}}{g_{m3}} \right) \left(\frac{v_{id}}{2} \right) + g_{m2} \left(\frac{v_{id}}{2} \right) \quad \dots(16)$$

If $g_{m3} = g_{m4}$ and $g_{m1} = g_{m2} = g_m$, then

$$i_0 = g_m \left(\frac{v_{id}}{2} \right) + g_m \left(\frac{v_{id}}{2} \right) \quad \dots(17)$$

or

$$i_0 = g_m v_{id}$$

Now

$$G_m = \left(\frac{i_0}{v_{id}} \right) = g_m \quad \dots(18)$$

19.7-6 COMMON-MODE GAIN (A_{CM})

The common mode MOS differential amplifier has a low gain but it has a high CMRR. Figure (19.47) shows the circuit with v_{iCM} applied and eliminating the power supplies. We have included the output resistance R_{SS} of bias current source. To make the circuit symmetrical, the contribution of R_{SS} is divided in the source of Q_1 and Q_2 as $2R_{SS}$. $2R_{SS}$ is usually much larger than $(1/g_m)$ of each of transistors Q_1 and Q_2 , and hence, the signals at the source terminals will be approximately equal to v_{iCM} . The effect of r_{o1} and r_{o2} is also negligibly small.

 


Fig. 19-47 Analysis of the active loaded MOS differential amplifier

The current i_1 and i_2 of transistors Q_1 and Q_2 respectively can be written as

We have,
$$i_1 = i_2 \cong \frac{(v_i)_{CM}}{2R_{SS}} \quad \dots(19)$$

The output resistance of each transistor can be obtained by using fig. (19.48).

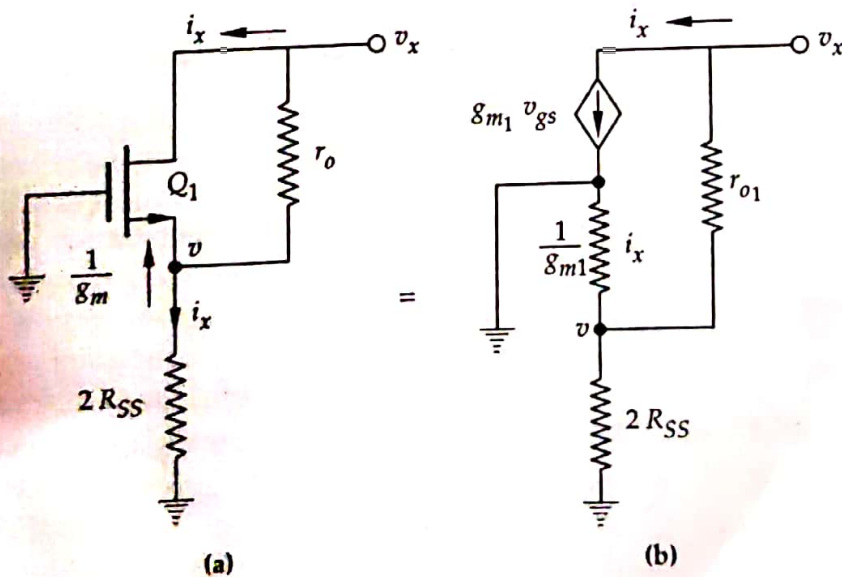


Fig. 19-48

The voltage at node v is given by

$$v = i_x (2 R_{SS}) = 2 i_x R_{SS}$$

Using circuit [19.48 (b)], we have

$$\begin{aligned} v_x &= i_x r_{01} + g_{m1} v + v \\ &= i_x r_{01} + 2 g_{m1} i_x R_{SS} r_{01} + 2 i_x R_{SS} \\ &= i_x [r_{01} + 2 g_{m1} R_{SS} r_{01} + 2 R_{SS}] \end{aligned}$$

Therefore, $R_{01} = r_{01} + 2 g_{m1} R_{SS} r_{01} + 2 R_{SS}$... (20)

or $R_{01} = R_{02} = r_0 + 2 R_{SS} + 2 g_m r_0 R_{SS}$

where $r_{01} = r_{02} = r_0$ and $g_{m1} = g_{m2} = g_m$. We can neglect R_{01} and R_{02} in finding the total resistance between each of the drain nodes and ground.

The current i_1 is passed through $[(1 / g_{m3}) \parallel r_{03}]$. This produces a voltage v_{g3} given by

$$v_{g3} = -i_1 \left(\frac{1}{g_{m3}} \parallel r_{03} \right) \quad \dots(21)$$

Resistor r_{04} senses this voltage and hence, provides a drain current i_4

$$i_4 = -g_{m4} v_{g3} = g_{m4} i_1 \left(\frac{1}{g_{m3}} \parallel r_{03} \right) \quad \dots(22)$$

Now, $v_0 = (i_4 - i_2) r_{04}$

or $v_0 = \left[g_{m4} i_1 \left(\frac{1}{g_{m3}} \parallel r_{03} \right) - i_2 \right] r_{04}$... (23)

or $v_0 = i_1 \left[g_{m4} \left(\frac{1}{g_{m3}} \parallel r_{03} \right) - 1 \right] r_{04} \quad (\because i_1 = i_2)$

$$= \frac{v_{iCM}}{2 R_{SS}} \left[g_{m4} \left(\frac{1}{g_{m3}} \parallel r_{03} \right) - 1 \right] r_{04}$$

$$= \frac{v_{iCM}}{2 R_{SS}} \left[g_{m4} \left(\frac{r_{03}}{g_{m3} r_{03} + 1} \right) - 1 \right] r_{04}$$

$$= \frac{v_{iCM}}{2 R_{SS}} \left[\frac{g_{m4} r_{03} - g_{m3} r_{03} - 1}{g_{m3} r_{03} + 1} \right] r_{04}$$

$$= \frac{v_{iCM}}{2 R_{SS}} \left[\frac{-1}{g_{m3} r_{03} + 1} \right] r_{04} \quad (\because g_{m3} = g_{m4})$$

$$\therefore v_0 = -\frac{v_{iCM} r_{04}}{2 R_{SS} (1 + g_{m3} r_{03})} \quad \dots(24)$$

Usually $g_{m3} r_{03} \gg 1$ and $r_{03} = r_{04}$. Therefore,

$$v_0 = i \frac{v_{iCM}}{2 R_{SS} g_{m3}}$$

Therefore,

$$A_{CM} = \frac{v_0}{v_{iCM}} = -\frac{1}{2 g_{m3} R_{SS}}$$

...(25)

19.7-7 COMMON MODE REJECTION RATIO (CMRR)

$$CMRR = \frac{|A_d|}{|A_{CM}|} = \frac{[g_m (r_{o1} \parallel r_{o4})]}{(1/2 g_{m3} R_{SS})}$$

or

$$CMRR = g_m (r_{o2} \parallel r_{o4}) \times (2 g_{m3} R_{SS})$$

...(26)

For $r_{o2} = r_{o4} = r_o$ and $g_{m3} = g_m$, we get

$$CMRR = g_m \left(\frac{r_o}{2} \right) \times 2 g_m R_{SS}$$

or

$$CMRR = (g_m r_o) (g_m R_{SS}) = g_m^2 r_o R_{SS}$$

...(27)