 


Half Adder

Half Adder- The addition of 2 bits is done using a combination circuit called a Half adder. The input variables are augend and addend bits and output variables are sum & carry bits. A and B are the two input bits.



Truth Table -

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Logical Expression:

1) For Sum:

A \ B	0	1
0	0	1
1	1	0


$$\text{Sum} = A \text{ X-OR } B$$

2) For Carry:

A \ B	0	1
0	0	0
1	0	1

$$\text{Carry} = A \cdot B$$


Implementation:

 

Note: Half adder has only two inputs and there is no provision to add a carry coming from the lower order bits when multi addition is performed.

Full Adder

Full Adder : It is the adder which adds three inputs and produces two outputs. The first two inputs are A and B and the third input is an input carry as C-IN. The output carry is designated as C-OUT and the normal output is designated as S which is SUM. A full adder logic is designed in such a manner that can take eight inputs together to create a byte-wide adder and cascade the carry bit from one adder to the another.

 

Truth Table:

Inputs			Outputs	
A	B	C-IN	Sum	C-Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Logical Expression for SUM:


$$\begin{aligned} &= A' B' C\text{-IN} + A' B C\text{-IN}' + A B' C\text{-IN}' + A B C\text{-IN} \\ &= C\text{-IN} (A' B' + A B) + C\text{-IN}' (A' B + A B') \\ &= C\text{-IN X-OR } A \text{ X-OR } B \\ &= \sum m (1,2,4,7) \end{aligned}$$

Logical Expression for C-OUT:

$$\begin{aligned} &= A B + B C\text{-IN} + A C\text{-IN} \\ &= \sum m (3,5,6,7) \end{aligned}$$

Implementation of Full Adder using Half Adders

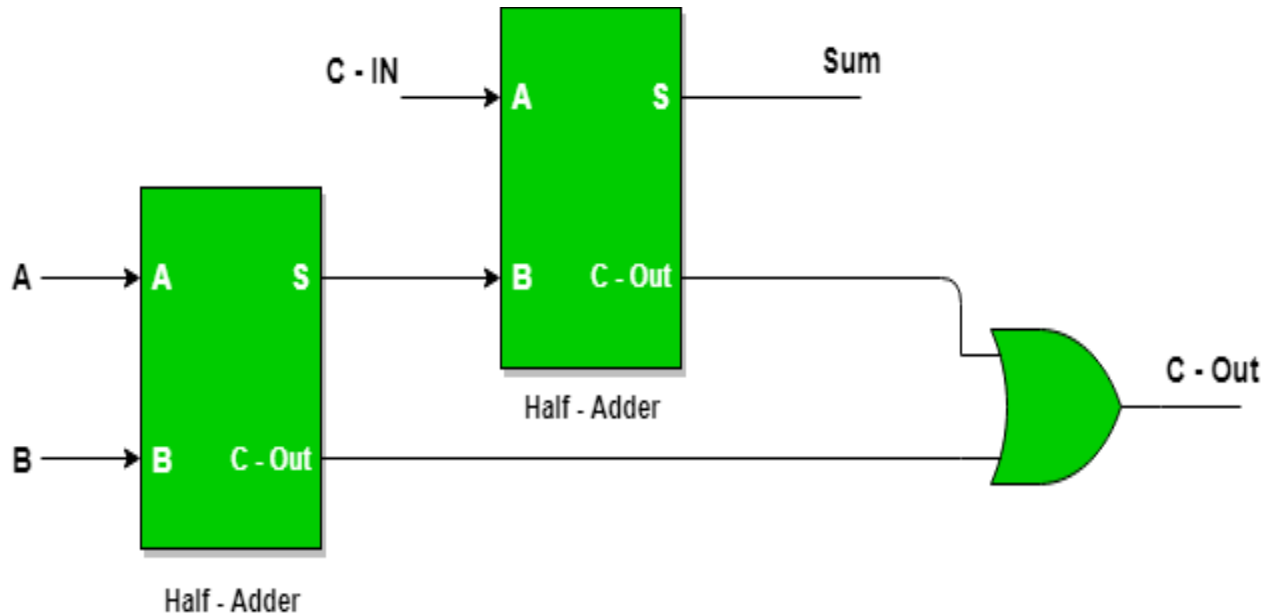2 Half Adders and a OR gate is required to implement a Full Adder.



With this logic circuit, two bits can be added together, taking a carry from the next lower order of magnitude, and sending a carry to the next higher order of magnitude.


Q1. Design and implement the following using half adder only.

$$D = A \text{ XOR } B \text{ XOR } C$$

$$E = A'BC + AB'C = (A'B + AB')C = (A \text{ XOR } B)C$$

$$F = AB'C + (A' + B')C = ABC' + A'B'C$$

$$G = ABC$$

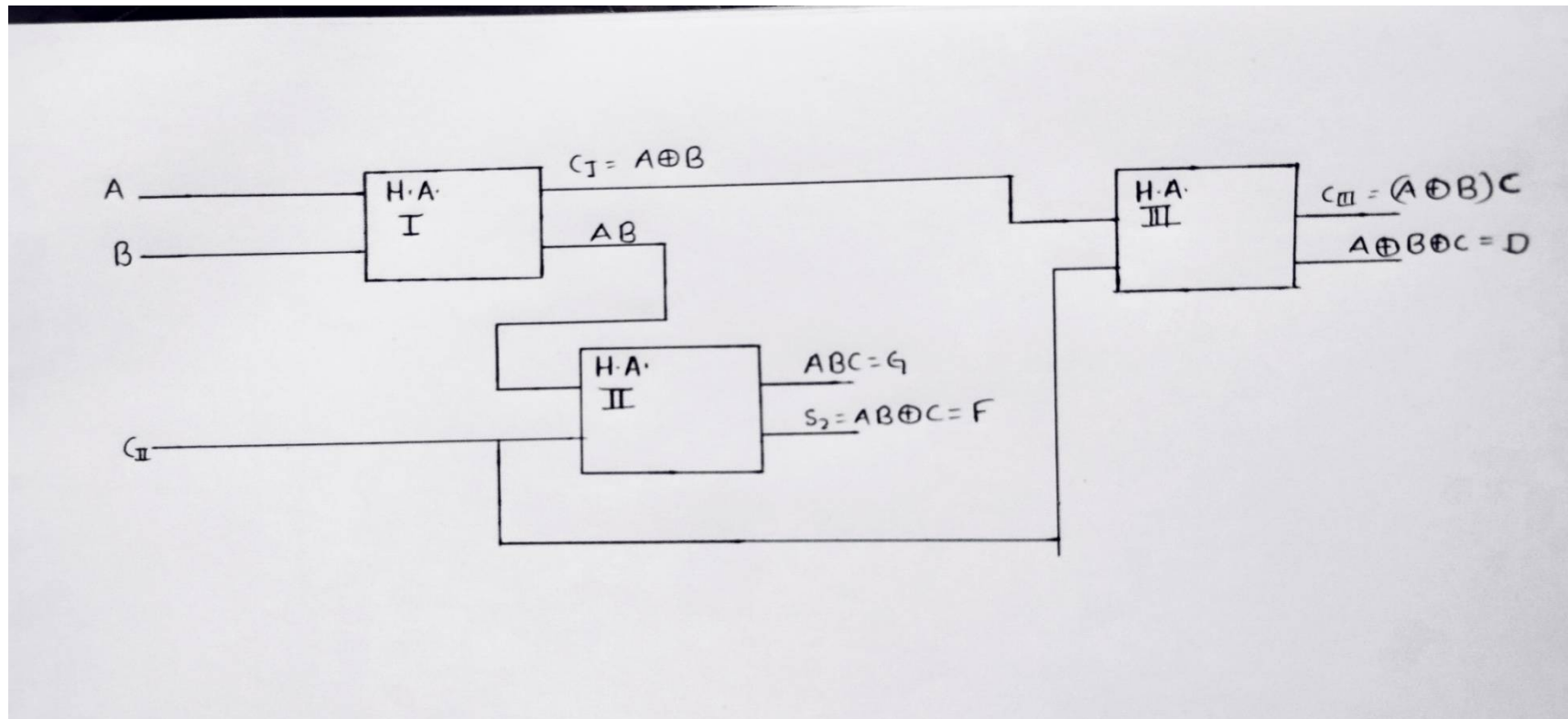


BCD ADDER


Procedure for BCD addition

1. Add two BCD numbers using ordinary binary addition.
2. If four-bit sum is equal to or less than 9, no correction is needed. The sum is in proper BCD form.
3. If the four-bit sum is greater than 9 or if a carry is generated from the four-bit sum, the sum is invalid.
4. To correct the invalid sum, add 0110_2 to the four-bit sum. If a carry results from this addition, add it to the next higher-order BCD digit.

Let A_3, A_2, A_1, A_0 and B_3, B_2, B_1, B_0 are two four-bit BCD numbers. these two BCD no. are added along with the carry in using 4-bit parallel binary adder as given below

1 st no.	A_3	A_2	A_1	A_0
2 nd no.	B_3	B_2	B_1	B_0
	S_3	S_2	S_1	S_0
	C_3	C_2	C_1	C_0
	S_3	S_2	S_1	S_0
	0	Y	Y	0
	0	0	0	0
	0	1	1	0

 

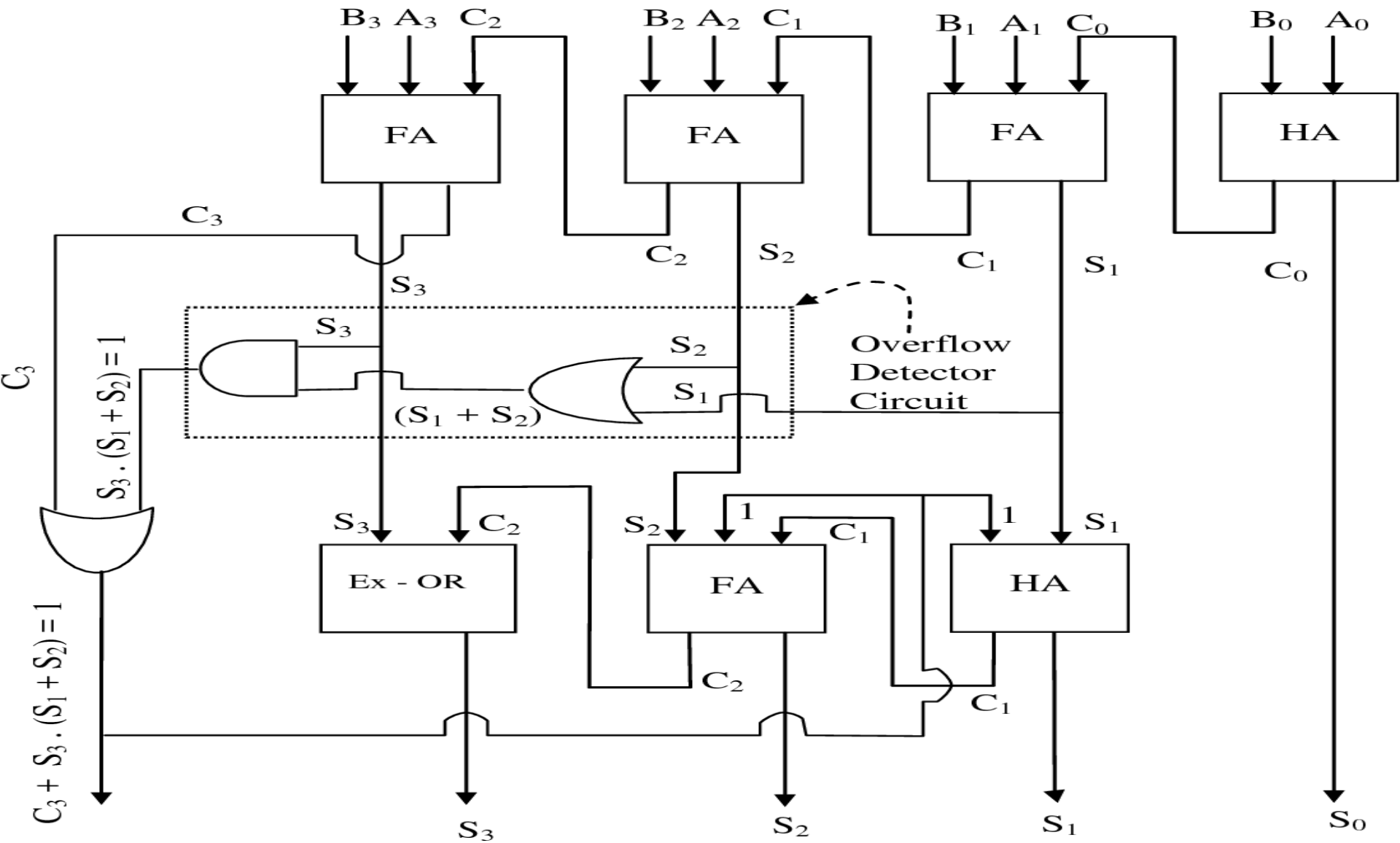

BCD Adder Block Diagram

The result obtained will be a binary no i.e; (C3 S3 S2 S1 S0) The logical circuit AND / OR gate is used to check the binary result obtained .

If (S3 S2 S1 S1) greater than 9 than , A=1 or B=1 , Hence Y=1. similarly if last carry C3 , then Y=1.

So when Y=1 , 6 (0 1 1 0) is added with a binary result.

If Y= 0 then , 0 (0 0 0 0) is added with a binary result .

Using half adder zero (HA₀) full adder (FA₄) and (HA₁) the addition of two numbers is performed as given below-

carry generated	C2'	C1'				
1 st No.	S3	S2	S1	S0		
2 ND NO.	0	Y	Y	0		
	Z3	Z2	Z1	Z0	----->	BCD RESULT