

1. Design NAND Gate logical circuit for implementing the SOPs equation.

$$Y = AB + BC + A'C + AB'C$$

soln

$$Y = AB \cdot 1 + 1 \cdot BC + A' \cdot 1 \cdot C + AB' \cdot C$$

$$Y = AB(C+C') + (A+A')BC + A'(B+B')C + AB'C$$


$$Y = ABC + ABC' + ABC + A'BC + A'BC + A'B'C + AB'C$$

$$Y = ABC + ABC' + A'BC + A'B'C + AB'C$$

1 1 1    1 1 0    0 1 1    0 0 1    1 0 1

$$\Sigma m = (1, 3, 5, 6, 7)$$

$$Y = C'' + A''B''$$

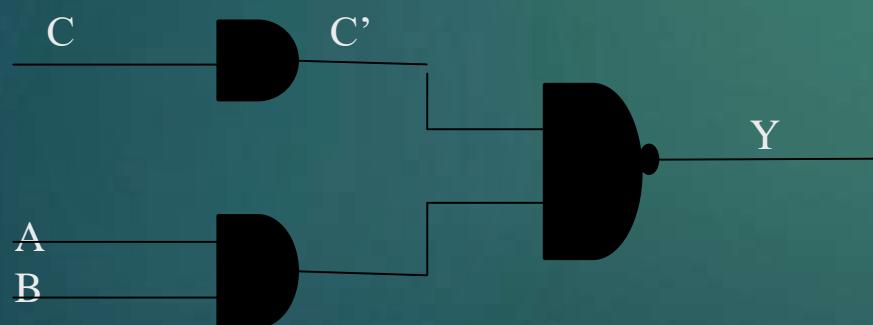

		A	0	1
		BC	00	
		00		
		01	1	1
		11	1	1
		10		1

2. Solve the logical function using k map

$$f(A,B,C,D) = A'B'C + AD + BD' + CD' + AC' + A'B'$$

soln

$$\begin{aligned} f(A,B,C,D) &= A'B'C \cdot 1 + AD \cdot 1 \cdot 1 + BD' \cdot 1 \cdot 1 + CD' \cdot 1 \cdot 1 + AC' \cdot 1 \cdot 1 + A'B' \cdot 1 \cdot 1 \\ &= A'B'C(D+D') + AD(B+B')(C+C') + BD'(A+A')(C+C') + CD'(A+A')(B+B') + AC'(B+B')(D+D') + \\ &\quad A'B'(C+C')(D+D') \\ &= A'B'CD + A'B'CD' + ABCD + ABC'D + AB'C'D + ABCD' + A'BCD' + ABC'D' + \\ &\quad A'BC'D' + ABCD' + AB'CD' + A'BCD' + A'B'CD' + ABC'D + ABC'D' + AB'C'D + AB'C'D' + \\ &\quad A'B'CD + A'B'CD' + A'B'C'D + A'B'C'D' \end{aligned}$$

$$f(A,B,C,D) = \Sigma m (0,1,2,3,4,6,8,9,10,11,12,13,14,15)$$

K-Map

		AB	00	01	11	10
		CD	00	01	11	10
		00	1	1	1	1
		01	1	0	1	1
		11	1	0	1	1
		10	1	1	1	1

$$Y = A + D' + B'$$

3. Solve the logical function using k-map  $F(A,B,C,D) = \Sigma m(1,2,4,7,8,11,13,14)$

Solution :

$$F(A,B,C,D) = \Sigma m(1,2,4,7,8,11,13,14)$$

k-map

AB	00	01	11	10
CD				
00		1		1
01	1		1	
11		1		1
10	1		1	

$$\begin{aligned} &= A'BCD + AB'CD + ABC'D + ABCD' + A'B'C'D + A'B'CD' + A'BC'D' + AB'C'D' \\ &= (A'B + AB')C'D' + (A'B' + AB)C'D + (A'B + AB')CD + (A'B' + AB)CD' \\ &= (A'B + AB')(C'D' + CD) + (A'B' + AB)(C'D + CD') \\ &= (A \oplus B)(C \odot D) + (A \odot B)(C \oplus D) \end{aligned}$$

Let  $(A \oplus B) = X, (C \oplus D) = Y$


Now  $F(A, B, C, D)$

$$= XY' + X'Y$$

$$= (X \oplus Y)$$

Now putting the values
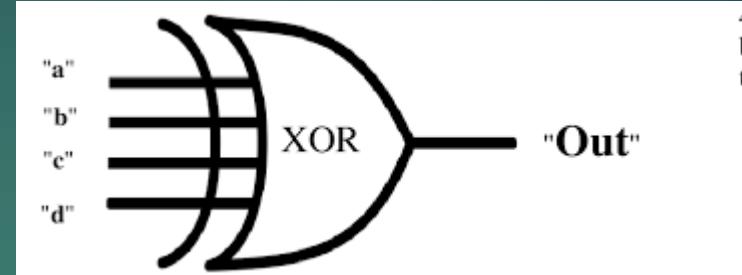
$$F(A, B, C, D) = (A \oplus B \oplus C \oplus D)$$



#### 4. Design Code converter

- a) Binary code to gray code converter.
- b) Gray code to Binary code converter.
- c) BCD Code to Excess-3 code converter.
- d) Excess-3 code to BCD code converter.

Solution:-

#### BINARY to GRAY CODE CONVERTER


\*K-map for  $g_0$

		b1,b0	00	01	11	10
		b3,b2	00	01	11	10
00	00	0	1	0	1	
01	01	0	1	0	1	
11	11	0	1	0	1	
10	10	0	1	0	1	


The truth table for the conversion is-

Binary				Gray Code			
b <sub>3</sub>	b <sub>2</sub>	b <sub>1</sub>	b <sub>0</sub>	g <sub>3</sub>	g <sub>2</sub>	g <sub>1</sub>	g <sub>0</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0


K-map for g1:-

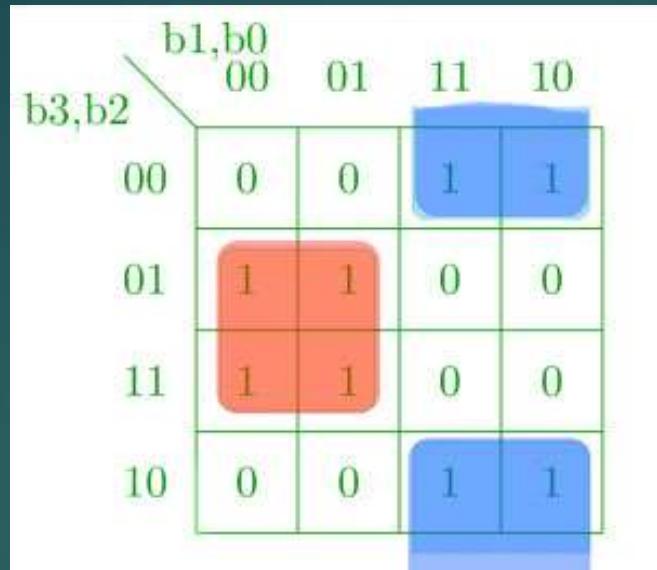

K-map for g2:-

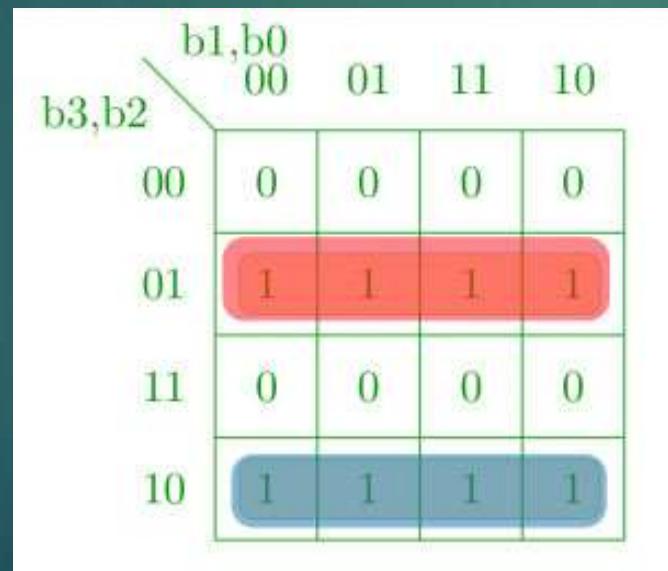

K-map for g3:-

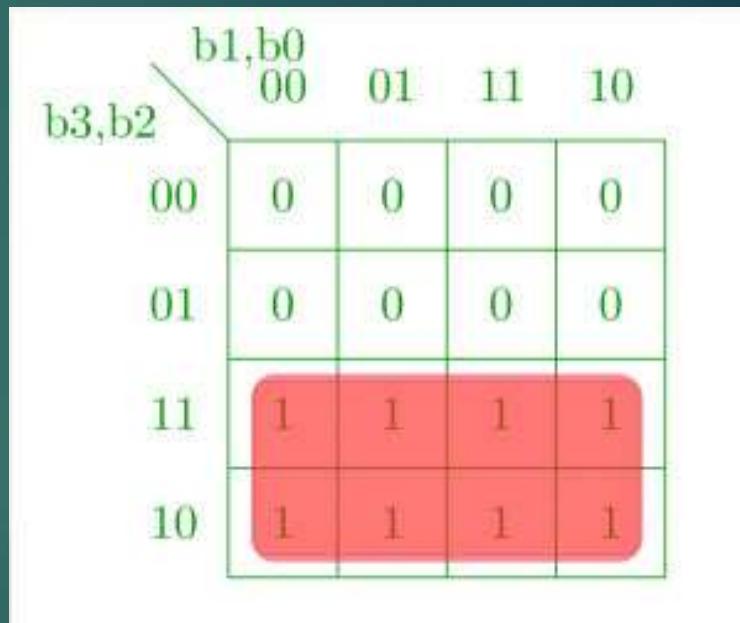

Corresponding minimized Boolean expressions for gray code bits


$$g_0 = b_0 b'_1 + b_1 b'_0 = b_0 \oplus b_1$$

$$g_1 = b_2 b'_1 + b_1 b'_2 = b_1 \oplus b_2$$

$$g_2 = b_2 b'_3 + b_3 b'_2 = b_2 \oplus b_3$$

$$g_3 = b_3$$

The corresponding digital circuit –

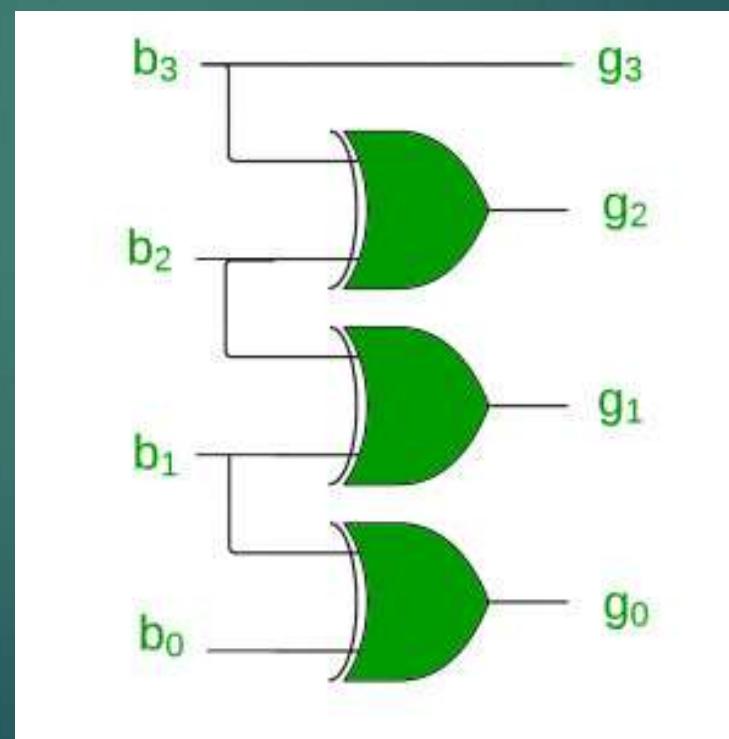

## Converting Gray Code to Binary :-


K-map for b<sub>0</sub> :-

		g <sub>1</sub> , g <sub>0</sub>	00	01	11	10
		g <sub>3</sub> , g <sub>2</sub>	00	01	11	10
		00	0	1	0	1
		01	1	0	1	0
		11	0	1	0	1
		10	1	0	1	0


Truth table:-

Gray Code				Binary			
g <sub>3</sub>	g <sub>2</sub>	g <sub>1</sub>	g <sub>0</sub>	b <sub>3</sub>	b <sub>2</sub>	b <sub>1</sub>	b <sub>0</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
1	0	0	0	1	1	1	1
1	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	0	1	0	1	1
1	1	1	1	1	0	1	0


K-map fro b1 :-

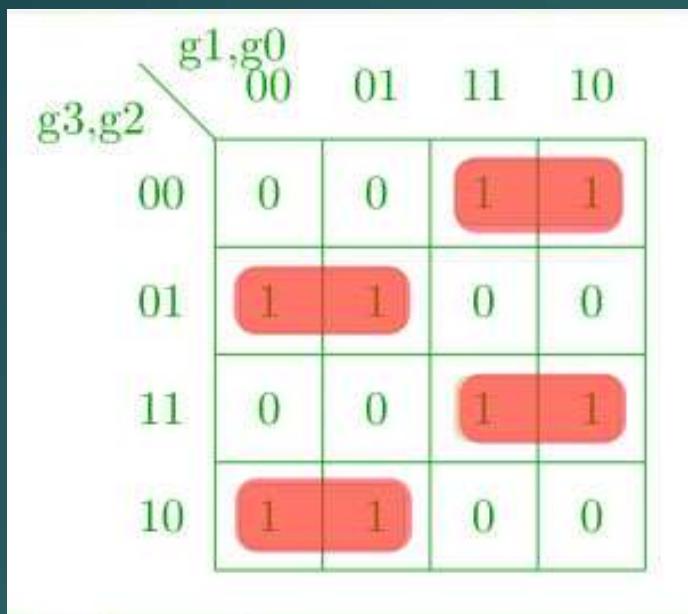

K-map fro b2 :-

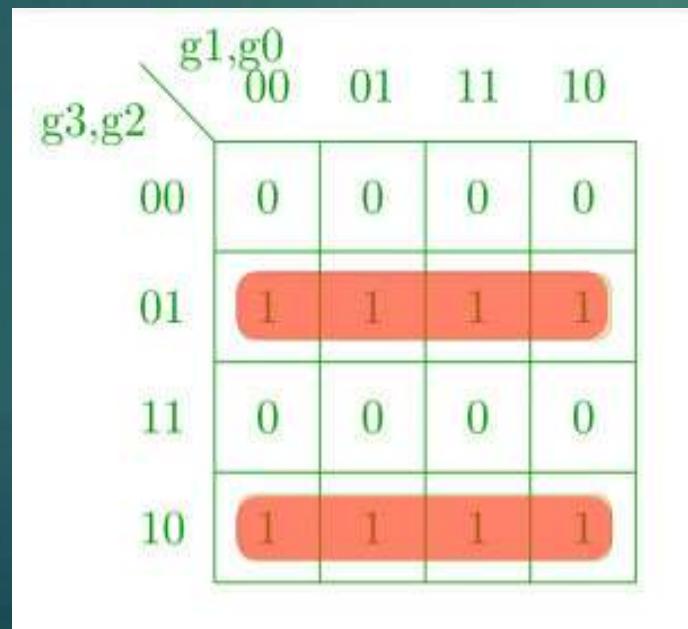

K-map fro b3 :-

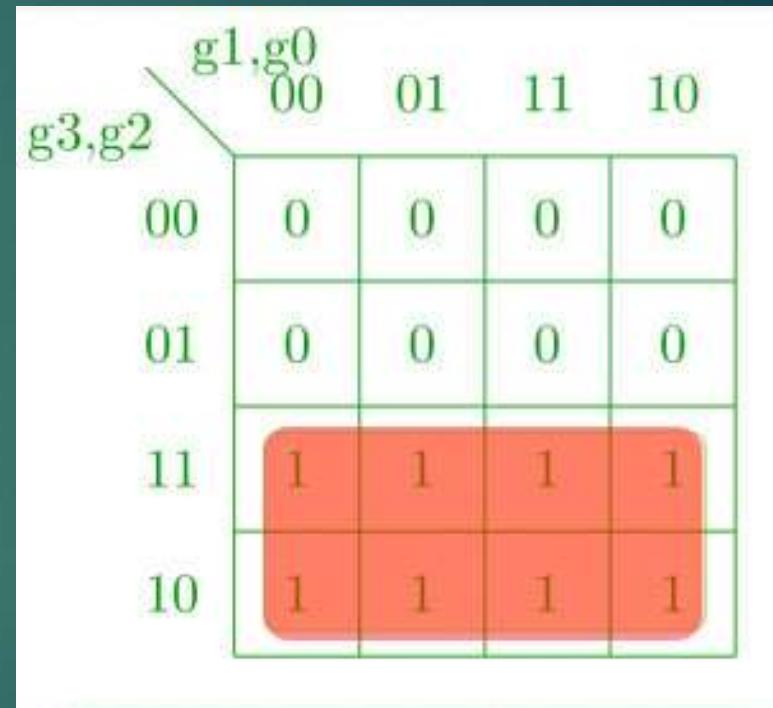

## Corresponding Boolean expressions –

$$\begin{aligned}b_0 &= g'_3g'_2g'_1g_0 + g'_3g'_2g_1g'_0 + g'_3g_2g'_1g'_0 + g'_3g_2g_1g_0 + g_3g'_2g'_1g'_0 + g_3g'_2g_1g_0 \\&\quad + g_3g_2g'_1g_0 + g_3g_2g_1g'_0\end{aligned}$$

$$\begin{aligned}&= g'_3g'_2(g'_1g_0 + g_1g'_0) + g'_3g_2(g'_1g'_0 + g_1g_0) + g_3g'_2(g'_1g'_0 + g_1g_0) \\&\quad + g_3g_2(g'_1g_0 + g_1g'_0)\end{aligned}$$

$$\begin{aligned}&= g'_3g'_2(g_0 \oplus g_1) + g'_3g_2(g_0 \odot g_1) + g_3g'_2(g_0 \odot g_1) + g_3g_2(g_0 \oplus g_1) \\&= (g_0 \oplus g_1)(g_2 \odot g_3) + (g_0 \odot g_1)(g_2 \oplus g_3)\end{aligned}$$

$$= g_3 \oplus g_2 \oplus g_1 \oplus g_0$$

$$b_1 = g'_3g'_2g_1 + g'_3g_2g'_1 + g_3g_2g_1 + g_3g'_2g'_1$$

$$= g'_3(g'_2g_1 + g_2g'_1) + g_3(g_2g_1 + g'_2g'_1)$$

$$= g'_3(g_2 \oplus g_1) + g_3(g_2 \odot g_1)$$


$$= g_3 \oplus g_2 \oplus g_1$$

$$b_2 = g'_3g_2 + g_3g'_2$$

$$= g_3 \oplus g_2$$




$$b_3 = g_3$$

## Corresponding digital circuit –

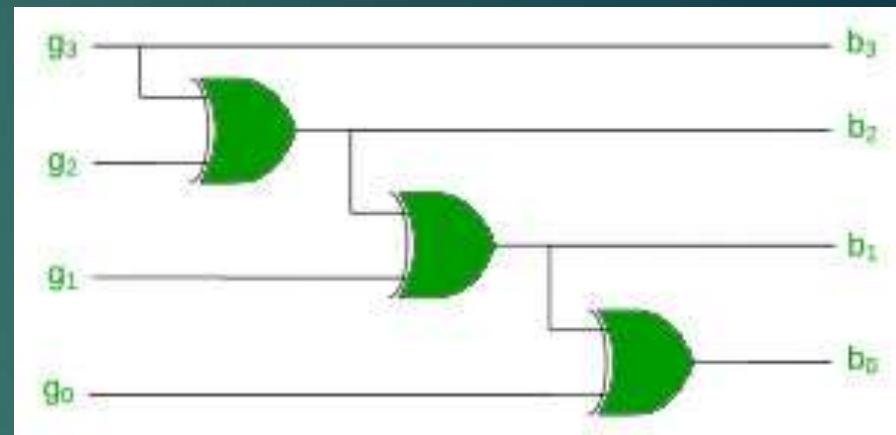
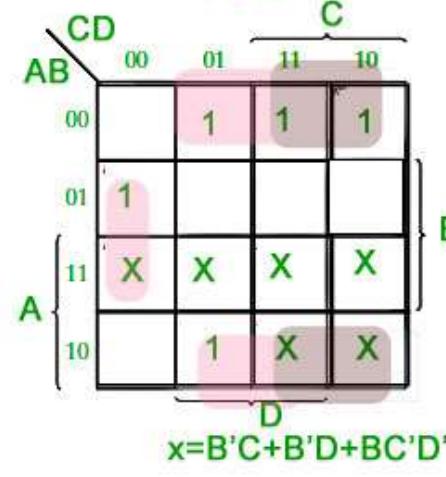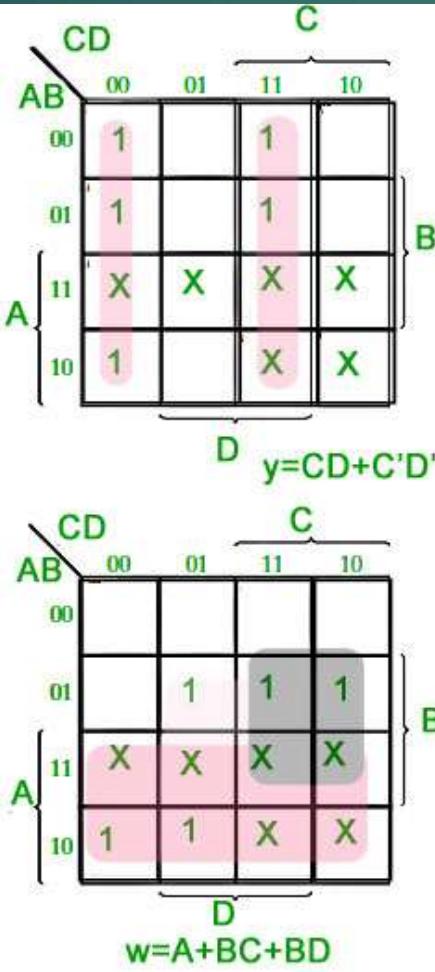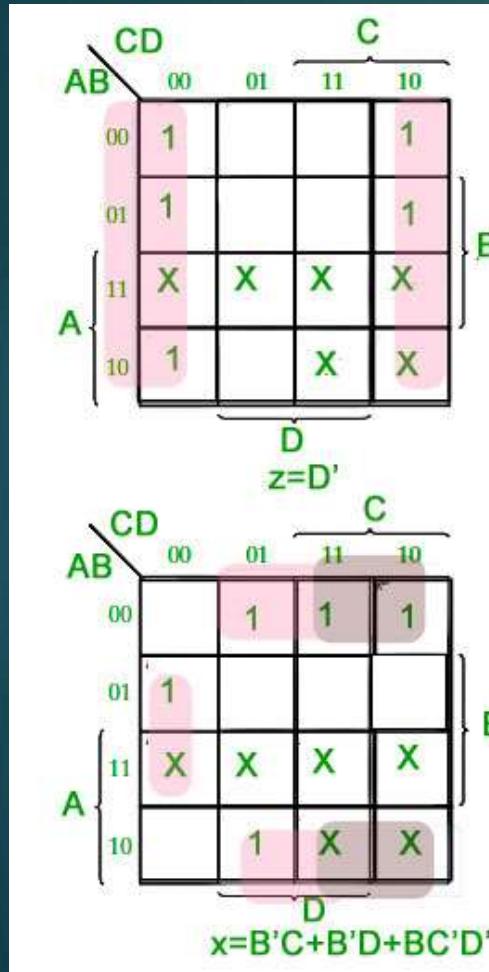
## BCD to Excess 3 code converter:-

To find the corresponding digital circuit, we will use the K-Map technique for each of the Excess-3 code bits as output with all of the bits of the BCD number as input.




BCD(8421)				Excess-3			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Corresponding minimized Boolean  
expressions for Excess-3 code bits –

$$\begin{aligned}w &= A + BC + BD \\x &= B'C + B'D + BC'D' \\y &= CD + C'D' \\z &= D'\end{aligned}$$

The corresponding digital circuit-

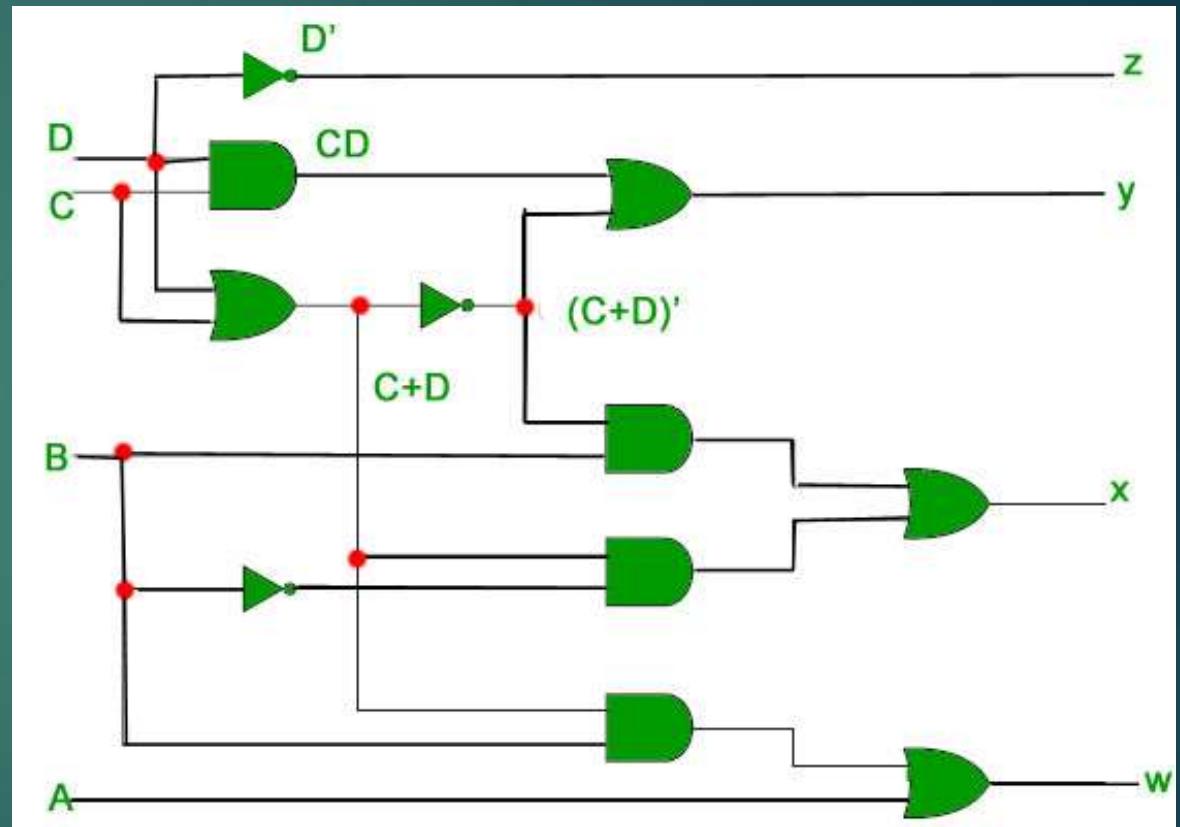

## Excess 3 to BCD code converter:-

K-map for D

wx \ yz	00	01	11	10
00	X	X	0	X
01	1	0	0	1
11	1	X	X	X
10	1	0	0	1

Excess-3				BCD			
w	x	y	z	A	B	C	D
0	0	0	0	X	X	X	X
0	0	0	1	X	X	X	X
0	0	1	0	X	X	X	X
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

K-map for C

wx \ yz	00	01	11	10
00	X	X	0	X
01	0	1	0	1
11	0	X	X	X
10	0	1	0	1

K-map for B

wx \ yz	00	01	11	10
00	X	X	0	X
01	0	0	1	0
11	0	X	X	X
10	1	1	0	1

K-map for A

wx \ yz	00	01	11	10
00	X	X	0	X
01	0	0	0	0
11	1	X	X	X
10	0	0	1	0

Corresponding minimized boolean expressions for Excess-3 code bits –

$$A = wx + wyz$$

$$B = x'y' + x'z' + xyz$$

$$C = y'z + yz'$$

$$D = z'$$

The corresponding digital circuit –

Here  $E_3, E_2, E_1, \text{ and } E_0$  correspond to  $w, x, y, \text{ and } z$  and

$B_3, B_2, B_1, \text{ and } B_0$  correspond to  $A, B, C, \text{ and } D$ .

