

SEQUENTIAL CIRCUITS

The Basic Latch



- ⊙ **Basic latch** is a feedback connection of two NOR gates or two NAND gates
- ⊙ It can store one bit of information

It can be set to 1 using the S input and reset to 0 using the R input


The Gated Latch

- ⊙ **Gated latch** is a basic latch that includes input gating and a control signal
- ⊙ The latch retains its existing state when the control input is equal to 0
- ⊙ Its state may be changed when the control signal is equal to 1. In our discussion we referred to the control input as the clock
- ⊙ We consider two types of gated latches:
 - **Gated SR latch** uses the S and R inputs to set the latch to 1 or reset it to 0, respectively.
 - **Gated D latch** uses the D input to force the latch into a state that has the same logic value as the D input.

Gated S/R Latch

  


(c) Timing diagram

 

(d) Graphical symbol


Gated D Latch

 


(a) Circuit

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

 

(c) Graphical symbol

 

(d) Timing diagram

Setup and Hold Times

● Setup Time t_{su}

The minimum time that the input signal must be stable prior to the edge of the clock signal.

● Hold Time t_h

The minimum time that the input signal must be stable after the edge of the clock signal.