


Flip-Flops

Flip-Flops


- ⦿ A **flip-flop** is a storage element based on the gated latch principle
- ⦿ It can have its output state changed only on the edge of the controlling clocksignal
- ⦿ We consider two types:

- **Edge-triggered flip-flop** is affected only by the input values present when the active edge of the clock occurs
- **Master-slave flip-flop** is built with two gated latches
- The master stage is active during half of the clock cycle, and the slave stage is active during the other half.
- The output value of the flip-flop changes on the edge of the clock that activates the transfer into the slave stage.


Master-Slave D Flip-Flop

 

(a) Circuit

 


(b) Timing diagram

 



(c) Graphical symbol

A Positive-Edge-Triggered D Flip-Flop

 


Graphical symbol

  Master-Slave D Flip-Flop with *Clear* and *Preset*




(a) Circuit

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

 


(b) Characteristic table (c) Graphical symbol

T Flip-Flop

 


(a) Circuit

T	Q(t+1)
0	Q(t)
1	$\bar{Q}(t)$

 

 (b) Characteristic table (c) Graphical symbol



(d) Timing diagram

Excitation Tables

Previous State -> Present State	D
0 -> 0	0
0 -> 1	1
1 -> 0	0
1 -> 1	1

Previous State -> Present State	J	K
0 -> 0	0	X
0 -> 1	1	X
1 -> 0	X	1
1 -> 1	X	0

Previous State -> Present State	S	R
0 -> 0	0	X
0 -> 1	1	0
1 -> 0	0	1
1 -> 1	X	0

Previous State -> Present State	T
0 -> 0	0
0 -> 1	1
1 -> 0	1
1 -> 1	0