

## Protection of Thyristors.

For satisfactory and reliable operation of thyristor, we need to protect it from various abnormal conditions.

A thyristor must be provided following protection, in order to obtain reliable operation.

- ① Over-current Protection.
- ② Over-voltage Protection.
- ③ High  $\frac{di}{dt}$  protection.
- ④ High  $\frac{dv}{dt}$  protection.
- ⑤ Thermal protection.
- ⑥ Gate protection.
  - ↳ (a) Over-current protection in gate
  - ↳ (b) Over-voltage protection in gate
  - ↳ (c) Protection against noise signals in gate

### ① Over-Current Protection of Thyristors.

- Over-current may be caused because of faults, short-circuits, or surge currents due to lightning strike.
- This kind of overcurrent may lead to damage of thyristors, due to the junction temperature exceeding its rated value.

- Overcurrent protection in Thyristor circuits is

achieved by use of two protective devices.

(a) Circuit Breaker

(b) Fast-acting fuses.


- The protection mechanism must isolate the faulty part of the circuit, before any damage is done to the SCR because of fault.

Use of circuit breakers :-

- Circuit breakers are used for protecting SCR's from surge current or fault current of long duration.
- Circuit breakers have longer tripping time.

Use of fast acting current-limiting fuses :-

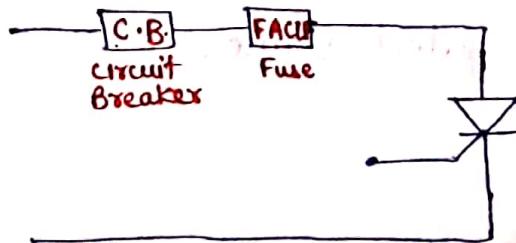- It is used for protecting SCR's from large surge currents of very short duration.
- In order that the fuse protects the thyristor reliably, the  $I^t$  rating of the fuse must be less than that of the SCR.



## ② Over-voltage Protection of Thyristors.

- Over-voltage transients are one of the main causes of failure of thyristors.
- Over-voltage may cause unwanted turn-on of a thyristor or permanent damage to the device.
- There are two reasons for over-voltages.

### (i) Internal causes for over-voltages.

↳ Over voltage generated during commutation of a thyristor.

↓  
Large  $\frac{di}{dt}$  during commutation, causes

Large transient voltage  $L \frac{di}{dt}$

↓  
Large transient voltage  $L \frac{di}{dt}$

### (ii) External causes of over-voltages.

① Due to interruption of current in an inductive circuit.

② Due to lightning strike on feeder lines

③ Due to energizing or de-energizing of primary of transformer connected in the circuit.

- Over-voltage protection of thyristors is achieved by use of.

(a) Voltage Snubber Circuit or RC circuits.

(b) Voltage Clamping devices or Non-linear resistors.

- Use of snubber circuit or RC circuits.

- Voltage snubber circuit or RC circuit is connected across the device to be protected

- Snubber circuit provides two protection  $\rightarrow$  Over-voltage protection

$$\frac{dv}{dt}$$

- Snubber circuit provides a local path for reverse recovery current, thus reducing internal over-voltages.

- Use of voltage-clamping device or Non-linear resistors.

- A voltage-clamping device is a non-linear resistor. It is also known as Varistor.

- For a non-linear resistor, resistance value decreases with increasing voltage.

- So, a non-linear resistor or varistor is connected across SCR to protect it from over-voltage.

## Under normal condition


→ Voltage is within limits  $\Rightarrow$  So, resistance is high  
 So, it only allows very small current.

## When over-voltage occurs

→ when surge voltage appears  $\Rightarrow$  the device resistance decreases  
 To start to store heat and then it almost creates a short-circuit path across SCR. Thus only a small voltage appears across SCR.

- Eg. ~~that~~ Selenium thyrector diodes, Metal-oxide varistors  $\rightarrow$  Used for over-voltage protection of SCRs.

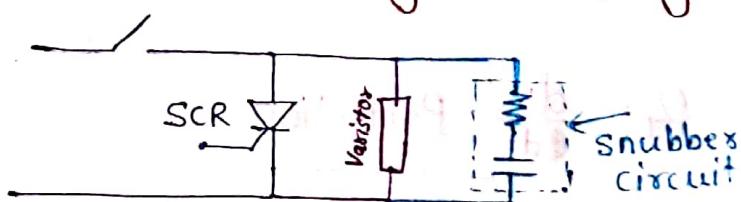
→ Generally, for protection of SCR against over-voltages, both snubber circuit as well as voltage clamping device are used.


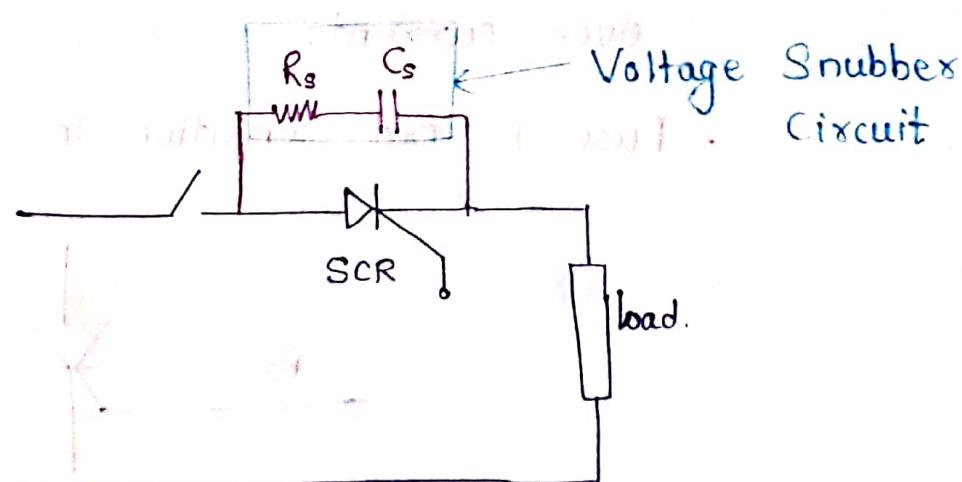
## (3) High $\frac{di}{dt}$ protection of SCRs.

- When we turn-on a thyristor, the anode current rises from zero, to its peak value.
- Also, we know that, initially after turning on, the anode current passes through a small area near gate-cathode junction and slowly spreads to whole area of junction.

- Voltage across  $C_s$ , builds up slowly. So,  $\frac{dV}{dt}$  across  $C_s$  is less than the specified maximum  $\frac{dV}{dt}$  rating of the device.
  - Purpose of connecting "Rs" in the snubber circuit.
  - $C_s$  is enough to protect SCR against high  $\frac{dV}{dt}$ , then why are we connecting  $R_s$  in series with  $C_s$ .
  - $R_s$  is connected to limit the current in the circuit, due to sudden discharge of the capacitor when SCR is turned-on.
- In absence of  $R_s$ , high discharge current through SCR capacitor may destroy the SCR.




## ⑤ Thermal Protection

- Heat sinks are used to dissipate the heat produced during operation of SCRs.
- Without using heat sinks, temperature of SCRs may rise above the rated thermal limit, and may damage the SCRs.

## ⑥ Gate Protection

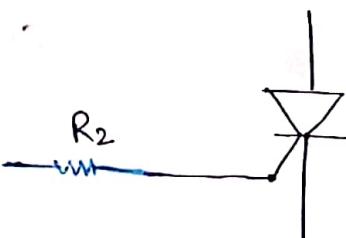
### a) Over-current protection in Gate

- Overcurrent in the gate circuit may raise junction temperature beyond specified limit, leading to its damage.
- Range of current in gate circuit is small.
- So, a resistor, connected in series with gate circuit is sufficient to limit over-current.
- Fuse is not sensitive in this case.



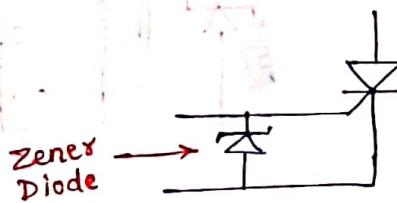
### (b) Over-voltage Protection in Gate

- over-voltage across the gate circuit can also cause false triggering of SCRs.
- Varistors are NOT used in the gate circuit to protect from over voltages as it is not sensitive to such small voltage.
- So, zener diode is used to limit voltage level in gate circuit. It is connected across gate circuit.



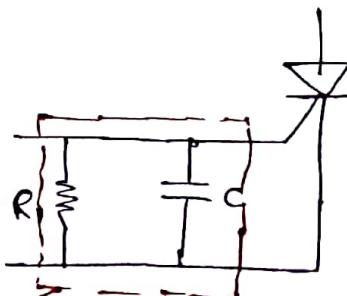
### (c) Protection against noise signals in Gate

- The noise or unwanted signals in gate circuit may lead to false triggering of the SCR.
- These noise signals must be diverted before they pass through the gate terminals.
- A parallel connected R-C circuit is connected across gate and cathode to bypass noise signals.



RC circuit to filter out noise.
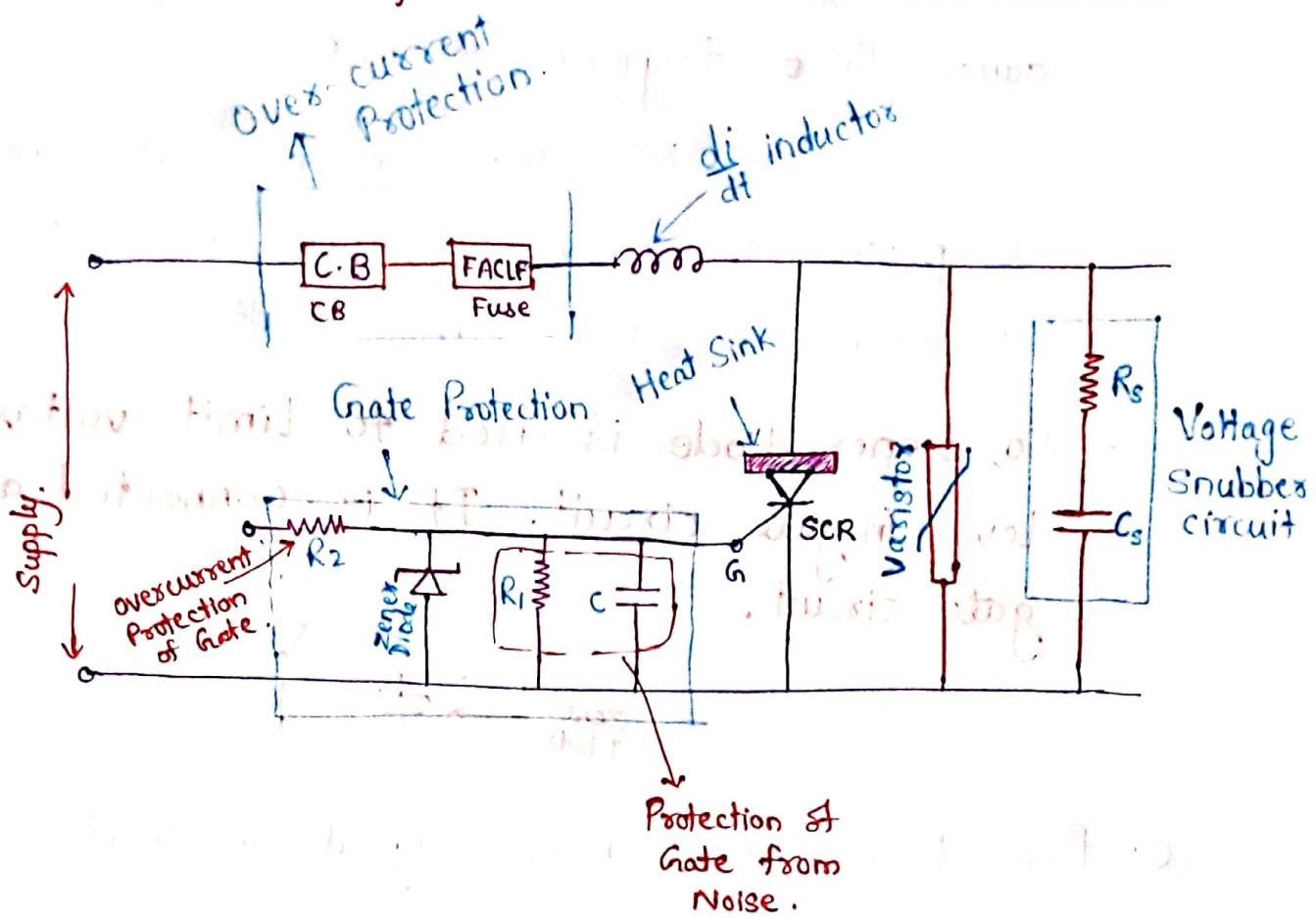
# Complete representation of SCR protection scheme



Forward step, in change between no load or on load  
will be appropriate value of load current  
and it's feedback of forward change or on load  
step, will happen along with primary load  
current increase

between di forward D.C. between falling A.  
during series circuit of shottcker bias step + over