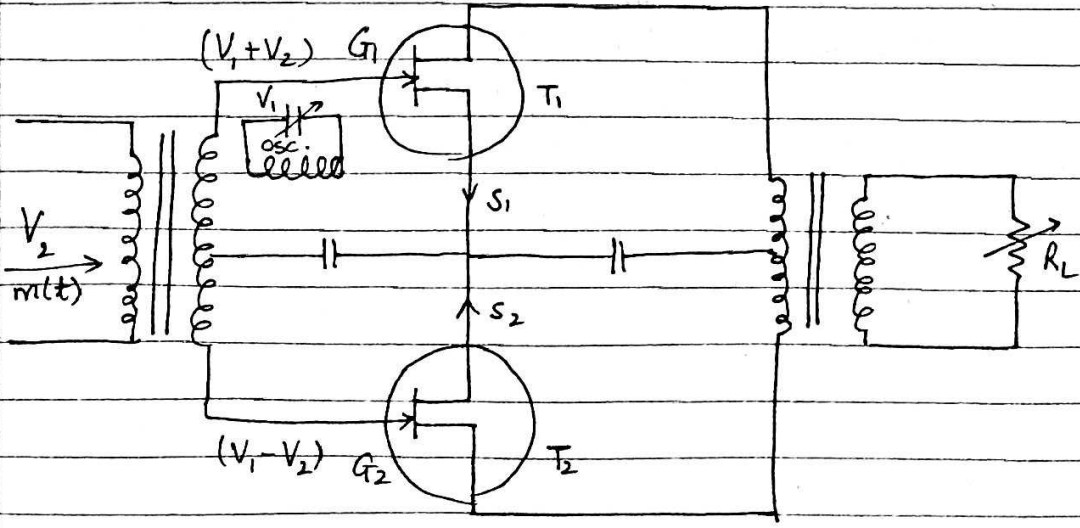


Product modulators

1. Balanced modulator circuit
2. Ring modulator circuit

Balanced modulator



$$V_2 = V_m \sin \omega_m t = m(t)$$

$$V_1 = V_c \sin \omega_c t = c(t)$$

For non linear devices:  $i = a + bv + cv^2$  : current characteristics

$$i_{d1} = a + b(V_1 + V_2) + c(V_1 + V_2)^2$$

$$i_{d2} = a + b(V_1 - V_2) + c(V_1 - V_2)^2$$


Current at centre tapped position:

$$\begin{aligned} \Delta i &= i_{d1} - i_{d2} \\ &= a + b(V_1 + V_2) + c(V_1 + V_2)^2 - a - b(V_1 - V_2) - c(V_1 - V_2)^2 \\ &= a + bV_1 + bV_2 + cV_1^2 + cV_2^2 + 2cV_1V_2 - a - bV_1 + bV_2 - cV_1^2 + cV_2^2 + 2cV_1V_2 \\ &= 2bV_2 + 4cV_1V_2 \end{aligned}$$

$$\Delta i = 2bV_m \sin \omega_m t + 4cV_c \sin \omega_m t V_m \sin \omega_c t$$

Ex 1.  $V_1(t) = 10 \cos(2000\pi t) + 4 \sin(200\pi t)$

$$V_2(t) = V_1(t) + 0.1 V_1^2(t)$$

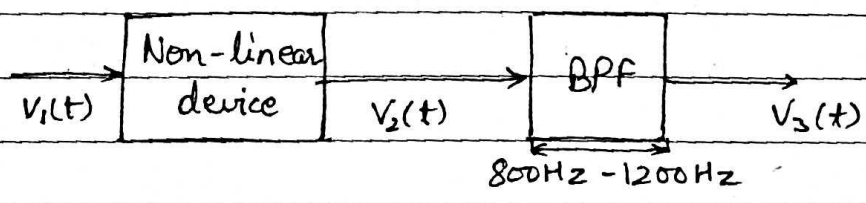

$$V_2(t) = 10 \cos(2000\pi t) + 4 \sin(200\pi t) + 0.1 (10 \cos(2000\pi t) + 4 \sin(200\pi t))^2$$

$$= 10 \cos(2000\pi t) + 4 \sin(200\pi t) + 0.1 (100 \cos^2(2000\pi t) + 16 \sin^2(200\pi t) + 80 \cos(2000\pi t) \sin(200\pi t))$$

$$V_2(t) = 10 \cos(2000\pi t) + 4 \sin(2000\pi t) + 0.1 \left( \frac{\cos(4000\pi t) + 1}{2} \right) + (1 - \cos(4000\pi t)) \frac{16}{2} + \frac{80}{2} (\sin(2200\pi t) - \sin(1800\pi t))$$

$$V_2(t) = 10 \cos(2000\pi t) + 4 \sin(2000\pi t) + 0.1 (50 + 50 \cos 4000\pi t + 8 - 8 \cos 4000\pi t + 40 \sin 2200\pi t - 40 \sin 1800\pi t)$$

$$V_2(t) = 10 \cos(2000\pi t) + 4 \sin(2000\pi t) + 5 + 5 \cos 4000\pi t + 8 - 0.8 \cos 4000\pi t + 4.0 \sin 2200\pi t - 4.0 \sin 1800\pi t$$

$$V_2(t) = 10 \cos 2\pi(1000)t + 4 \sin 2\pi(100)t + 5 + 5 \cos 2\pi(2000)t + 8 - 0.8 \cos 2\pi(200)t + 4.0 \sin 2\pi(1100)t - 4.0 \sin 2\pi(900)t$$

On passing it through the BPF :


$$V_3(t) = 10 \cos 2000\pi t + 4 \sin 2\pi(1100)t - 4 \sin 2\pi(900)t$$

$$\therefore V_3(t) = 10 \cos 2000\pi t + 4 \sin 2200\pi t - 4 \sin 1800\pi t$$

Q. An amplitude modulated waveform shown in fig. Determine: i) modulation index (m),

ii) efficiency

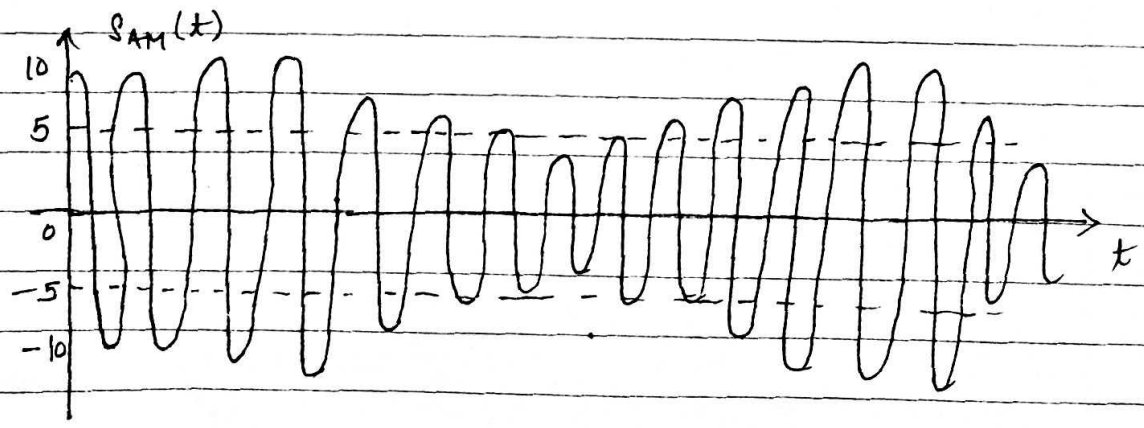iii) find out amplitude of carrier signal which must be added to attain  $m=0.1$



Soln: i) 
$$m = \frac{V_{\max} - V_{\min}}{V_{\max} + V_{\min}}$$

$$= \frac{10 - 5}{10 + 5} = \frac{5}{15} = \frac{1}{3} = 33\%$$

$$V_{\max} = V_c + V_m$$

$$= V_c + mV_c \quad \text{--- (i)}$$

$$V_{\min} = V_c - V_m$$

$$= V_c - mV_c \quad \text{--- (ii)}$$

$$V_c = \frac{V_{\max} + V_{\min}}{2} = \frac{10 + 5}{2} = 7.5V$$

$$V_c = \frac{V_{\max} - V_{\min}}{2m} = \frac{10 - 5}{2 \times \frac{1}{3}} = 7.5V$$

ii)  $m' = 0.1$

$$V_c' = \frac{V_{\max} - V_{\min}}{2m'}$$

$$= \frac{10 - 5}{2 \times 0.1} = \frac{5}{0.2}$$

$$= 25V$$

$$V_c' - V_c = 25 - 7.5 = 17.5V$$


Q. Using the message signal  $m(t) = t$ . Obtain the expression for AM wave when  $1+t^2$  the % of modulation are: i) 50%  
ii) 100%

Soln: 
$$V(t) = V_c (1 + m \sin \omega_m t) \sin \omega_c t$$



$$= V_c (1 + k_a m(t)) \sin \omega_c t$$

$$\frac{dm(t)}{dt} = 0 \quad \text{for maximum value.}$$

## Ring Modulator

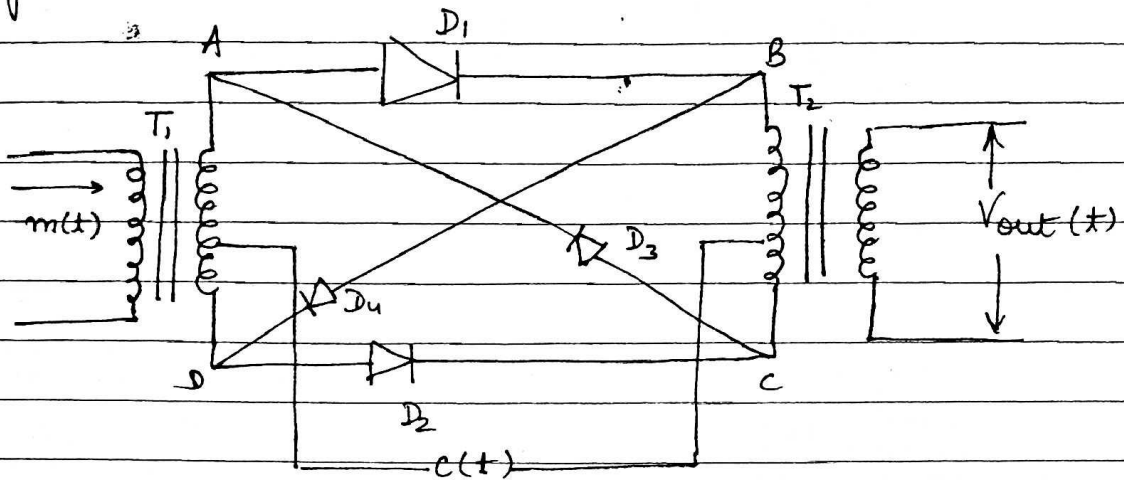

Theory - Book.

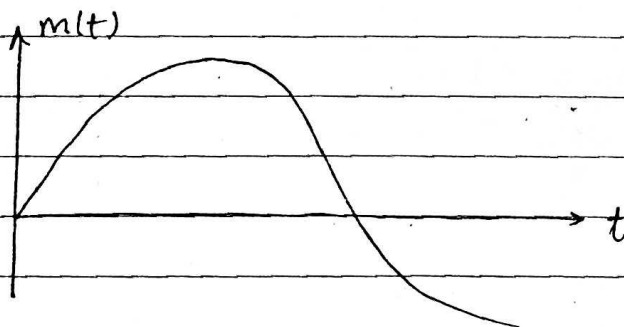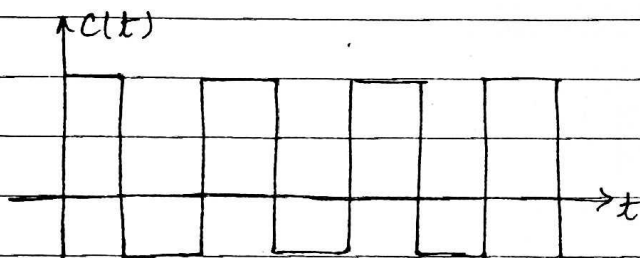

1. For +ve half cycle of  $m(t)$   
Case 1: For +ve half cycle of  $c(t)$

$$D_1 \cdot D_2 = \text{ON}$$

$$D_3 \cdot D_4 = \text{OFF}$$


- Case 2: For -ve half cycle of  $c(t)$

$$D_1 \cdot D_2 = \text{OFF}$$

$$D_3 \cdot D_4 = \text{ON}$$

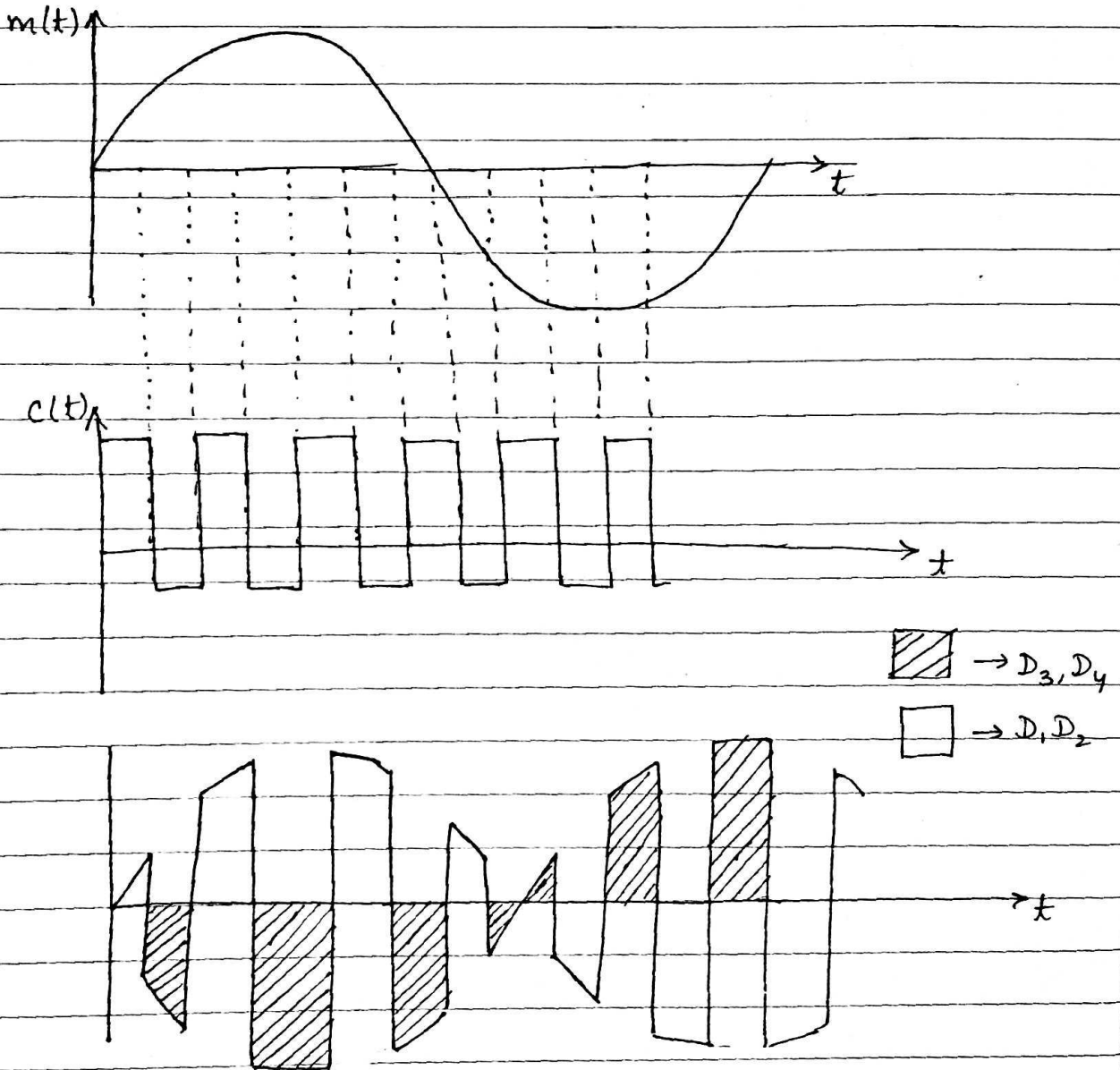2. For -ve half cycle of  $m(t)$


Voltage at  $D_1$  and  $D_2 = -ve$   
Voltage at  $D_3$  and  $D_4 = +ve$



### Demodulation of DSBSC :

- i) Coherent / synchronous demodulation
- ii) Carrier Re-insert technique.

## Coherent / Synchronous demodulation

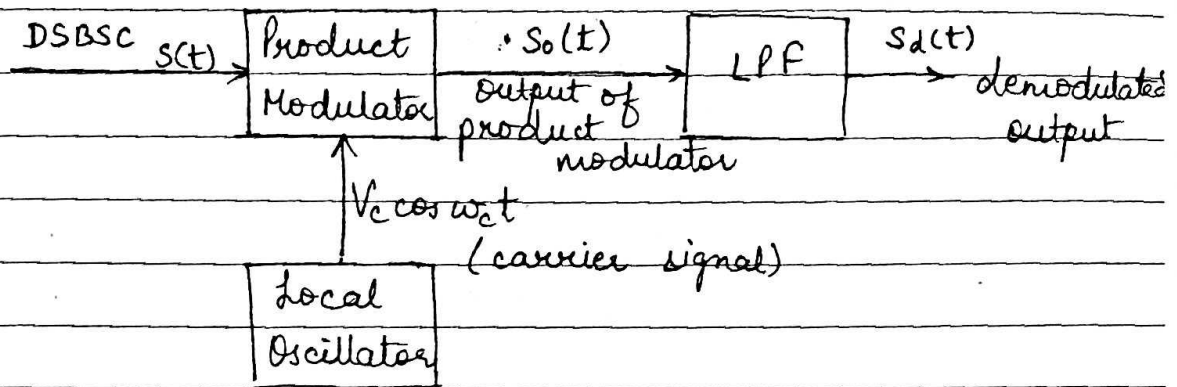

$$\text{DSBSC } s(t) = V_m \cos \omega_m t \times V_c \cos \omega_c t$$

$$\begin{aligned} S_o(t) &= S(t) \cdot V_c \cos \omega_c t \\ &= V_c \cos \omega_c t \cdot m(t) \cdot V_c \cos \omega_c t \\ &= V_c \cos \omega_c t \cdot V_m \cos \omega_m t \cdot V_c \cos \omega_c t \\ &= V_c^2 \cos^2 \omega_c t \cdot V_m \cos \omega_m t \\ &= V_c^2 V_m \left( \frac{1 + \cos 2\omega_c t}{2} \right) \cos \omega_m t \end{aligned}$$

$$S_o(t) = \frac{V_c^2 V_m \cos \omega_m t}{2} + \frac{V_c^2 V_m \cos 2\omega_c t \cdot \cos \omega_m t}{2}$$

The output of low pass filter :

$$S_d(t) = \frac{V_c^2 V_m \cos \omega_m t}{2} = \frac{V_c V_c' m(t)}{2}$$

There are 2 types of error -

- i) Phase error
- ii) Frequency error

Phase error - When the frequency of local oscillator generated by the carrier signal matches with the frequency of original oscillator and there is arbitrary phase difference between these two signals then the error is called phase error.