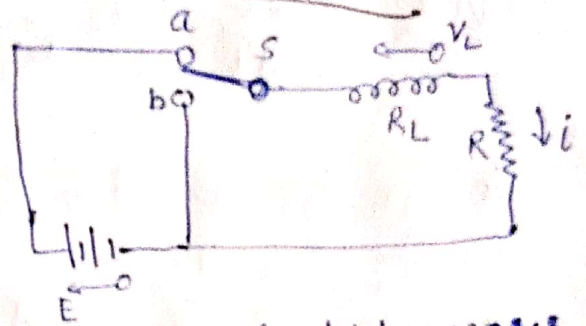


Growth of Current in an L-R (Inductance-Resistance)

Circuit \Rightarrow let us consider a circuit containing a resistance less coil of self-inductance L and a non inductive resistance R connected to battery of constant emf E through a two way switch S . when the circuit is closed (switch stuck) a self induced emf is set up in the coil which opposes



the growth of current in the circuit. Hence the current does not reach its final steady value E/R instantly, but grows at a rate depending upon the values of L and R in the circuit.

During the variable state, when the current is growing, let i be the current and di/dt the rate of growth of current at any instant t . Then the instantaneous p.d. across the resistance R is

$$V_R = iR$$

and p.d. across the inductance L is, $V_L = -L \frac{di}{dt}$

Since V_L is opposite to E , the net p.d. that appears across the resistance is $E - L \left(\frac{di}{dt}\right)$. This by ohm's law, must equal to

$$iR. \text{ Hence } E - L \frac{di}{dt} = iR \text{ or } E - iR = L \frac{di}{dt}$$

$$\text{or } dt = \frac{L di}{E - iR}. \text{ Integrating, we get}$$

$$t = -\frac{L}{R} \log_e (E - iR) + C$$

Here C is integration constant - Now at $t = 0, i = 0 \Rightarrow$

$$C = \frac{L}{R} \log_e E$$

$$\text{then } t = -\frac{L}{R} \log_e (E - iR) + \frac{L}{R} \log_e E$$


$$\text{or } -\frac{R}{L} t = \log_e (E - iR) - \log_e E = \log_e \left(\frac{E - iR}{E} \right)$$

$$e^{-\frac{R}{L}t} = \frac{E - iR}{E} = 1 - \frac{iR}{E}$$

$$\frac{iR}{E} = 1 - e^{-\frac{R}{L}t}$$

$$\text{or } i = \frac{E}{R} [1 - e^{-\frac{R}{L}t}]$$

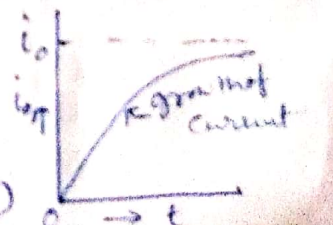But $\frac{E}{R} = i_0 \Rightarrow$ final steady value of current $i = i_0 (1 - e^{-\frac{R}{L}t})$ (1)



The rate of growth of the Current is obtained by differentiating eqn (1),

$$\frac{di}{dt} = i_0 \frac{R}{L} e^{-(R/L)t} = i_0 \frac{R}{L} \left(1 - \frac{i}{i_0}\right) \quad \text{Since } i_0$$

$$= \frac{R}{L} (i_0 - i).$$

So greater the ratio, $\frac{R}{L}$ or smaller ratio $\frac{L}{R}$, the more rapidly does the Current approach its maximum value. The ratio $\frac{L}{R}$ is called the 'Inductive time constant' (τ_L) of

the circuit and expressed in second

of L and R in henry and ohm respectively. Putting $t = \tau_L = \frac{L}{R}$ in eqn (1) we get

$$i = i_0 (1 - e^{-1}) = i_0 \frac{e-1}{e} = i_0 \frac{2.718-1}{2.718} = 0.632 i_0 \quad (\because e=2.718)$$

So the inductive time constant of an L-R circuit is the time in which the Current grows from zero to 0.632 of its steady value.

Decay of Current in L-R circuit.

When the switch S is thrown over to b , the battery is cut off, the L-R circuit is again closed and the Current in the circuit decays. The self induced emf in the coil now opposes the decay of the Current, since now $E=0$, then equation for decay is

$$-L \frac{di}{dt} = iR \quad \text{or} \quad dt = -\frac{L}{R} \frac{di}{i} \quad (\text{Integrating}) \text{ we get}$$

$$\Rightarrow t = -\frac{L}{R} \log_e i + C \quad (\text{Here } C \text{ is integration constant})$$


Now at $t=0$, $i=i_0$ so

$$C = \frac{L}{R} \log_e i_0. \text{ Thus}$$

$$t = -\frac{L}{R} \log_e i + \frac{L}{R} \log_e i_0$$

$$-\frac{R}{L} t = \log_e i - \log_e i_0 = \log_e \frac{i}{i_0}$$

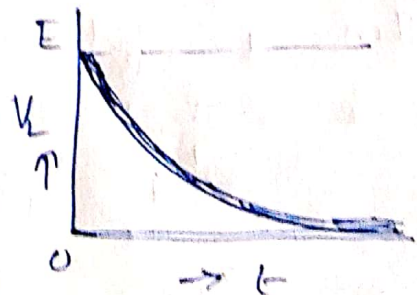
$$e^{-(R/L)t} = i/i_0 \quad \text{or} \quad \boxed{i = i_0 e^{-(R/L)t}} \quad \text{--- (2)}$$



Next to Page - 07

Unit - 03Decay of Current in L-R Circuit

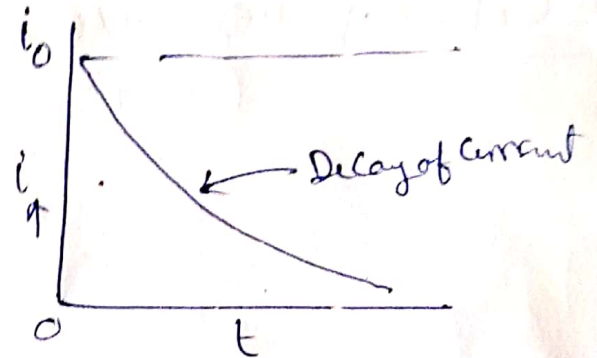eq (2) is the differential equation for the decay of current in an L-R circuit. It shows that current in L-R circuit decays exponentially, reaching zero at $t \rightarrow \infty$ (asymptotically).



The rate of decay of current is obtained by differentiating eq (2) that is

$$\begin{aligned} \frac{di}{dt} &= -i_0 \frac{R}{L} e^{-(R/L)t} = -i_0 \frac{R}{L} \frac{i}{i_0} \quad (\text{from eq 2}) \\ &= -\frac{R}{L} i. \end{aligned}$$

So it is clear that greater the ratio $\frac{R}{L}$, or smaller the inductive time constant $\frac{L}{R}$, the more rapidly does the current decay. Putting $t = \tau_L = \frac{L}{R}$ in eq (2) we get

$$i = i_0 e^{-1} = \frac{i_0}{e} = \frac{i_0}{2.718} = 0.36 i_0$$

So the inductive time constant of an L-R circuit may also be defined as the time in which the current decays from maximum to 0.368 of the maximum value.