

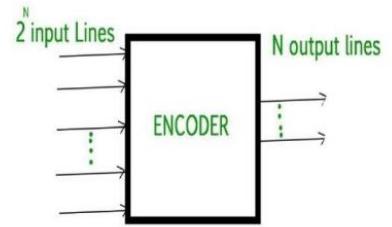


Encoder

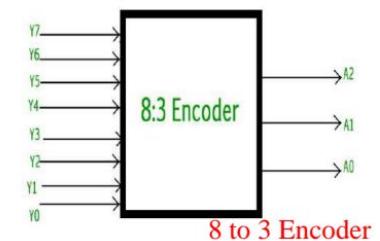- ▶ An Encoder is a combinational circuit that performs the reverse operation of Decoder.
- ▶ It has maximum of **2^N input lines** and '**N**' output lines, hence it encodes the information from 2^N inputs into an N-bit code.
- ▶ It will produce a binary code equivalent to the input.




- ▶ The 4 to 2 Encoder consists of **four inputs Y₃, Y₂, Y₁, Y₀** and **two outputs A₁ and A₀**.
- ▶ At any time, only one of these 4 inputs can be ‘1’ in order to get the respective binary code at the output.
- ▶ The 8 to 3 Encoder or octal to Binary encoder consists of **8 inputs : Y₇ to Y₀** and **3 outputs : A₂, A₁ & A₀**.
- ▶ Each input line corresponds to each octal digit and three outputs generate corresponding binary code.

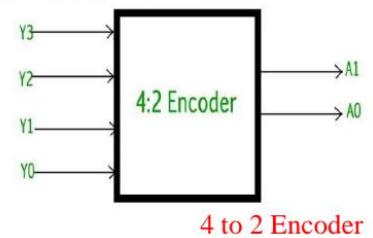

4-to-2 Binary Encoder


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

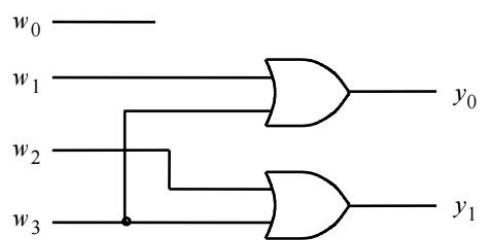

8-to-3 Binary Encoder

At any one time, only
one input line has a value of 1.

Inputs								Outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

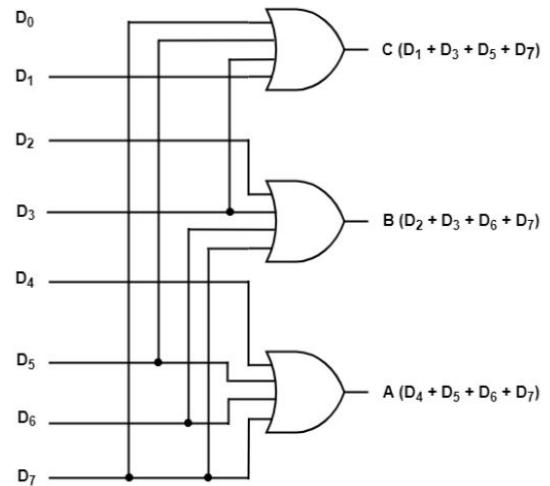

Priority Encoder

- ▶ One of the main disadvantages of standard digital encoder is that they can generate the wrong output code when there is more than one input present at logic level “1”.
- ▶ One simple way to overcome this problem is to “Prioritize” the level of each input pin.
- ▶ If there is more than one input at logic level “1” at the same time, the actual output code would only correspond to the input with the highest designated priority.
- ▶ This type of digital encoder is known as **Priority Encoder** or **P-Encoder** for short.
- ▶ The **Priority Encoder** solves the problems by allocating a priority level to each input.
- ▶ The *priority encoders* output corresponds to the currently active input which has the highest priority.
- ▶ So, when an input with a higher priority is present, all other inputs with a lower priority will be ignored.

4-to-2 Priority Encoder

Truth Table

w_3	w_2	w_1	w_0	y_1	y_0	w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	0	x	x	0	0	0	0	x	x
0	0	0	1	0	0	0	0	1	0	0	0
0	0	1	x	0	1	0	0	1	x	0	1
0	1	x	x	1	0	0	1	x	x	1	0
1	x	x	x	1	1	1	x	x	x	1	1

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	0	x	x
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1

K-Map

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	0	x	x
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1

$w_3 \backslash w_2$	00	01	11	10
$w_I \backslash w_\theta$	00	0	0	0
00	x	0	0	0
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1


$$y_1 = w_3 + w_2$$

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	0	x	x
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1


$w_3 \ w_2$	$w_I \ w_\theta$	00	01	11	10
00	x	0	1	1	1
01	0	0	0	0	0
11	1	1	1	1	1
10	1	1	1	1	1

$$y_0 = w_3 + w_1 \overline{w_2}$$

Circuit for the 4-to-2 priority encoder

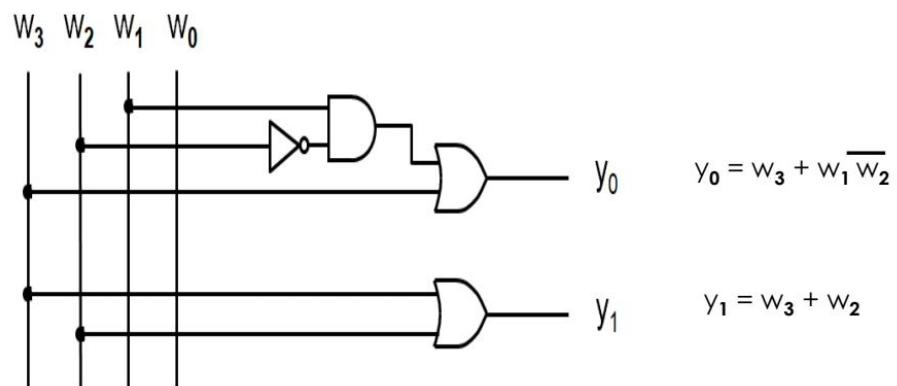

8-to-3 Priority Encoder

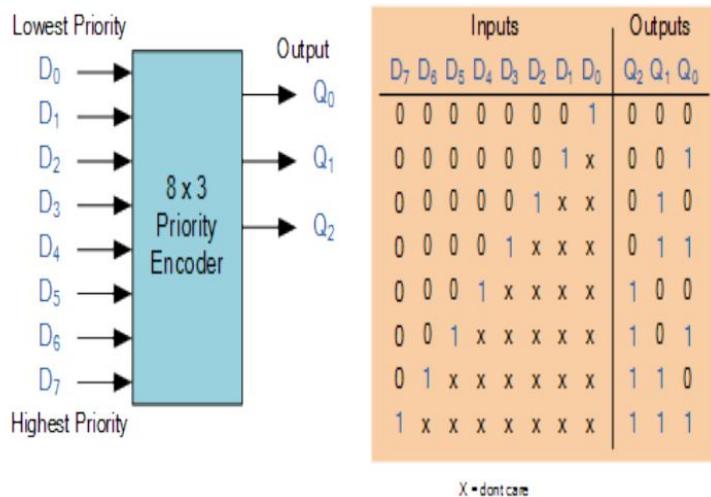

- From the truth table of the Priority Encoder, the Boolean expression with data inputs D₀ to D₇ and outputs Q₀, Q₁, Q₂ is given as:

$$Q_0 = \sum(\bar{D}_6(\bar{D}_4\bar{D}_2D_1 + \bar{D}_4D_3 + D_5) + D_7)$$

$$Q_1 = \sum(\bar{D}_5\bar{D}_4(D_2 + D_3) + D_6 + D_7)$$

$$Q_2 = \sum(D_4 + D_5 + D_6 + D_7)$$