

Enter Rita


- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR if he (Matt) already feels like going, **UNLESS** Rita decides to go.

Enter Rita

- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.


Enter Rita

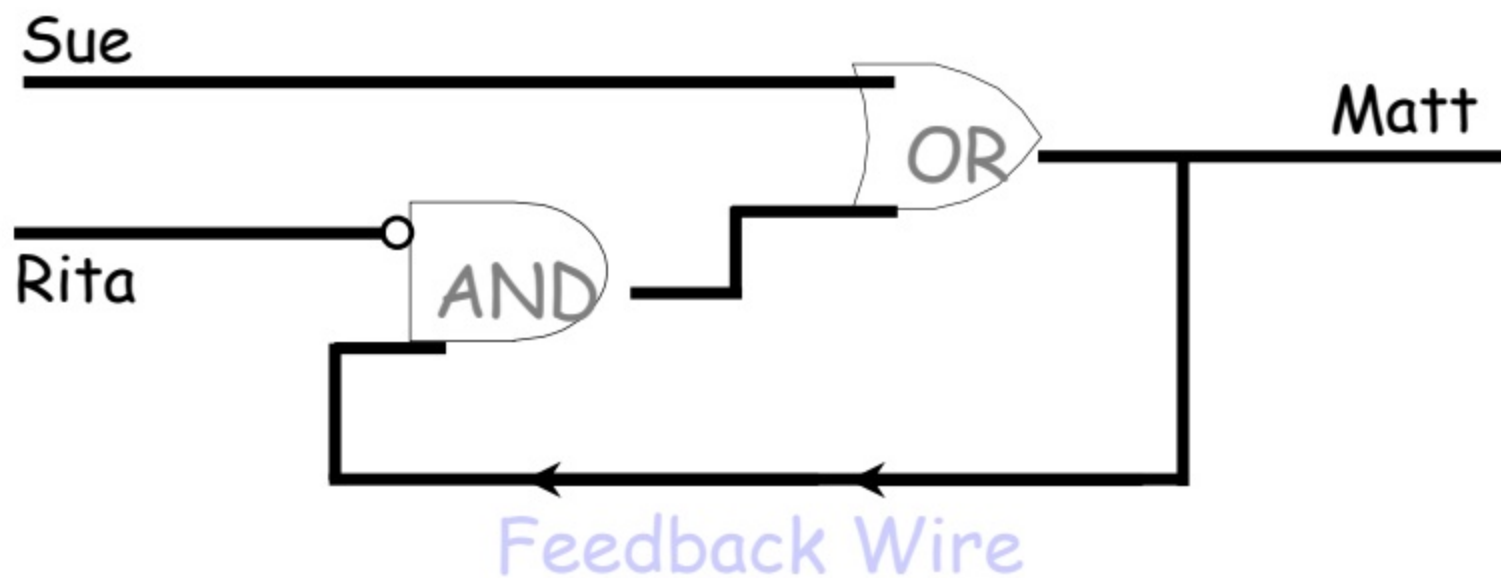- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

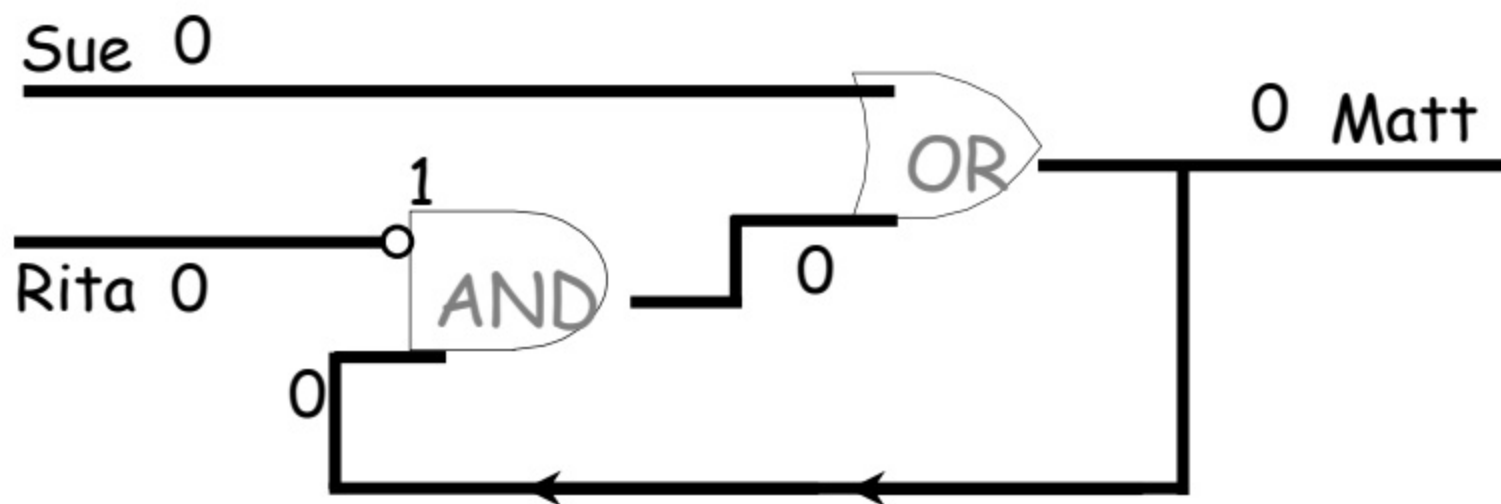- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

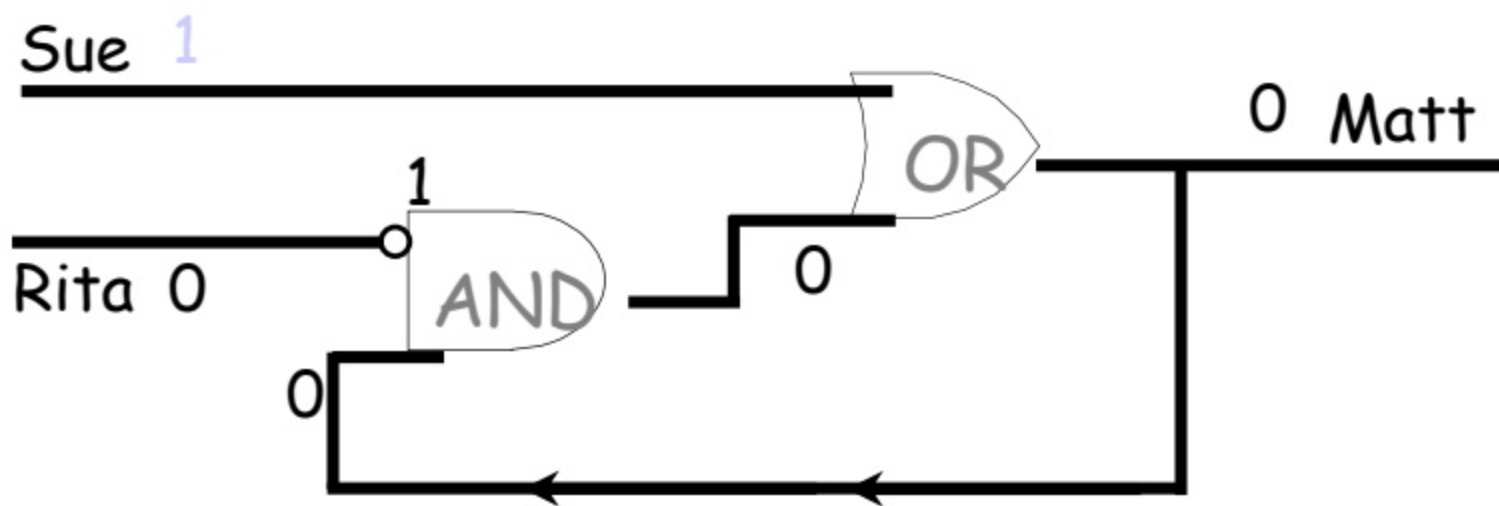- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

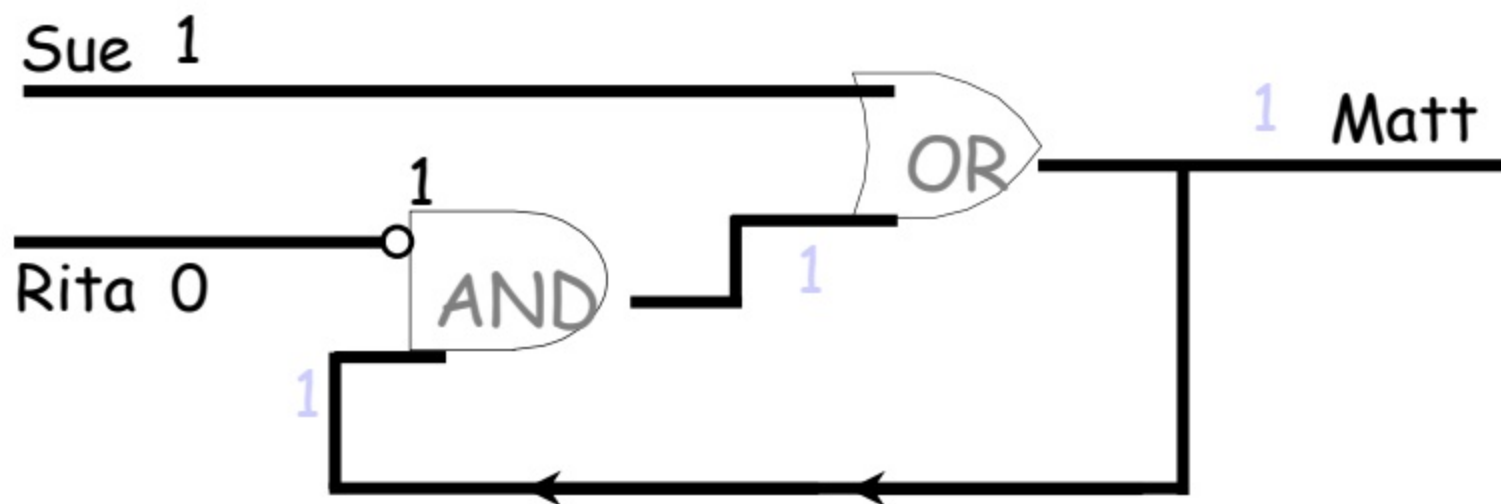- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

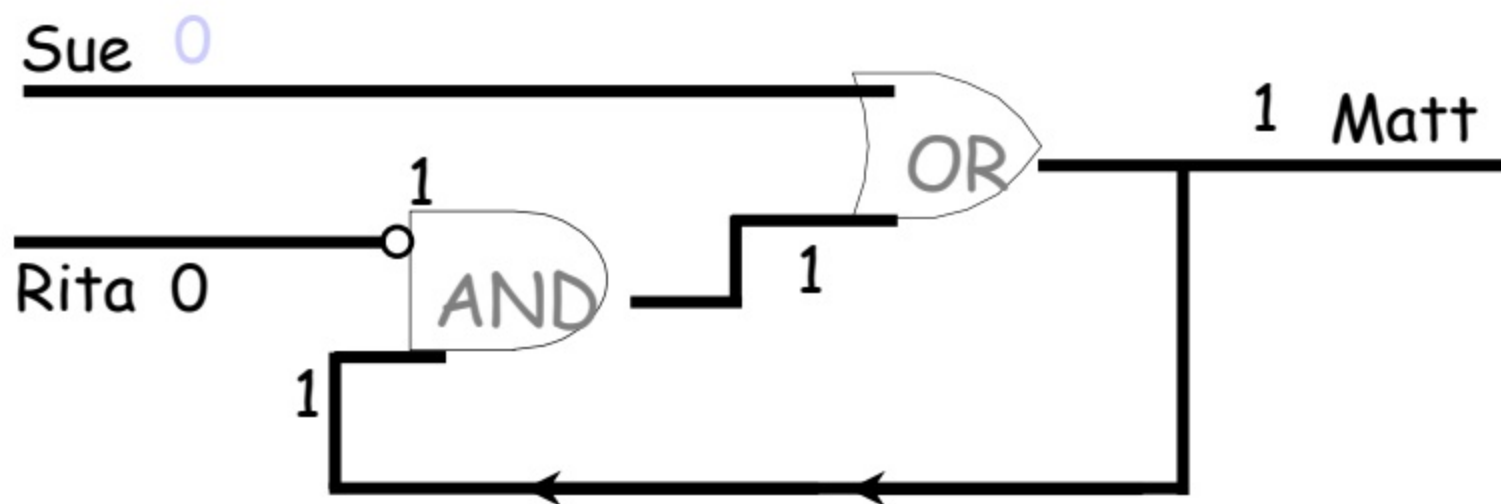- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

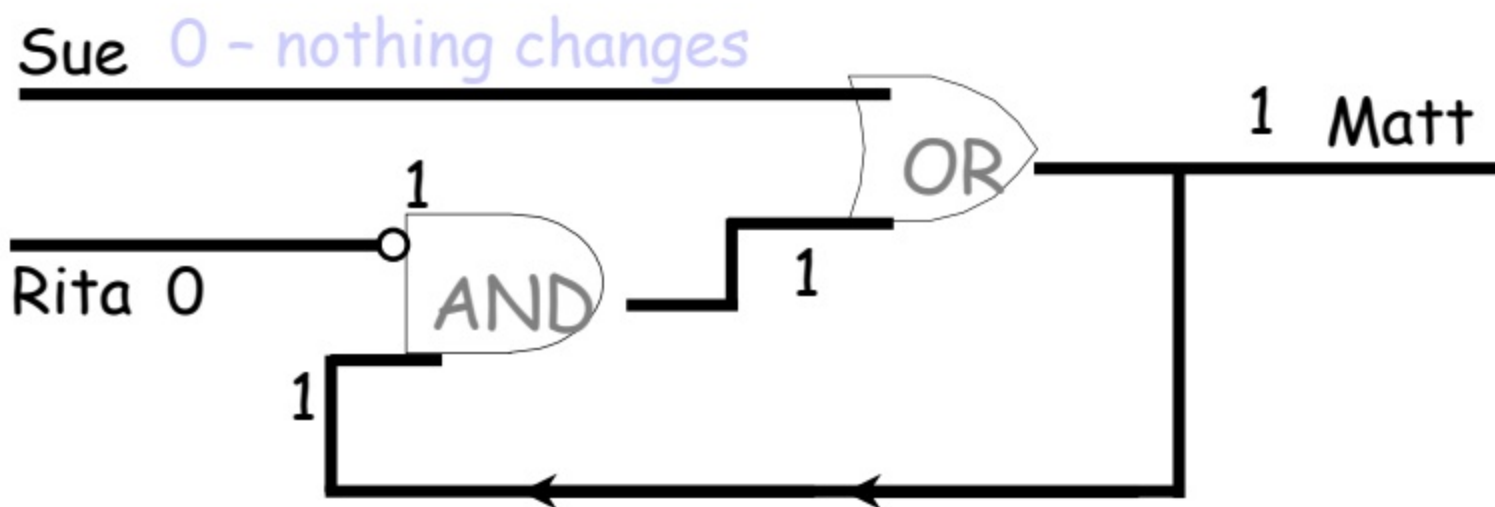- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

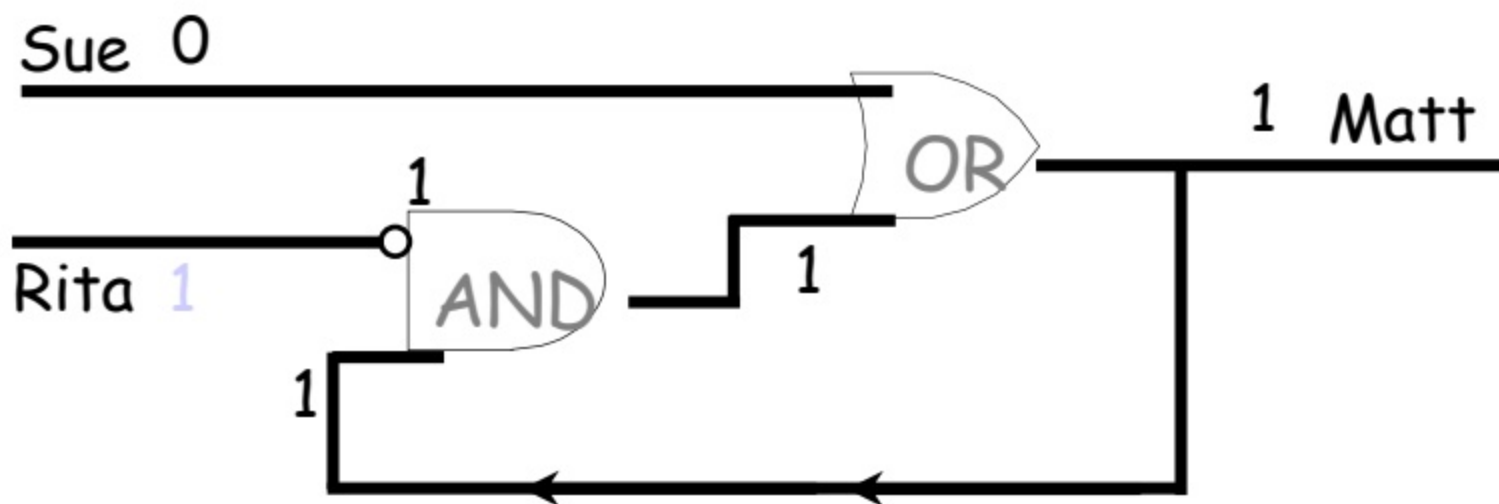- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

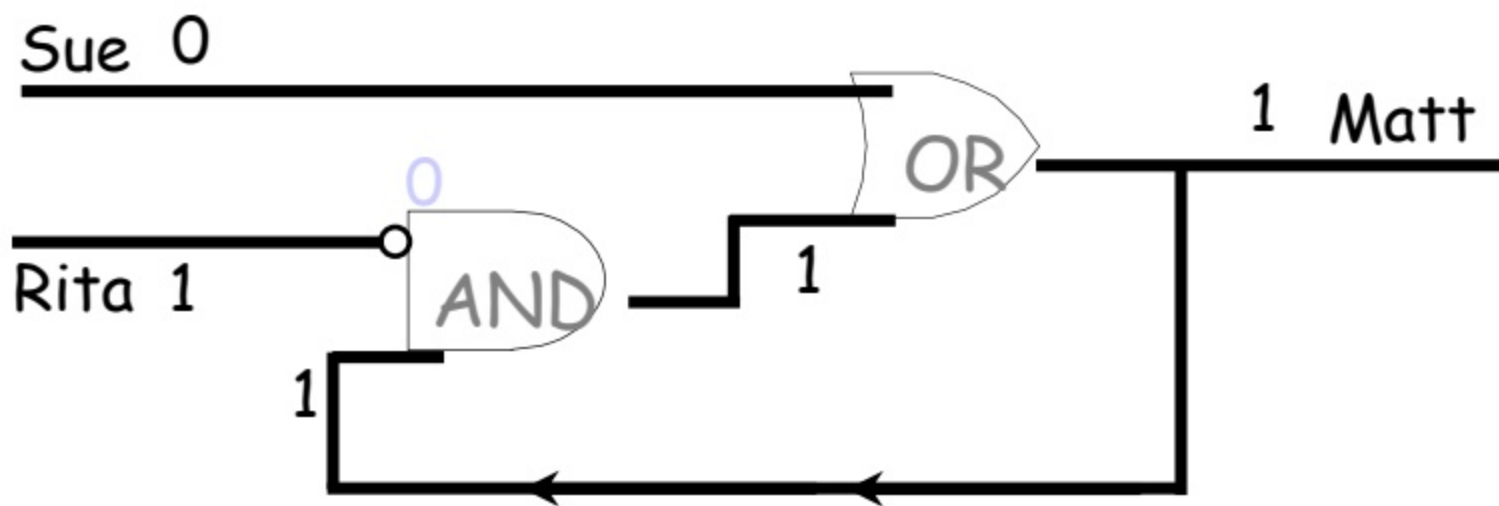- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

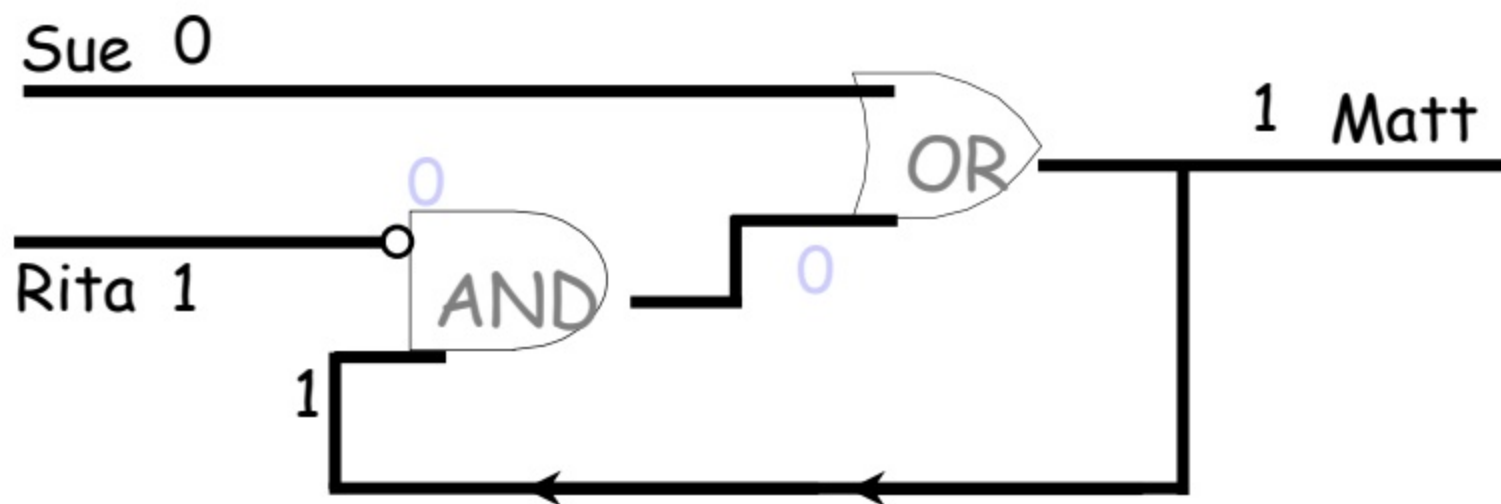- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

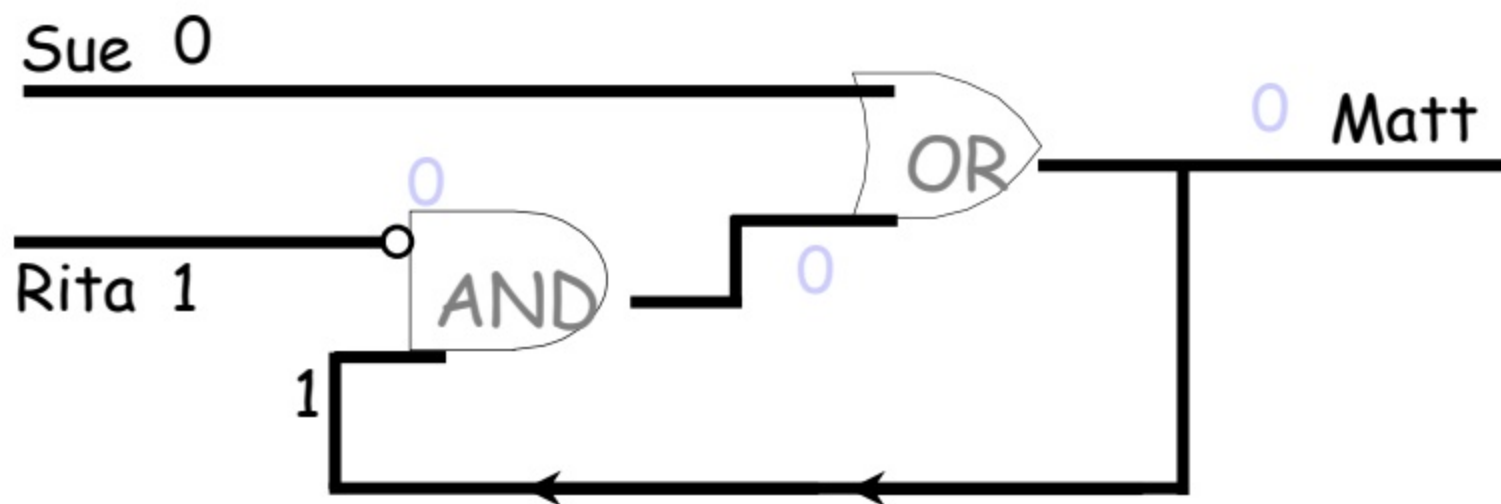- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

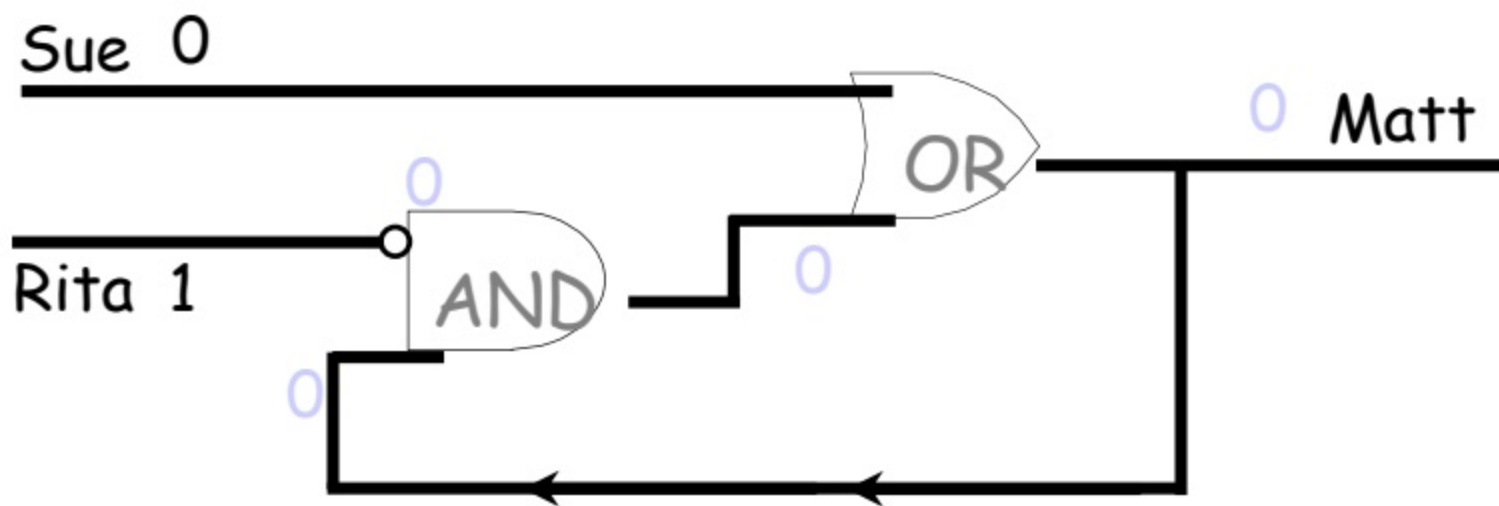- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

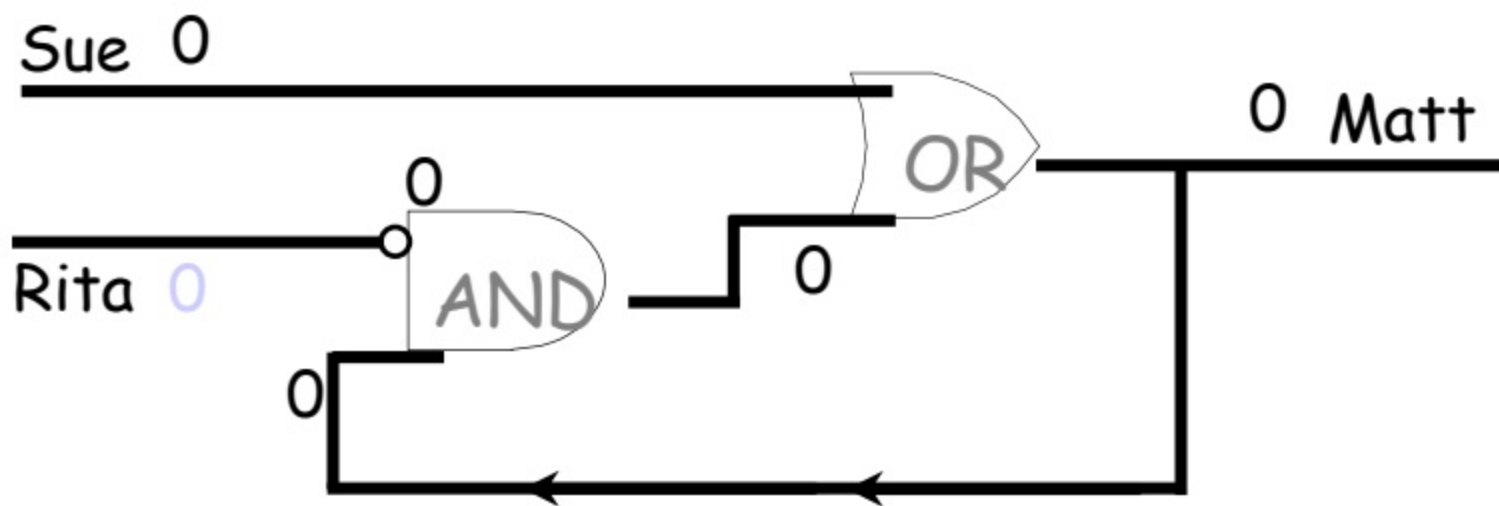- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




Enter Rita

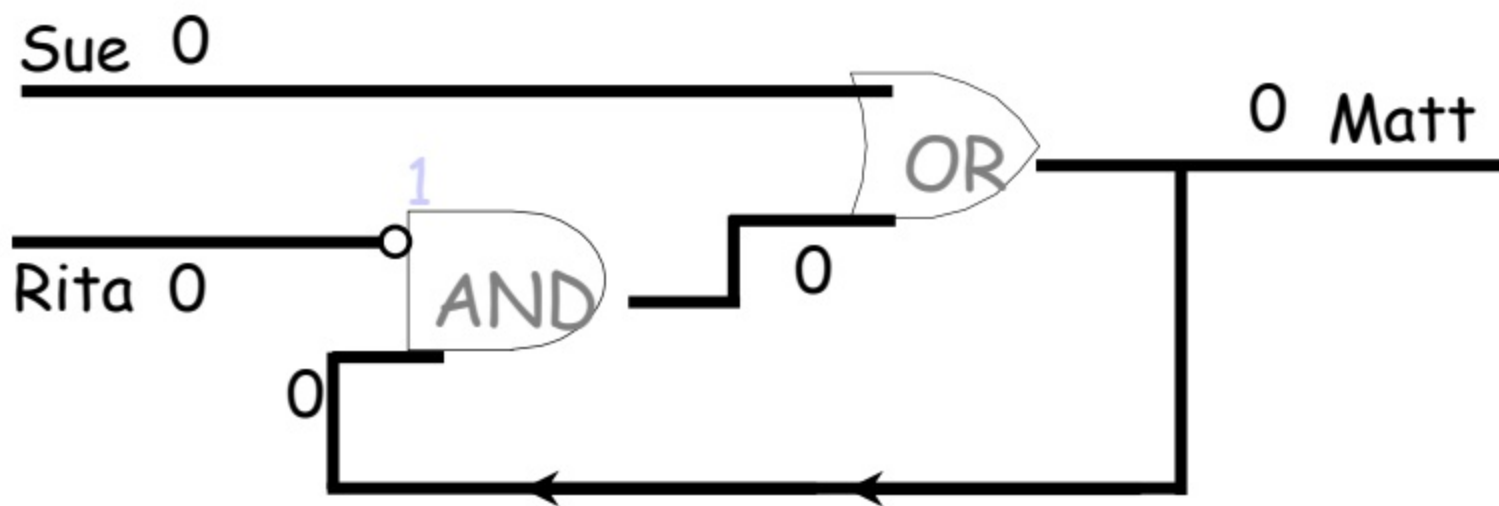- Matt doesn't like Rita
- Matt decides to go to the party if Sue decides to go OR:
 - If he (Matt) already feels like going AND Rita decides NOT to go.




The Flip-Flop

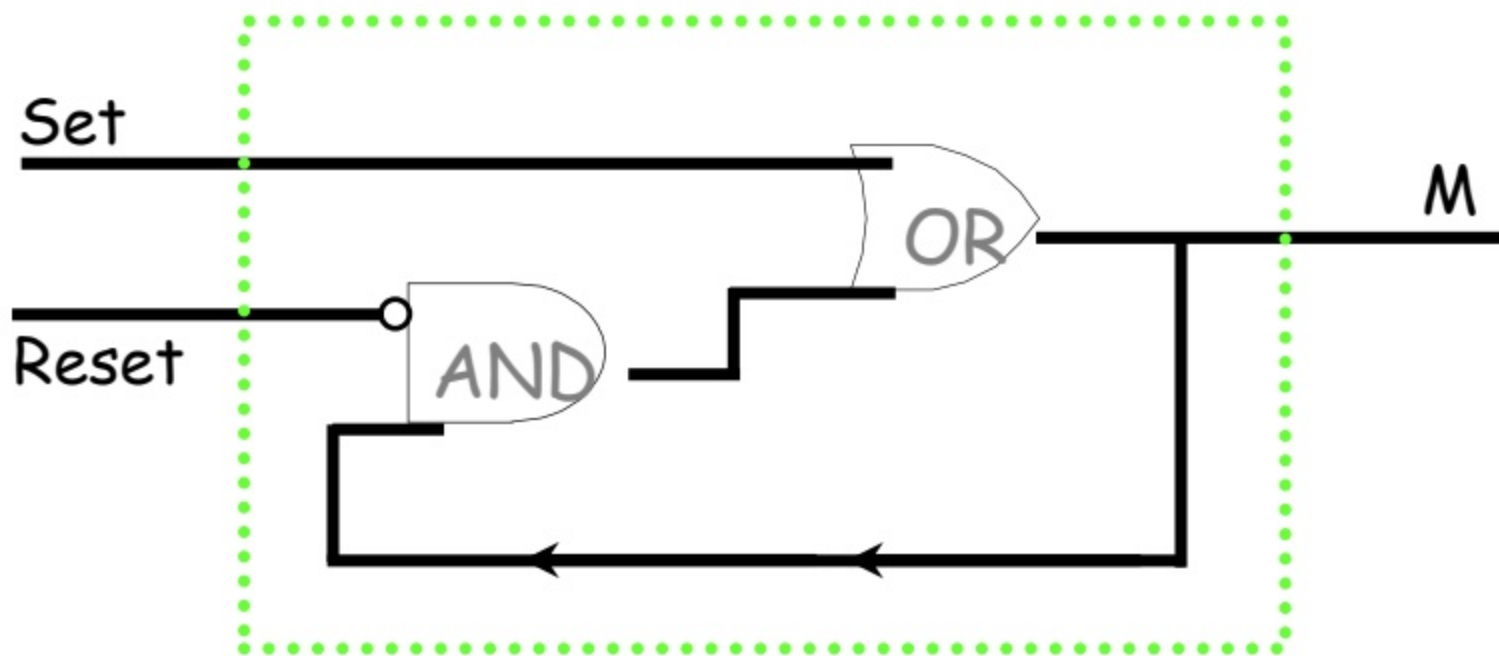


- M becomes 1 if Set is turned on
- M becomes 0 if Reset is turned on
- Otherwise (if Set and Reset are both 0), M just remembers its value

The Flip-Flop

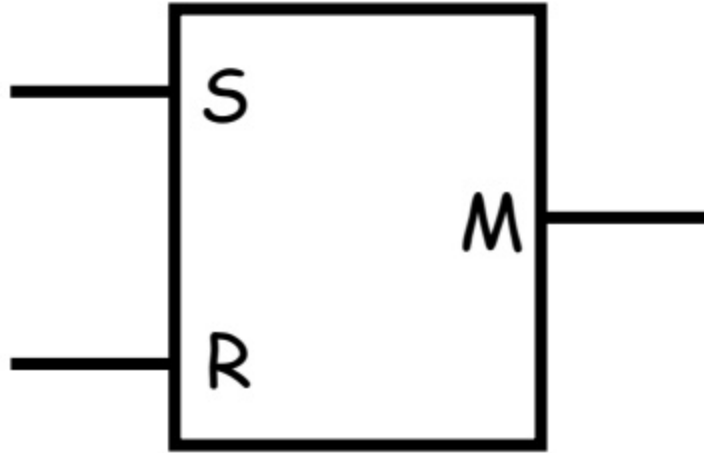


- M becomes 1 if Set is turned on
- M becomes 0 if Reset is turned on
- Otherwise (if Set and Reset are both 0), M just remembers its value

The Data Flip-Flop

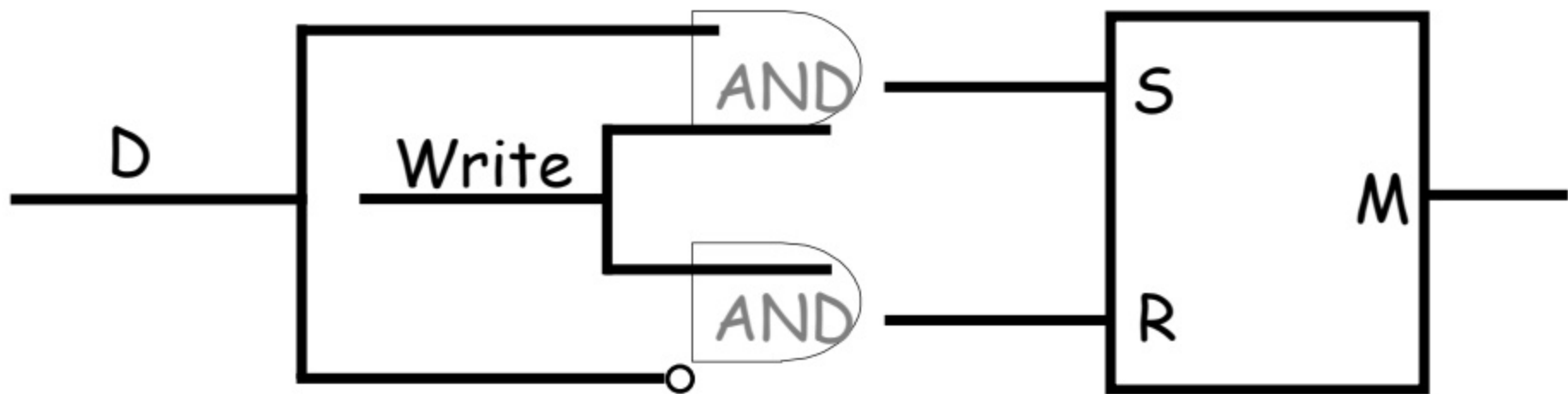


- Nothing happens unless $Write = 1$

The Data Flip-Flop

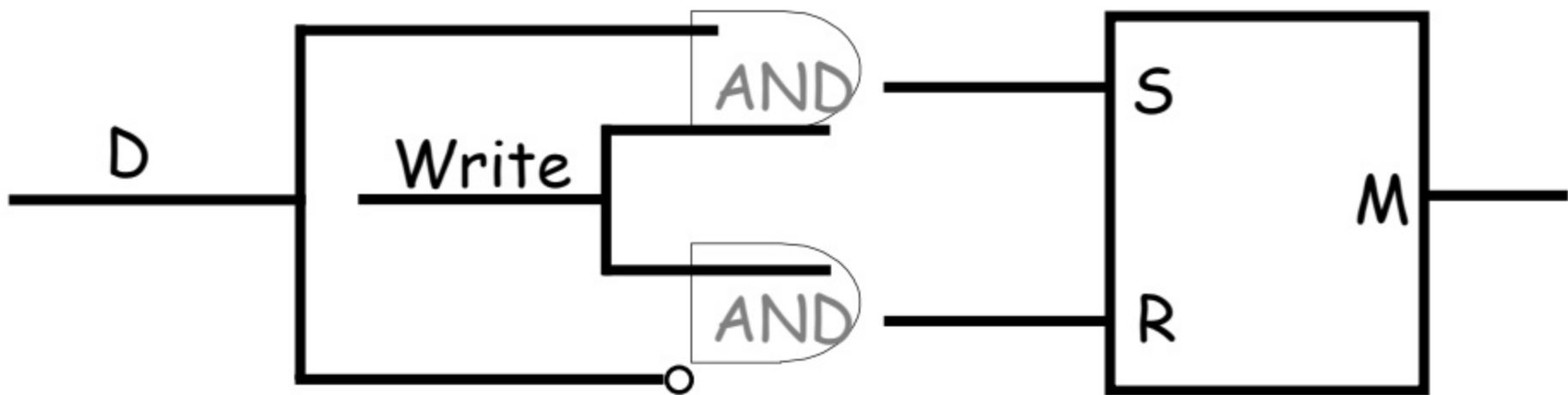


- Nothing happens unless $Write = 1$
- If $Write = 1$, then M becomes set to D
- Once $Write = 0$ again, M just keeps its value. (It ignores D .)

Using a Data Flip-Flop

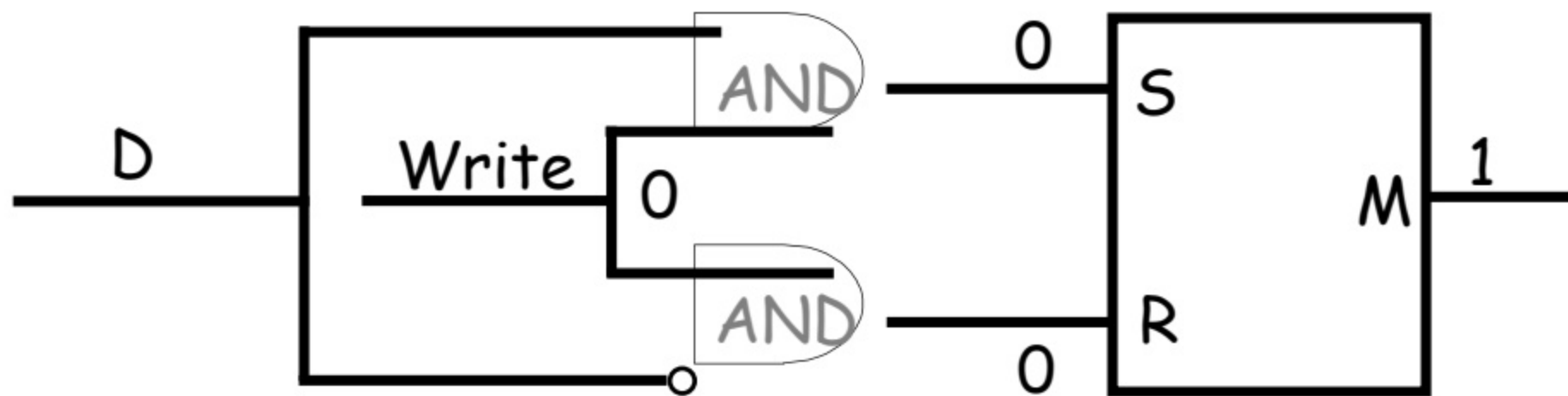


- Initially, Write = 0. Let's say M = 1.

Using a Data Flip-Flop

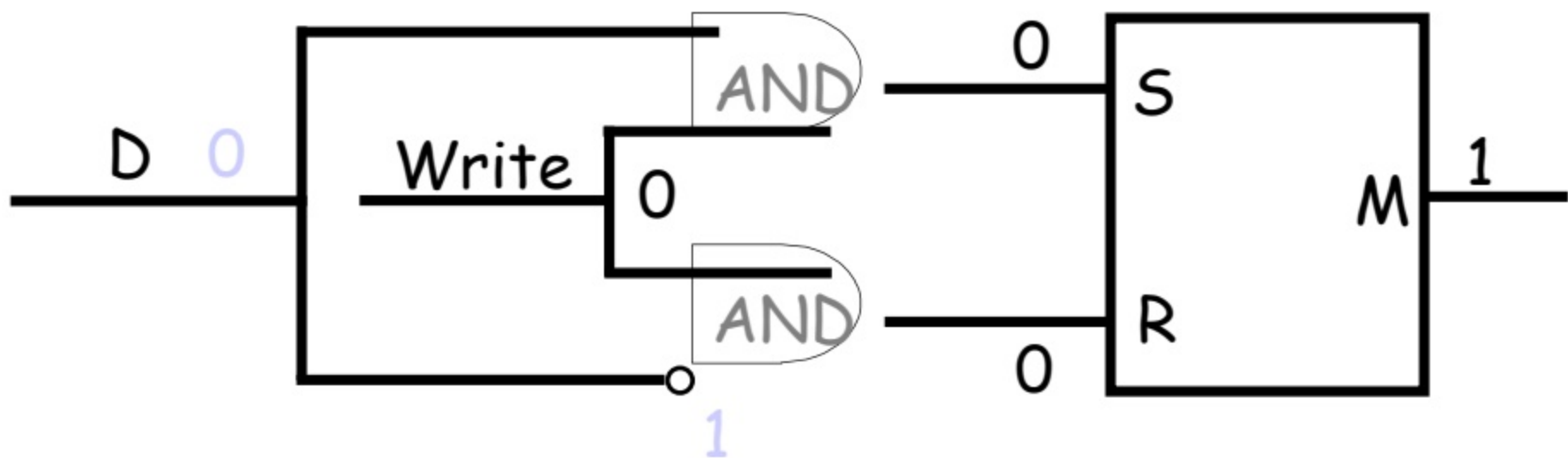


- Initially, Write = 0. Let's say M = 1.
- First, set D to desired value, say 0.

Using a Data Flip-Flop

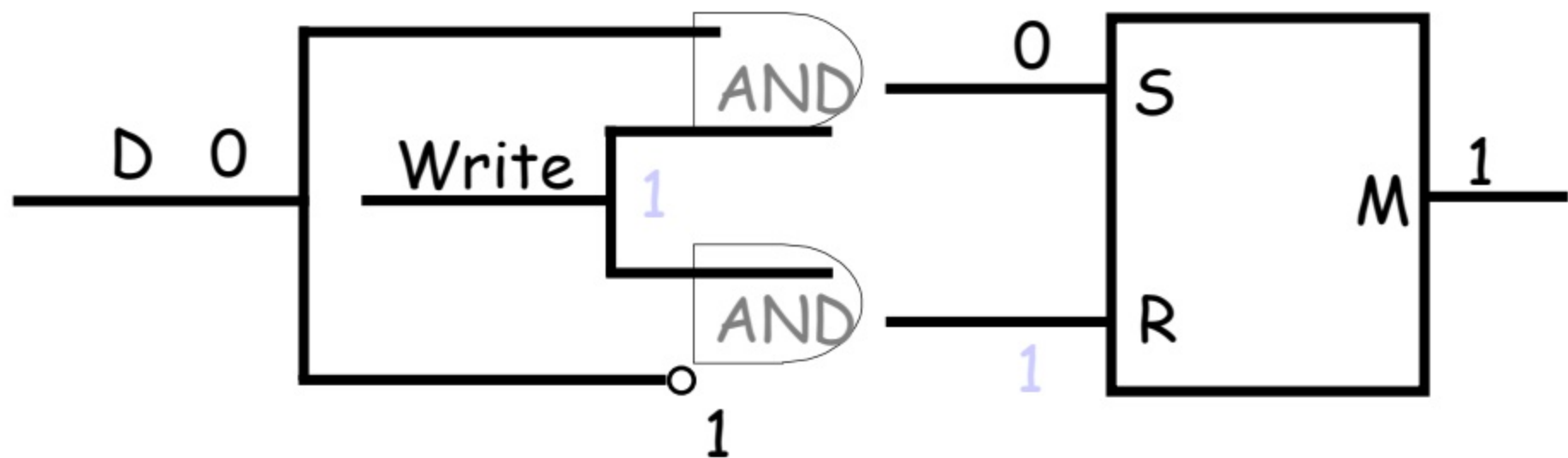


- Initially, Write = 0. Let's say M = 1.
- First, set D to desired value, say 0.
- Then, set Write to 1.

Using a Data Flip-Flop

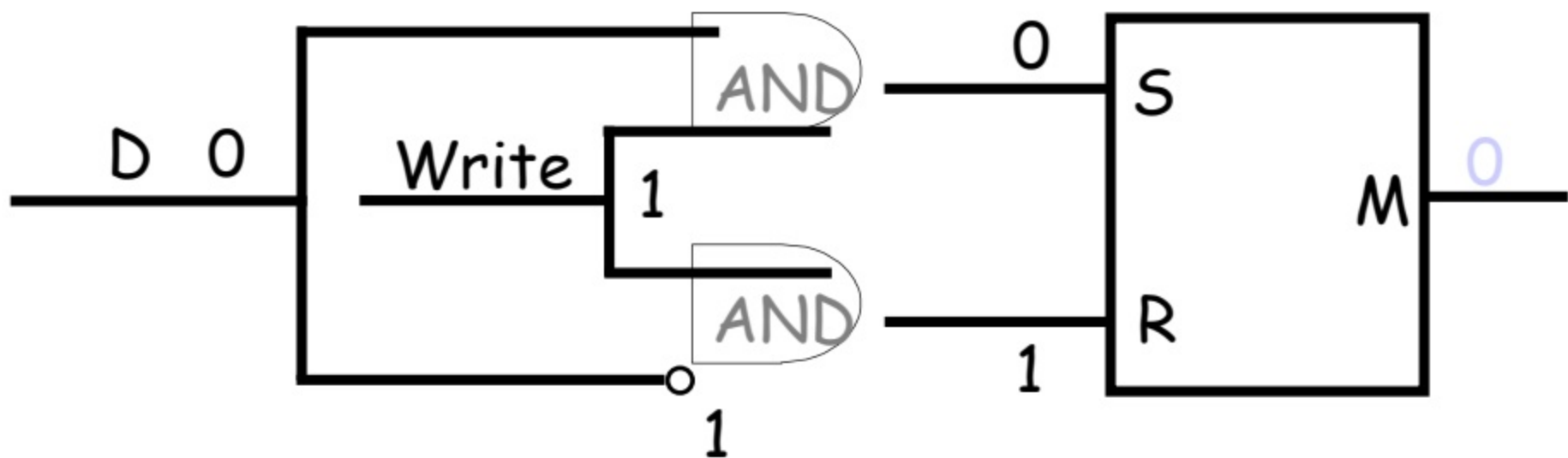


- Initially, Write = 0. Let's say M = 1.
- First, set D to desired value, say 0.
- Then, set Write to 1.
- This causes M to be reset to 0.

Using a Data Flip-Flop

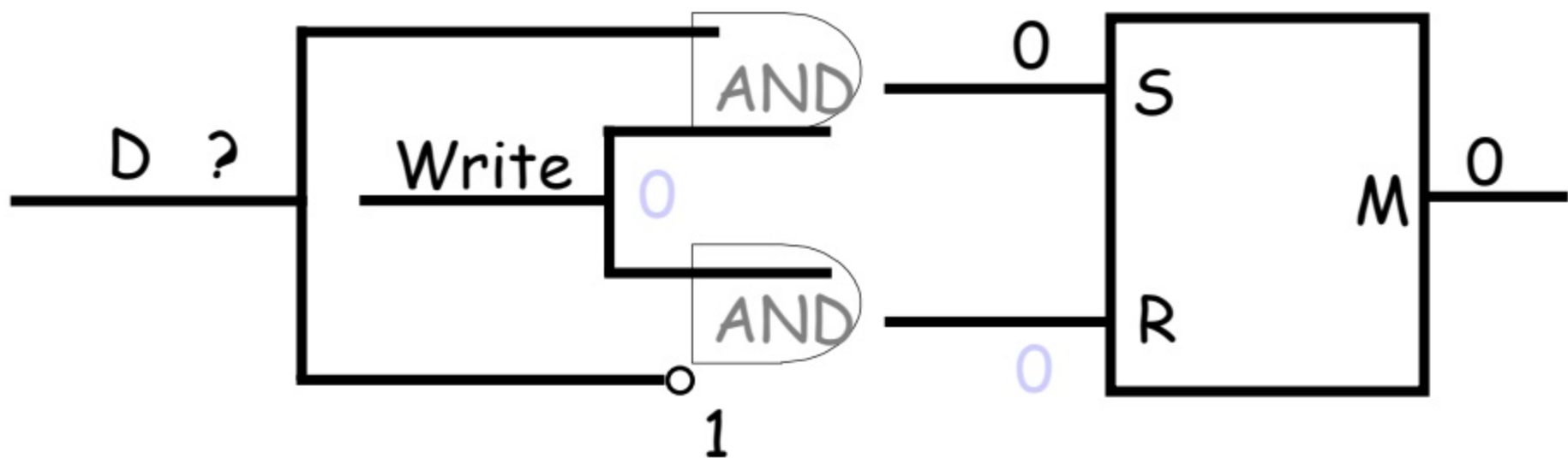


- Initially, Write = 0. Let's say M = 1.
- First, set D to desired value, say 0.
- Then, set Write to 1.
- This causes M to be reset to 0.
- Finally set Write back to 0. Now D irrelevant.

The Data Flip-Flop

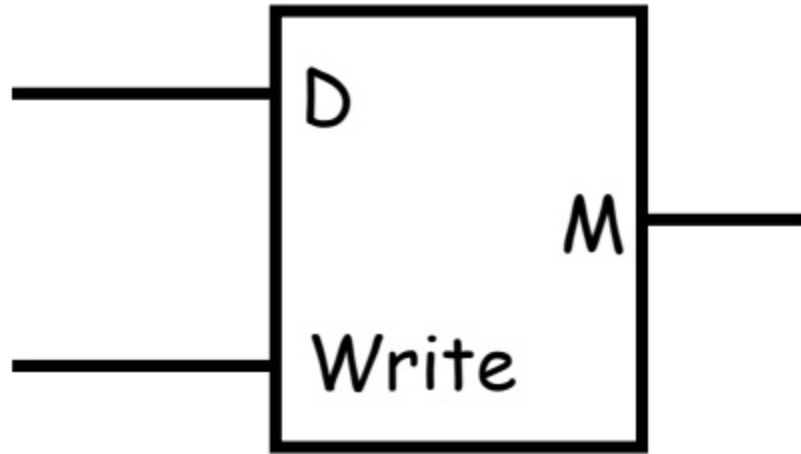


- If $Write = 0$, M just keeps its value. (It ignores D .)
- If $Write = 1$, then M becomes set to D

A subtle problem

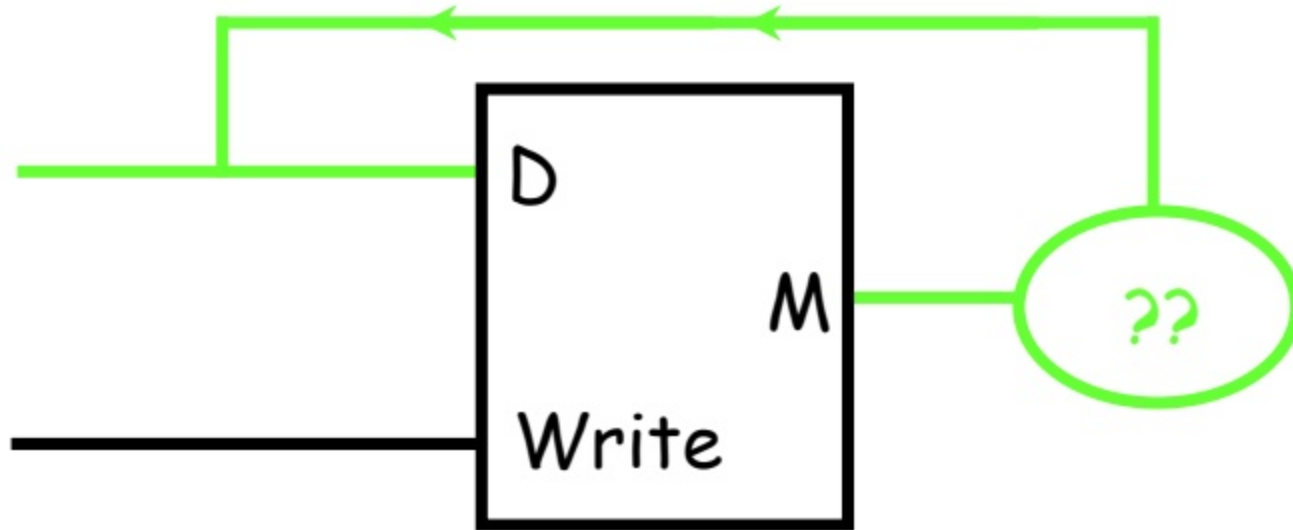


- When $Write = 1$, then $M = D$.
- If we have some feedback between M and D , then circuit could go haywire.

A subtle problem

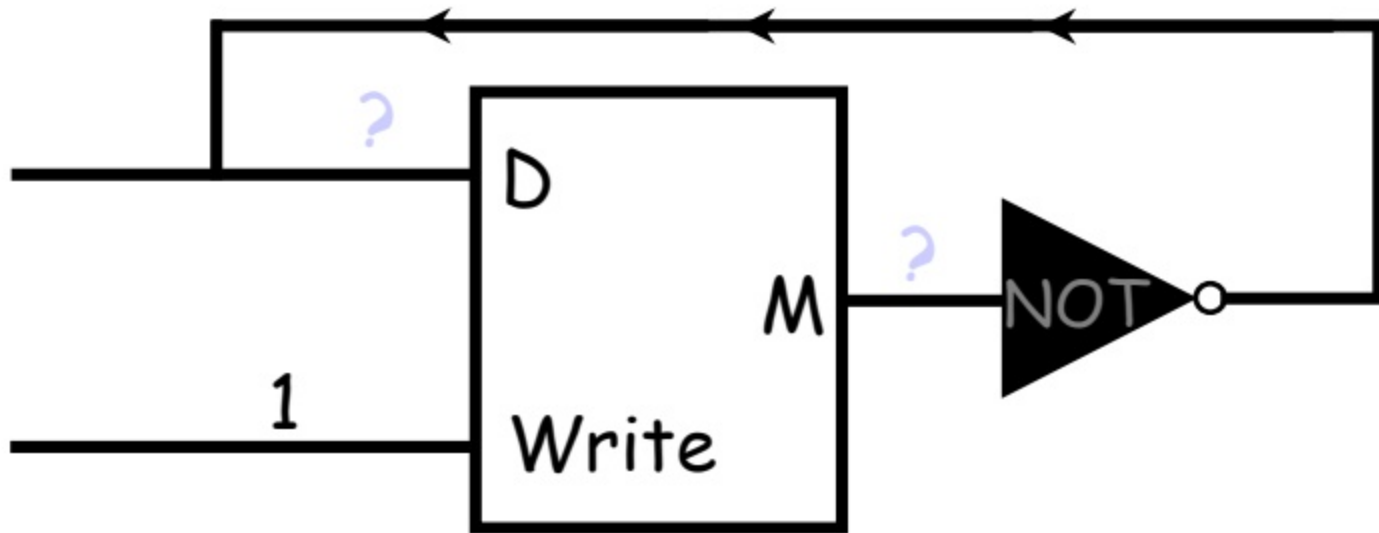


- For example, suppose NOT gate connects M and D.
- When Write = 1, M and D keep changing. We have no control.

A subtle problem

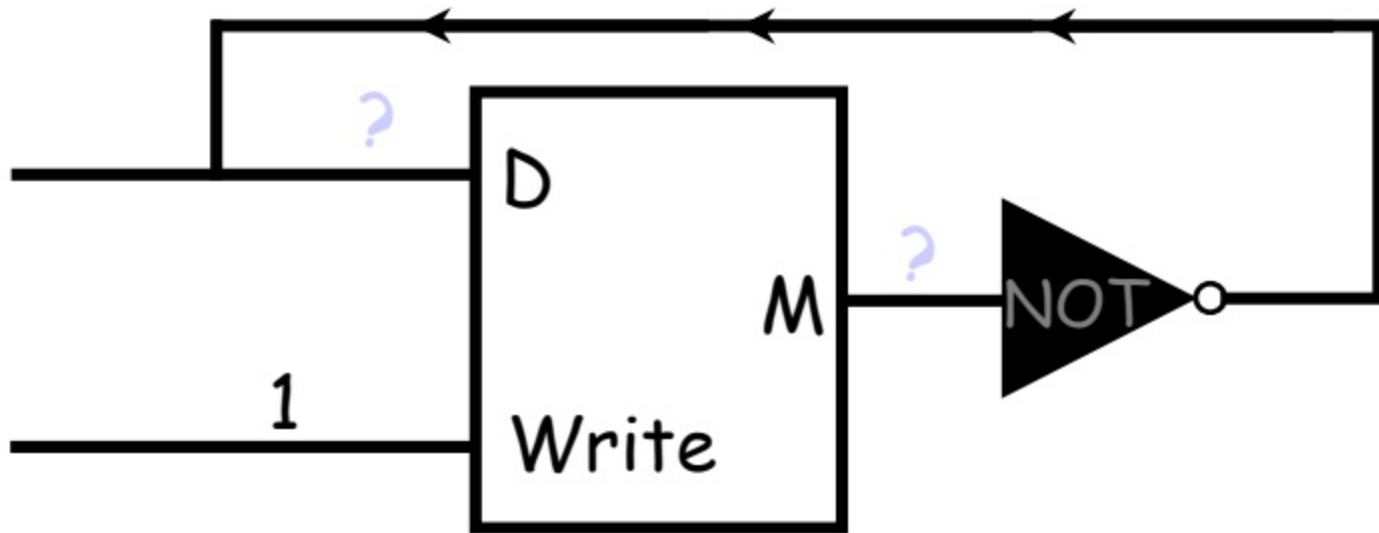


- We want to control the feedback, so that each time we set Write to 1 and then back to 0, M stores only the last value of D
- (In this case, M should invert itself **once** each time we set Write to 1 and back to 0)

"Airlock" Flip-Flop

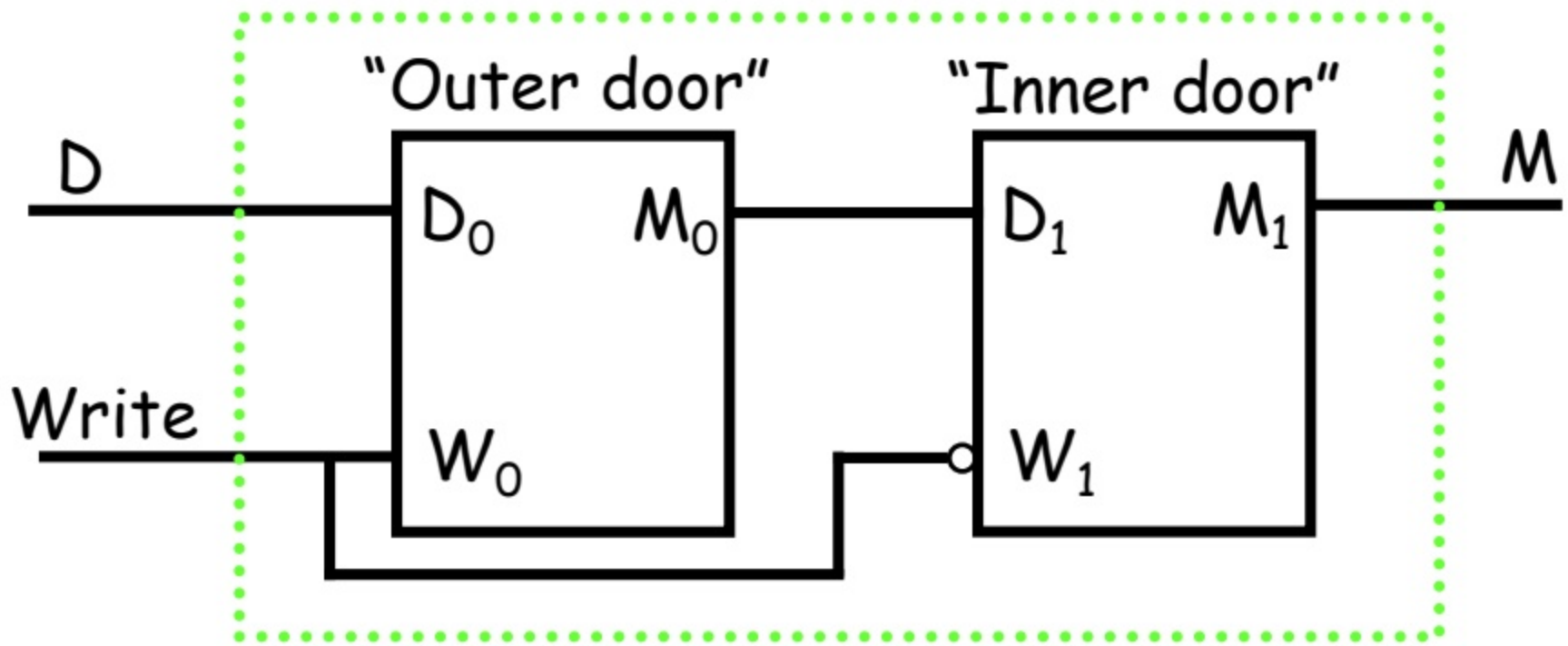


- Two-Stage System to prevent feedback loop.

"Airlock" Flip-Flop

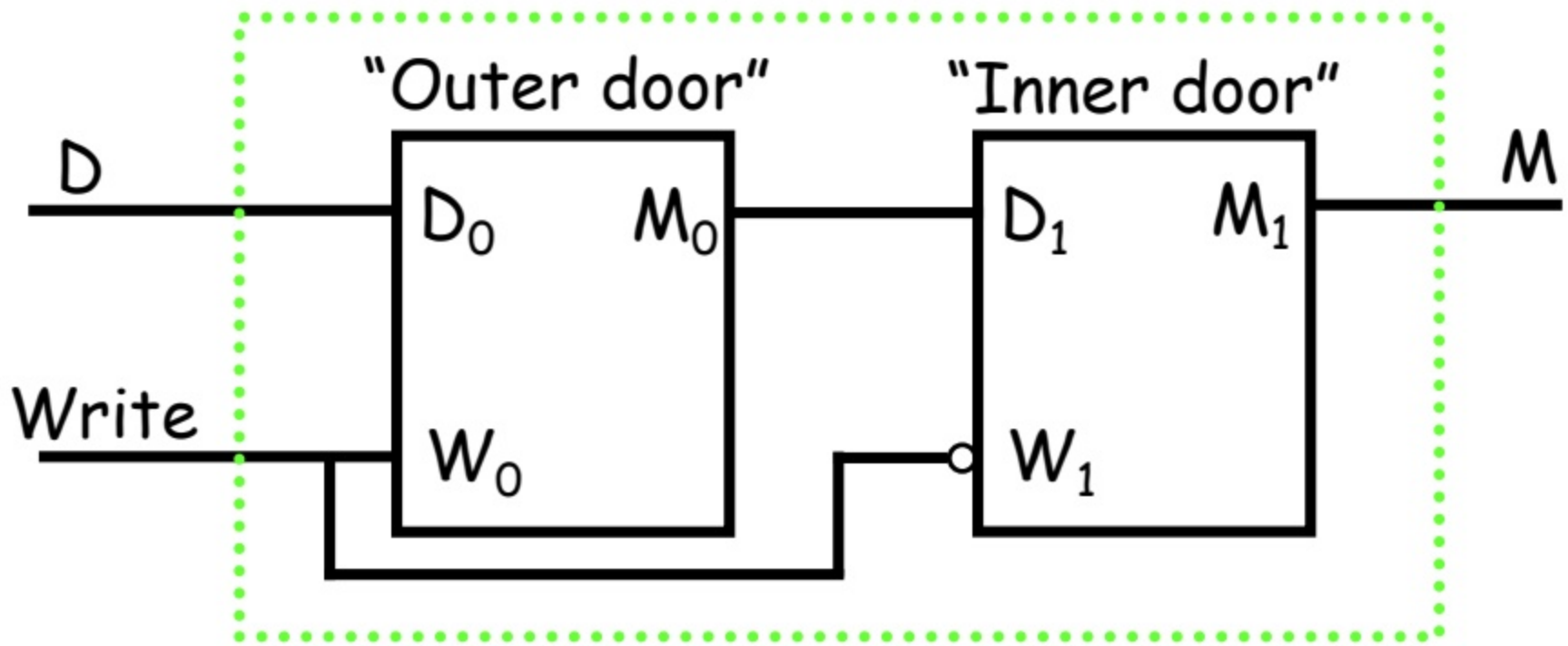


- We start with $W_{write} = 0$.
- Let's say D is always NOT M .
Start with $D = 0, M = 1$.

"Airlock" Flip-Flop

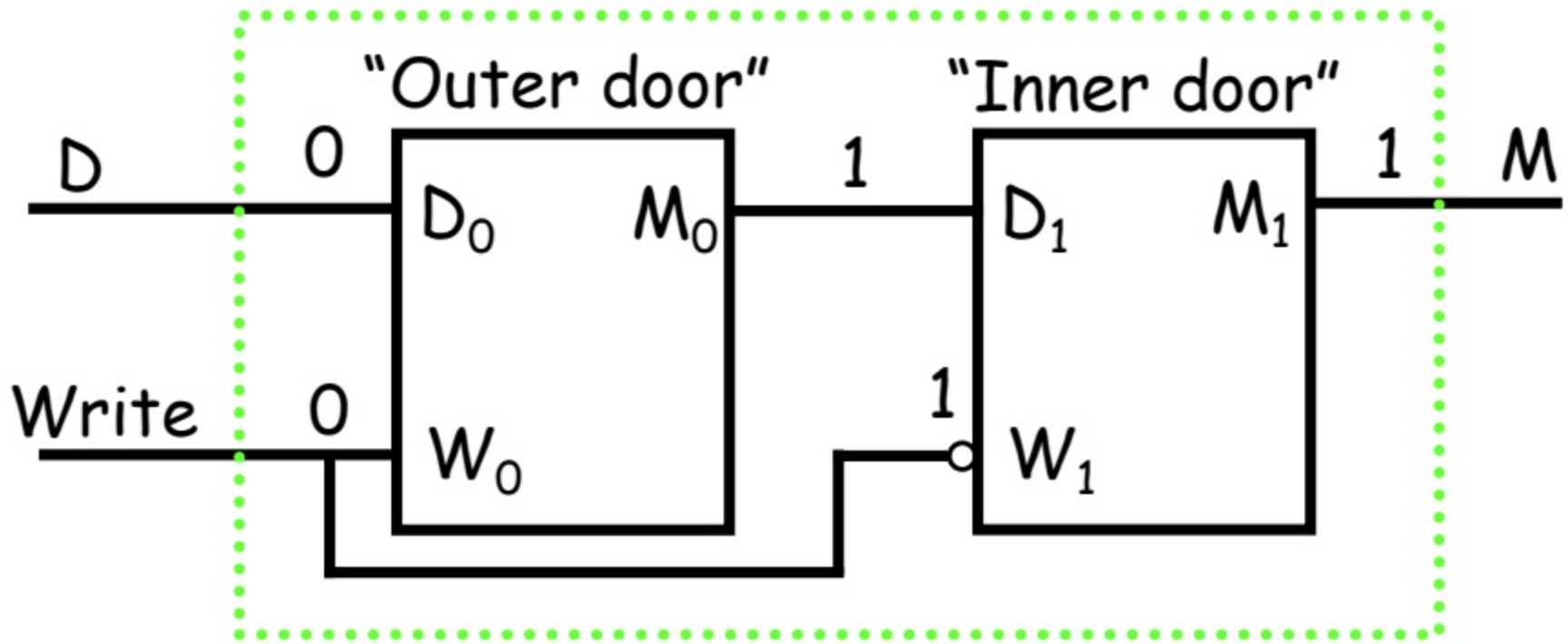


- We start with $Write = 0$.
- Let's say D is always NOT M .
Start with $D = 0, M = 1$.

"Airlock" Flip-Flop

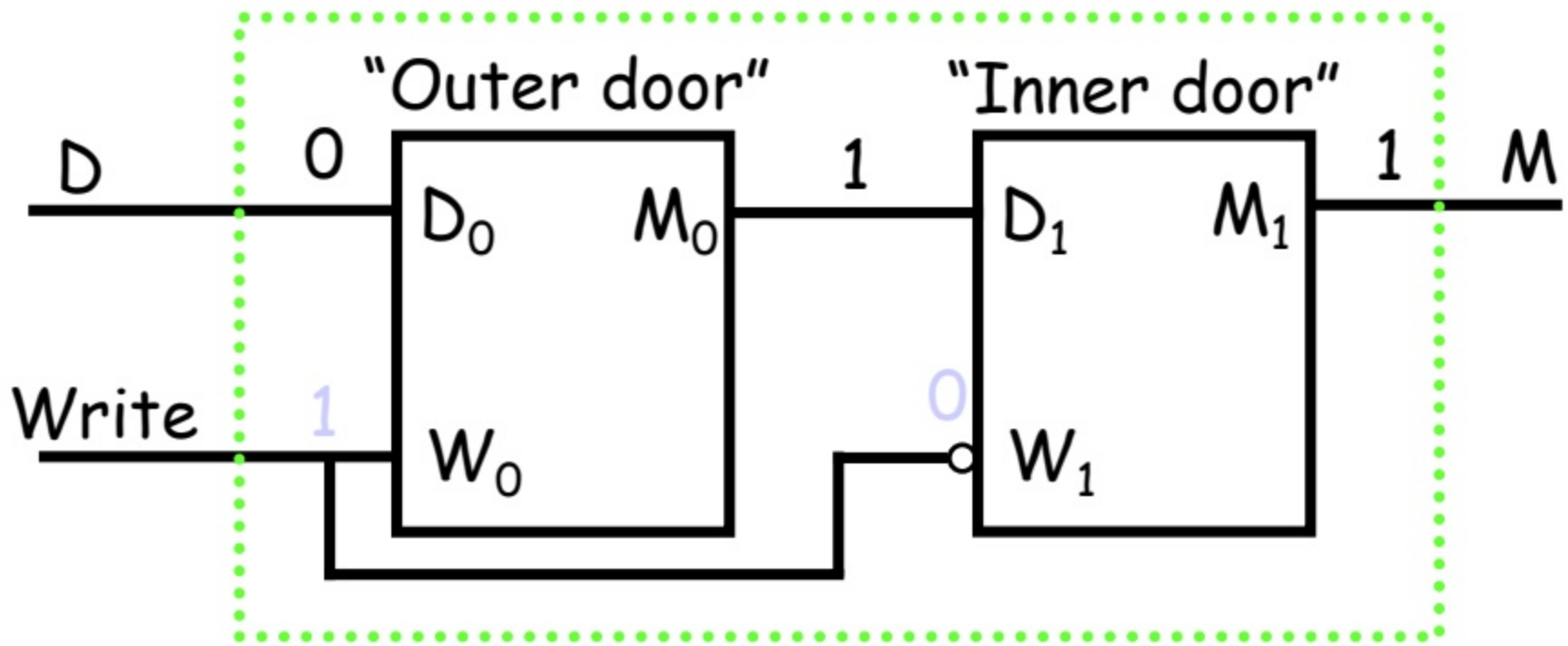


- Want to store D in memory.
- Set $Write$ to 1

"Airlock" Flip-Flop

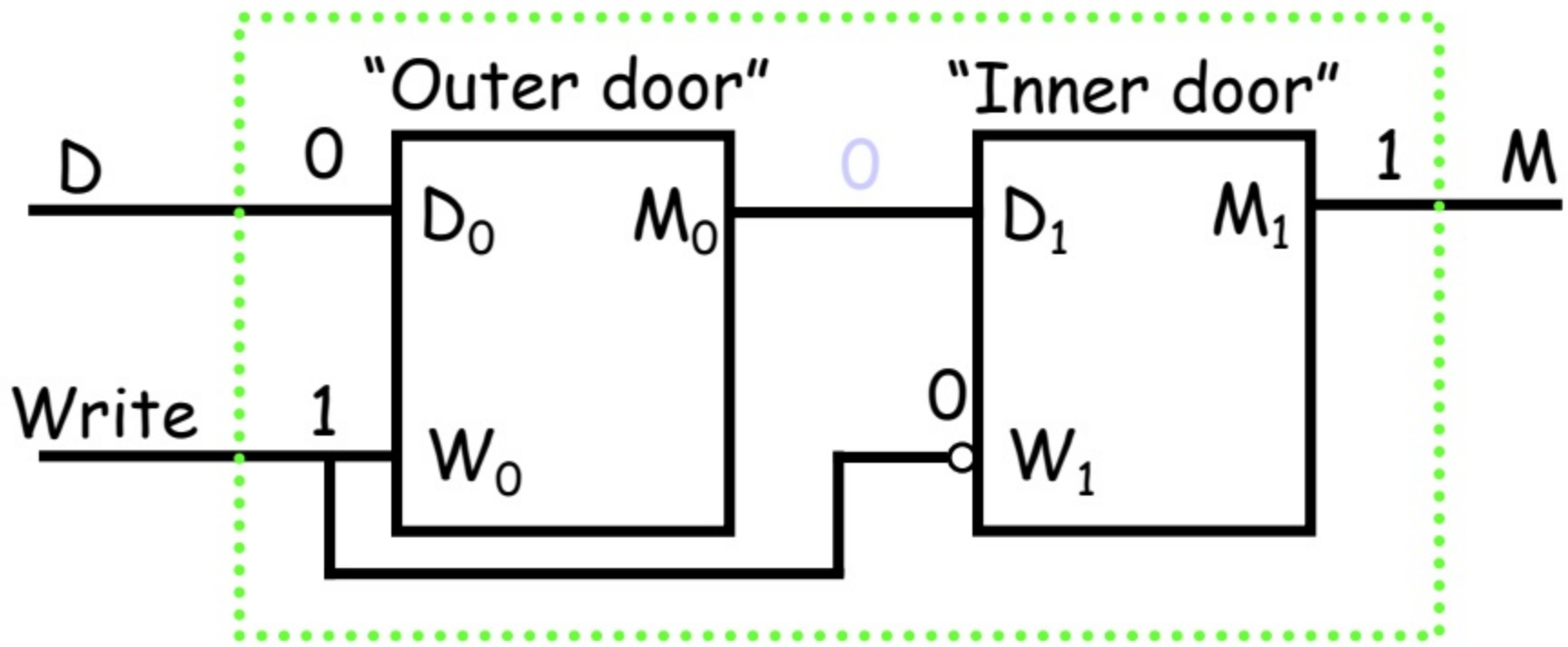


- Want to store D in memory.
- Set Write to 1
- "Outer" flip-flop sets $M_0 = D_0 = 0$
- "Inner" flip-flop ignores D_1 since $W_1 = 0$

"Airlock" Flip-Flop

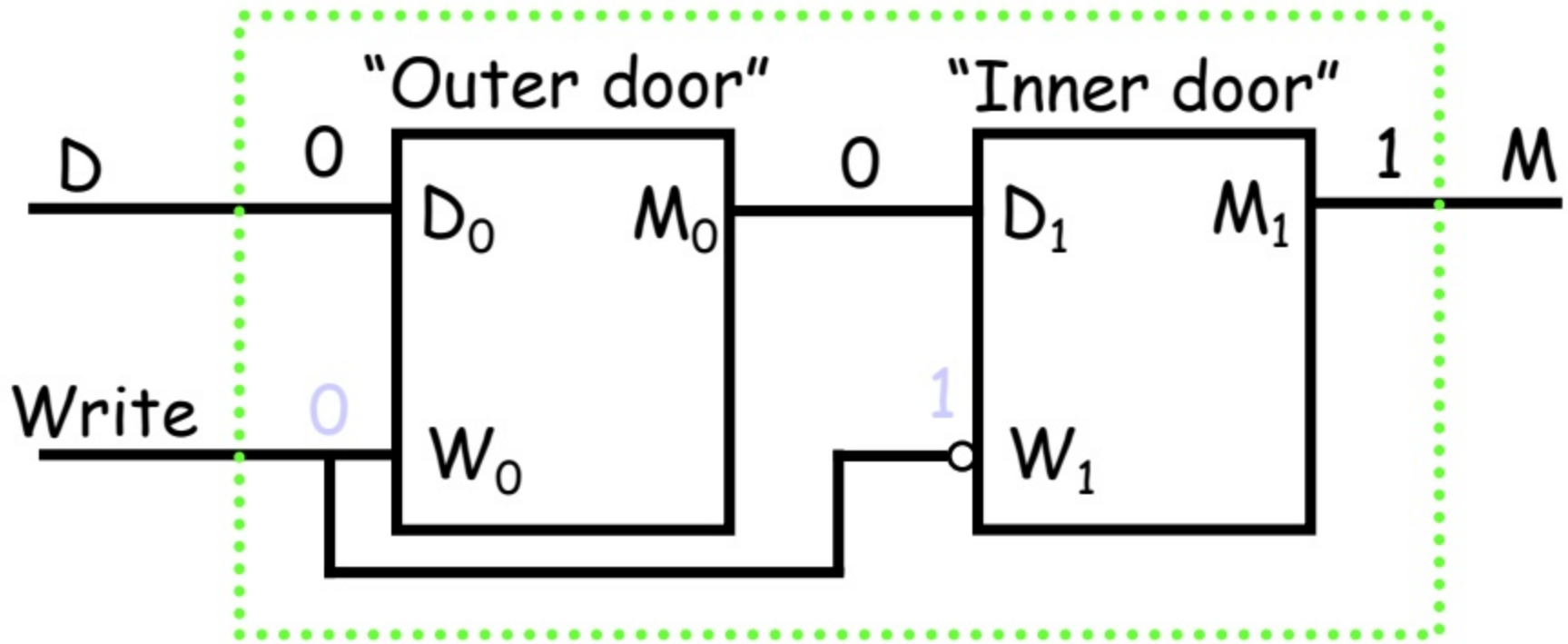


- Now, set $Write$ back to 0

"Airlock" Flip-Flop

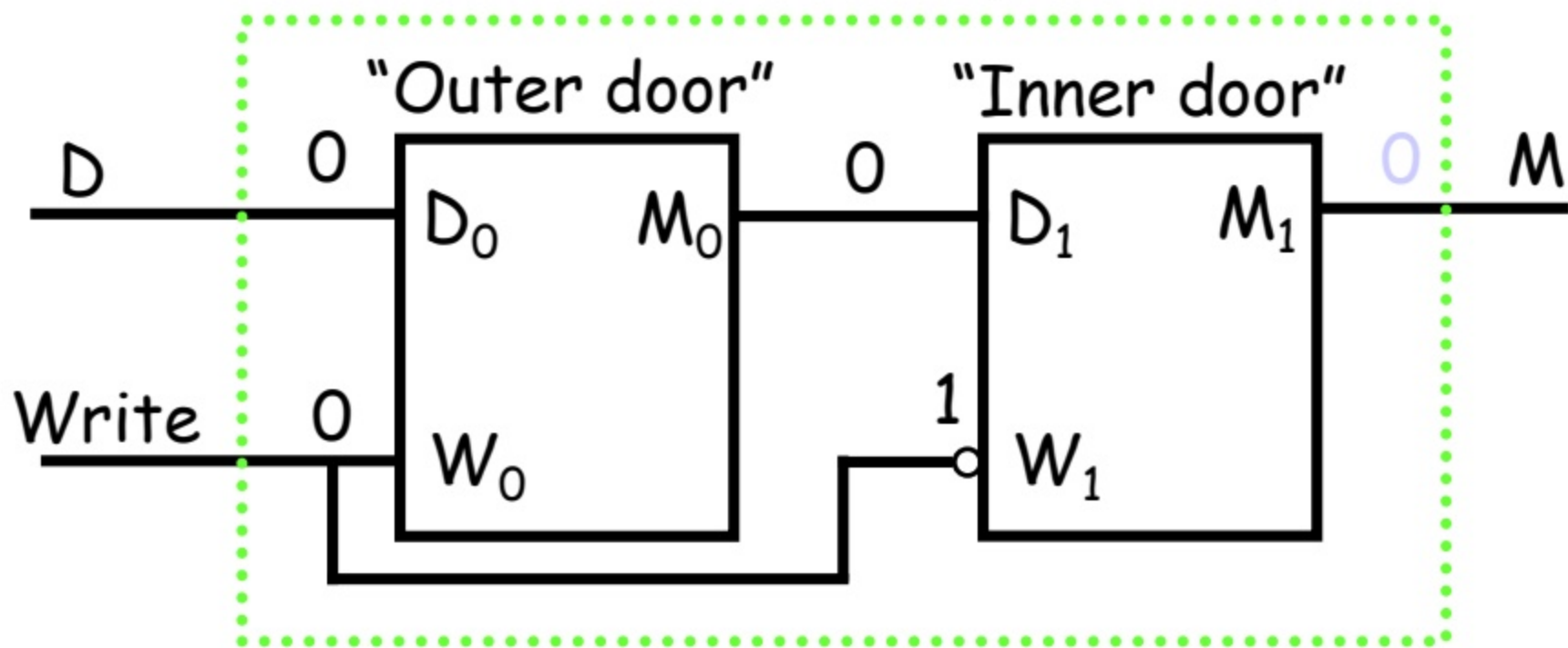


- Now, set $Write$ back to 0
- Now "Inner" flip-flop sets $M = D_1 = 0$

"Airlock" Flip-Flop

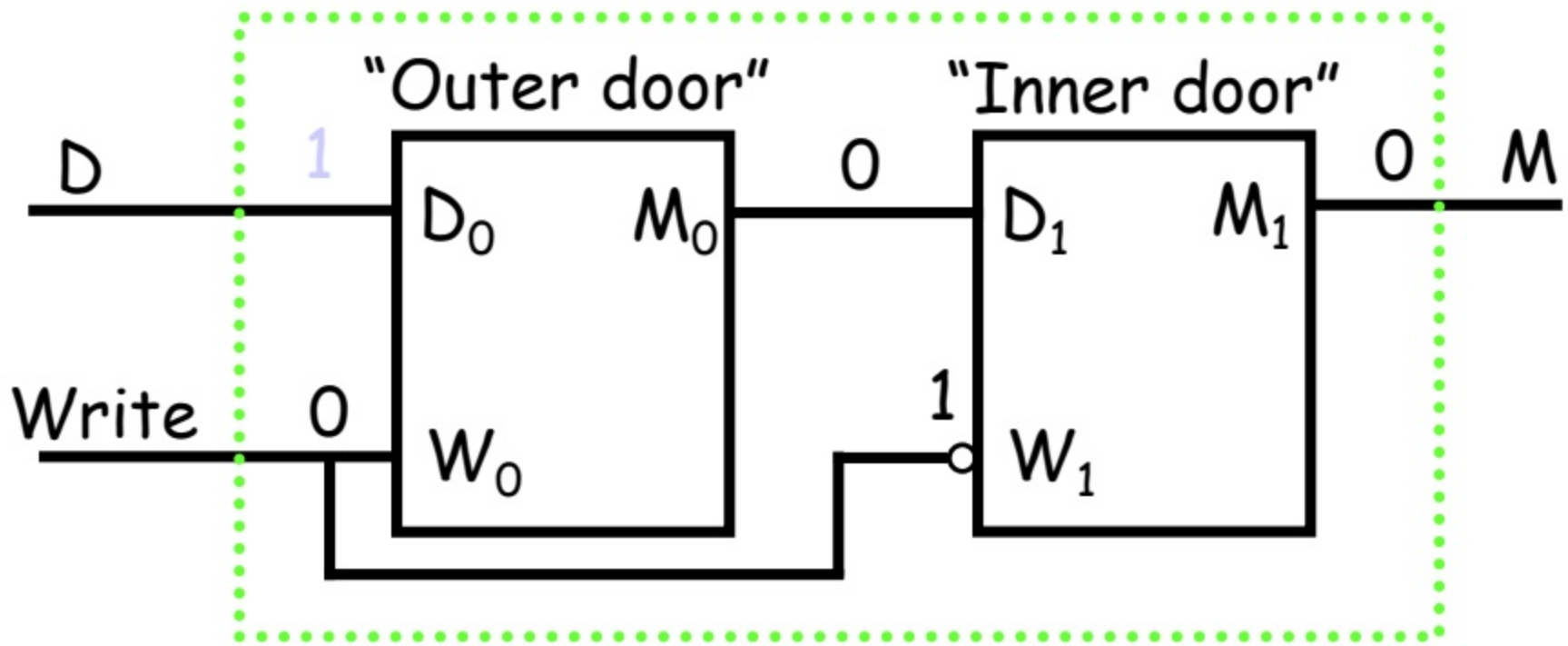


- Because of feedback, D might change to (NOT M), which is 1
- But $Write = 0$, so "Outer" flip-flop ignores D , and so M_0 stays 0.

"Airlock" Flip-Flop

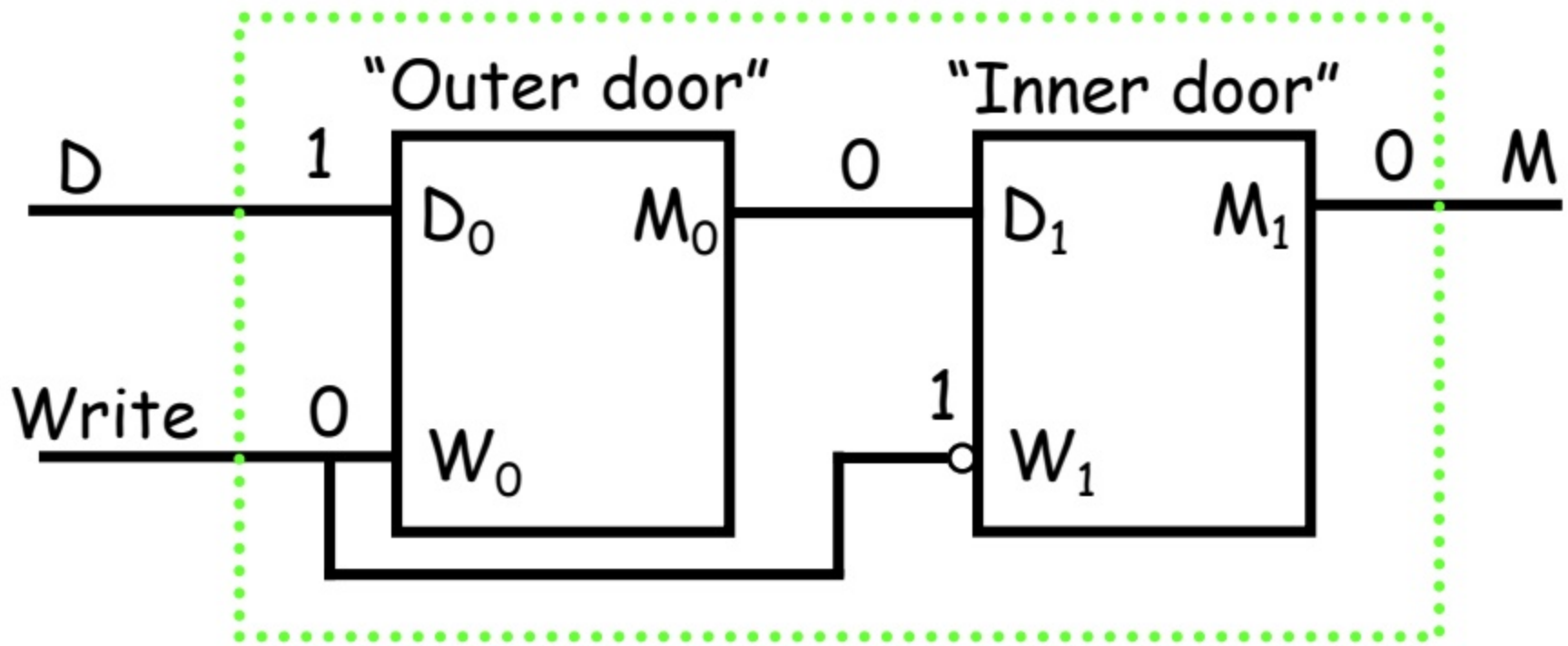


- So memory does not change until we "toggle" Write.
- ("toggle" means change from 0 to 1 or vice versa)

"Airlock" Flip-Flop

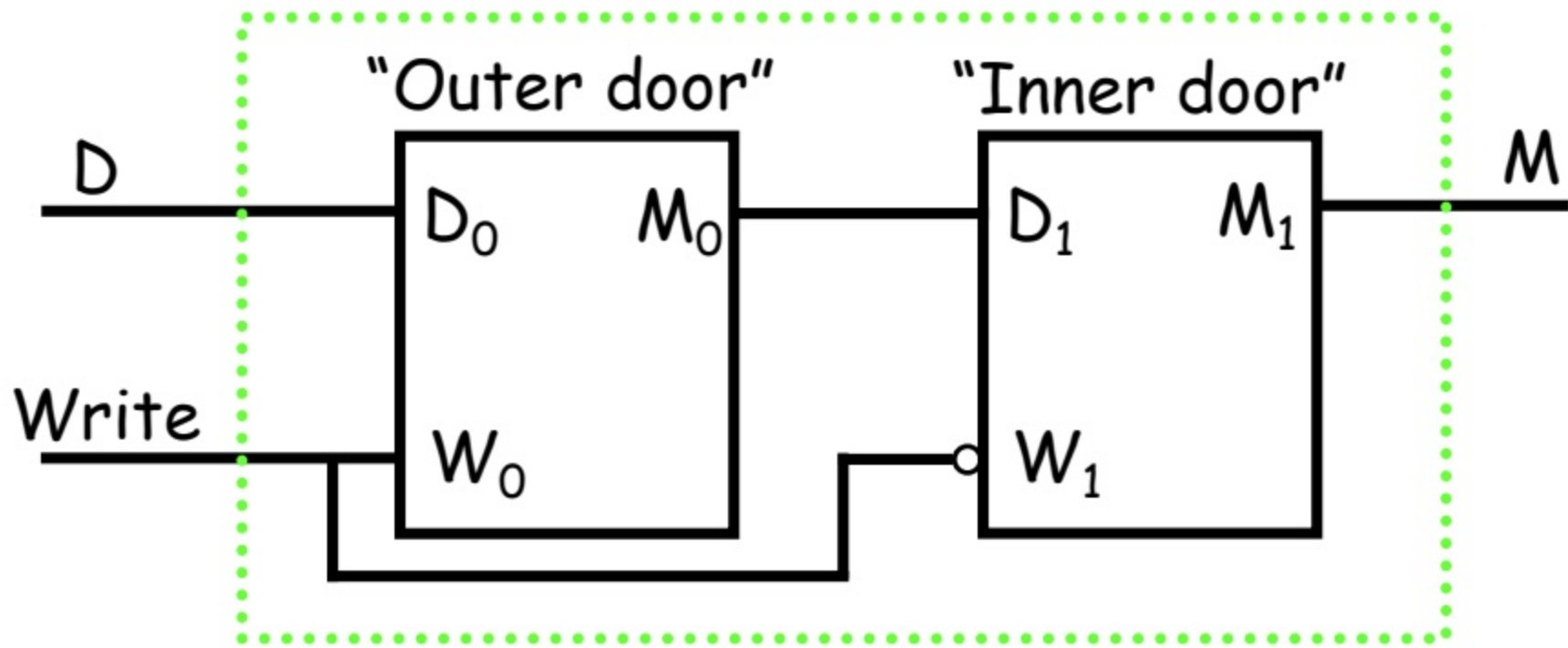

- This is Real Memory!

Memory "Register": 4 bits

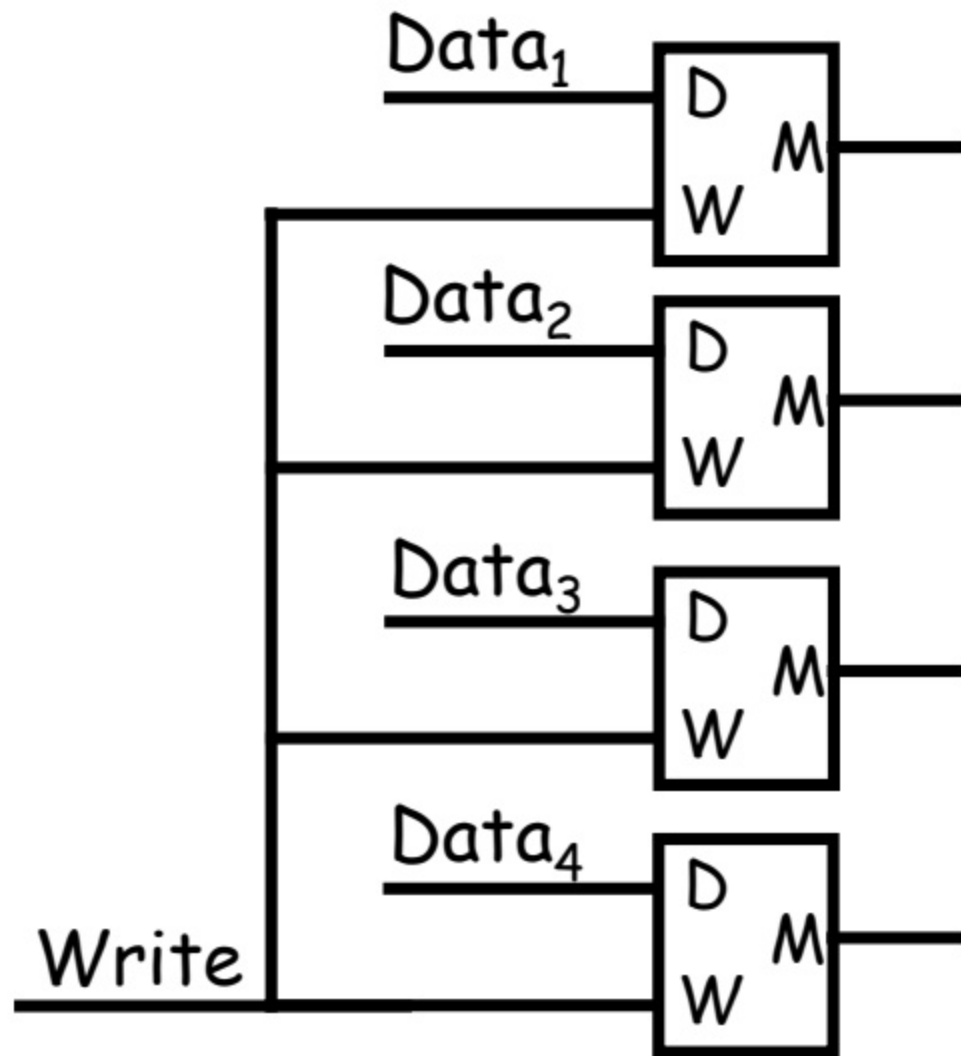

Review

- We have used the Universal method to build
 - ALU
 - Memory
- Next steps
 - State machines to computer with memory
 - Building the computer
 - Writing a program to use the computer