

De-Morgan's Theorem

A famous mathematician **DeMorgan** invented the two most important theorems of boolean algebra. The DeMorgan's theorems are used for mathematical verification of the equivalency of the NOR and negative-AND gates and the negative-OR and NAND gates. These theorems play an important role in solving various boolean algebra expressions. In the below table, the logical operation for each combination of the input variable is defined.

Input variables		Output Condition			
A	B	AND	NAND	OR	NOR
0	0	0	1	0	1
0	1	0	1	1	0
1	0	0	1	1	0
1	1	1	0	1	0


The rules of De-Morgan's theorem are produced from the Boolean expressions for **OR**, **AND**, and **NOT** using two input variables x and y. The first theorem of Demorgan's says that if we perform the AND operation of two input variables and then perform the NOT operation of the result, the result will be the same as the OR operation of the complement of that variable. The second theorem of DeMorgan says that if we perform the OR operation of two input variables and then perform the **NOT** operation of the result, the result will be the same as the AND operation of the complement of that variable.

De-Morgan's First Theorem

According to the first theorem, the complement result of the AND operation is equal to the OR operation of the complement of that variable. Thus, it is equivalent to the **NAND** function and is a negative-OR function proving that $(A.B)' = A'+B'$ and we can show this using the following table.

Inputs		Output For Each Term				
A	B	A.B	(A.B)'	A'	B'	A'A+B'
0	0	0	1	1	1	1


0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

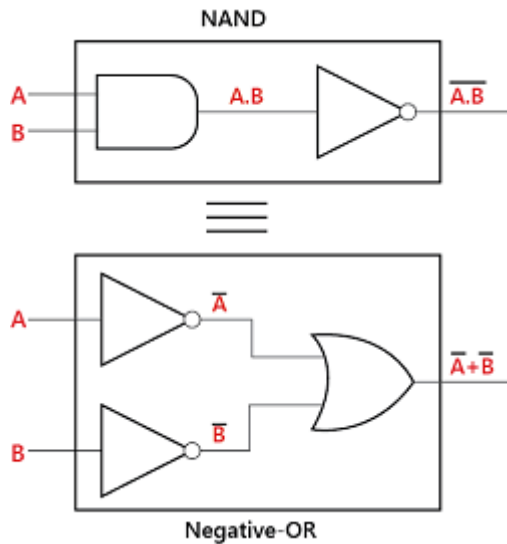

De-Morgan's Second Theorem

According to the second theorem, the complement result of the OR operation is equal to the AND operation of the complement of that variable. Thus, it is the equivalent of the NOR function and is a negative-AND function proving that $(A+B)' = A'.B'$ and we can show this using the following truth table.

Inputs		Output For Each Term				
A	B	A+B	$(A+B)'$	A'	B'	A'.B'
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

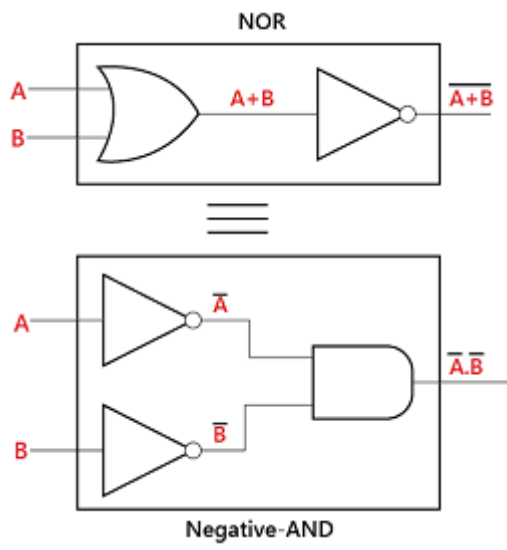

References:

<https://www.javatpoint.com/>